

ANALOG INTERFACING AND INDUSTRIAL CONTROL (PART I)


Book: Microprocessors and Interfacing-Douglas V. Hall (Chapter 10)

Prepared By: Anika Binte Islam, Lecture, CSE Dept, MIST

Embedded System

- ❑ A computer hardware system having software embedded in it.
- ❑ An independent system or it can be a part of a large system.
- ❑ A microcontroller or microprocessor based system which is designed to perform a specific task.
- ❑ For example, a fire alarm is an embedded system; it will sense only smoke.
- ❑ An embedded system has three components
 - ❑ It has hardware.
 - ❑ It has application software.
 - ❑ It has Real Time Operating system (RTOS) that defines the way the system works. It sets the rules during the execution of application program.
- ❑ We can define an embedded system as a Microcontroller based, software driven, reliable, real-time control system.

Basic Structure of An Embedded System

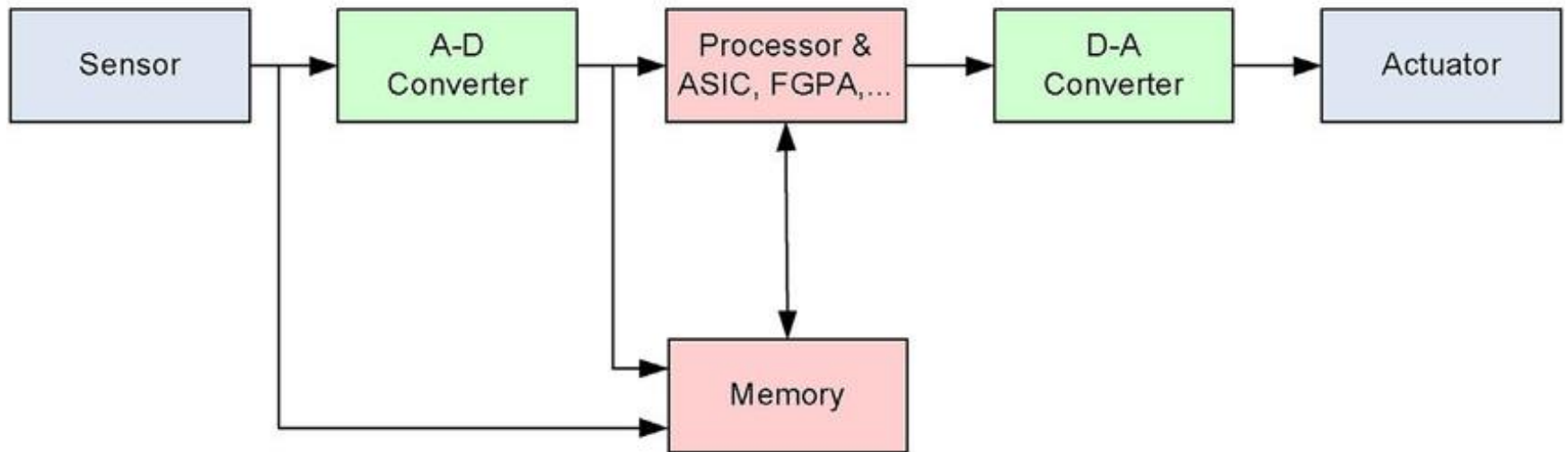

Basic Structure of An Embedded System


- ❑ **Sensor** – It measures the physical quantity and converts it to an electrical signal which can be read by an observer or by any electronic instrument like an A/D converter. A sensor stores the measured quantity to the memory.
- ❑ **A-D Converter** – An analog-to-digital converter converts the analog signal sent by the sensor into a digital signal.
- ❑ **Processor & ASICs** – Processors process the data to measure the output and store it to the memory.
- ❑ **D-A Converter** – A digital-to-analog converter converts the digital data fed by the processor to analog data
- ❑ **Actuator** – An actuator compares the output given by the D/A Converter to the actual (expected) output stored in it and stores the approved output.

D/A CONVERTER OPERATION, INTERFACING AND APPLICATIONS

- ❑ Why D/A converter?
 - ❑ Simpler
 - ❑ Several A/D converters have D/A as part of their circuitry.
 - ❑ So, we will discuss D/A converters first.

D/A Converter: Operation

- ❑ The purpose of a Digital to Analog converter is to convert a binary word to a proportional current or voltage
- ❑ In a simple 4 bit D/A converter , inverting input of the circuit is referred to as the summing point
- ❑ When one of the switches is closed, current will flow from $-V$ to the summing point
- ❑ The equation of O/P voltage, $V_{out} = - R_f / R (V_{in})$
- ❑ If we close the switch D0 , $V_{out} = - 10 / 100(-5) = 0.5 \text{ V}$
- ❑ If we close the switch D0 & D1 , $V_{out} = - 10 / 33.33(-5) = 1.5 \text{ V}$
- ❑ The point here is that, binary weighted resistors produce currents which are summed by the op amp to produce a proportional output voltage
- ❑ The heart of a D/A converter is a set of binary weighed current sources which can be switched on or off according to a binary word applied to its input

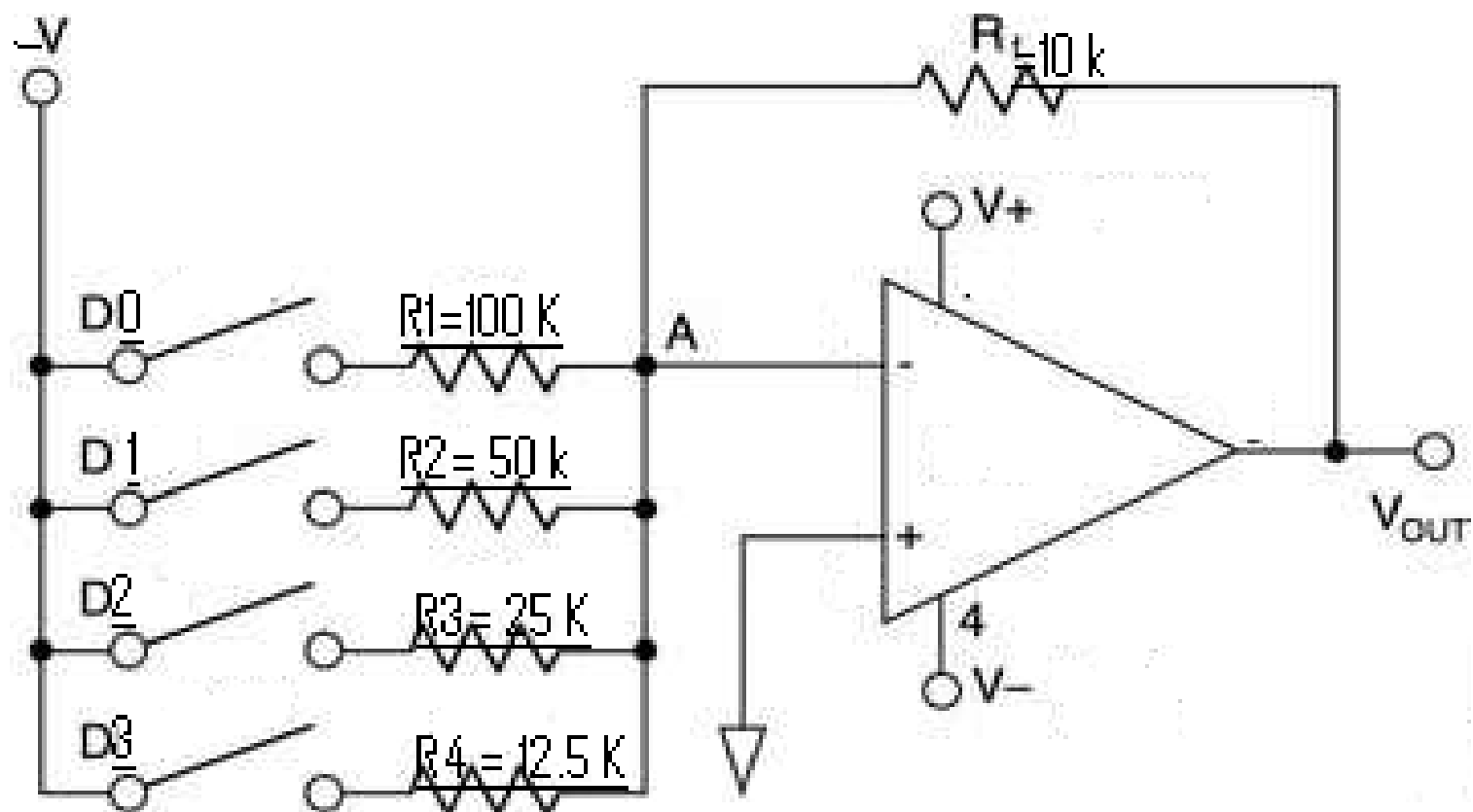

D/A Converter: Characteristics

❖ Resolution

- ❑ The minimum possible change at the o/p for any change in the digital i/p.
- ❑ This is determined by the number of bits in the input binary word.
- ❑ A converter with 8 binary inputs has 2^8 or 256 possible output levels.
- ❑ Thus its resolution is 1 part in 256.

➤ Example:

- ❑ 12 bit converter has a resolution of 1 part in 2^{12} or 4096.
- ❑ Resolution is sometimes expressed in percentage.
- ❑ The resolution of an 8 bit converter can be expressed as a percentage is $(1/256) \times 100$ percent or 0.39 percent.

D/A Converter: Characteristics

❖ Full scale output voltage

- ❑ The maximum output voltage of a converter will always have a value 1 least significant bit less than the named value.

➤ Example:

- ❑ 12 bit, 10-V converter
- ❑ The value of 1 LSB = $(10\text{V})/4096 = 2.44\text{mV}$
- ❑ The highest voltage output for the converter when it is properly adjusted will then be : $(10 - 0.0024)\text{V}$ or 9.9976V .

D/A Converter: Characteristics

❖ Accuracy

- ❑ The accuracy specification for a D/A converter is a comparison between the actual output and the expected output
- ❑ It is specified as a percentage of the full scale output voltage or current

➤ Example

- ❑ If the converter has a output of 10V and ± 0.2 percent accuracy
- ❑ Maximum error for any output will be $0.002 * 10V$ or 20mV

D/A Converter: Characteristics

❖ **Linearity**

- ❑ Linearity is the measure of how much the output ramp deviates from a straight line as the converter is stepped from no switches on to all switches on
- ❑ Ideally the deviation of the output from a straight line should be no greater than $\pm \frac{1}{2}$ the value of LSB to maintain overall accuracy

D/A Converter: Characteristics

❖ Settling Time

- ❑ When we change the binary word applied to the input of a converter, the output will change to the appropriate new value
- ❑ The output may overshoot the correct value, “ring” for a while before finally settling down to the correct value
- ❑ The time the output takes to get within $\pm \frac{1}{2}$ LSB of the final value is called settling time
- ❑ This specification is important, because if a converter is operated at too high frequency, it may not have time to settle to one value before it is switched to the next

D/A Converter: Interfacing to Microcomputers

- ❑ The inputs of the D/A circuit can be connected directly to the microcomputer output port
- ❑ Thus interfacing an 8 bit converter involves simply connecting the inputs of the converter to an output port
- ❑ For some application we need to interface a 12 bit converter to a microcomputer
- ❑ If we are working with a system which has an 8 bit data bus
 - ❑ The first thought might be – to connect the lower 8 inputs of the 12 bit converter to one output port and upper 4 bits to another port
 - ❑ In that case, we could send the lower 8 bits with one write operation and the upper 4 bits with another write operation
 - ❑ Time between the two writes introduces a potential problem in this approach

D/A Converter: Interfacing to Microcomputers



Example:

- ❑ Suppose we want to change the pattern of a 12 bit converter from 0000 1111 1111 to 0001 0000 0000
- ❑ When we will write the lower 8 bits, the output will go from 0000 1111 1111 to 0000 0000 0000
- ❑ When we will write the upper 4 bits the output will go back up to the desired 0001 0000 0000
- ❑ The point here is that for the time between the two writes the output will go to an unwanted value
- ❑ In many systems this could be disastrous
- ❑ The cure of this problem is to put latches on the input lines
- ❑ The latches can be loaded separately and then strobed together to pass all 12 bits to the D/A converter at the same time

A/D Converter

- ❑ The function of an A/D converter is to produce a digital word which represents the magnitude of some analog voltage or current
- **A/D converter Specification**
 - ❖ Resolution: Same as D/A Converter
 - ❖ Accuracy: Same as D/A Converter
 - ❖ Linearity: Same as D/A Converter
 - ❖ Conversion Time
 - ❑ This is simply the time it takes the converter to produce a valid output binary code for an applied input voltage
 - ❑ When we refer to a converter as high speed , we mean that it has a short conversion time

INL

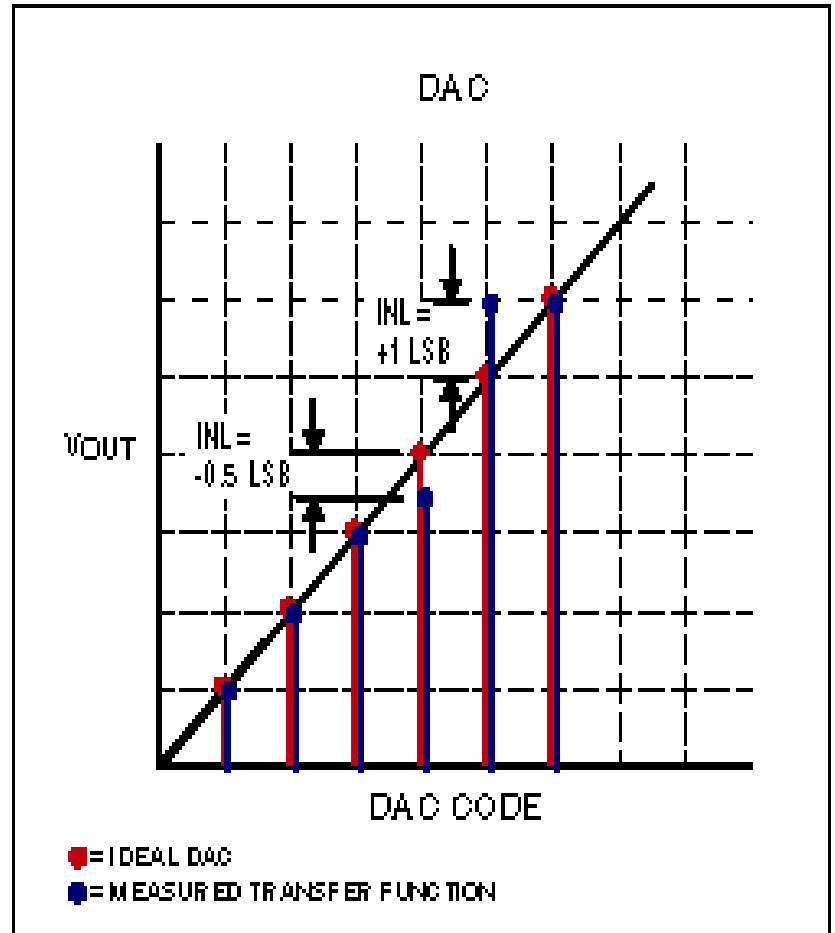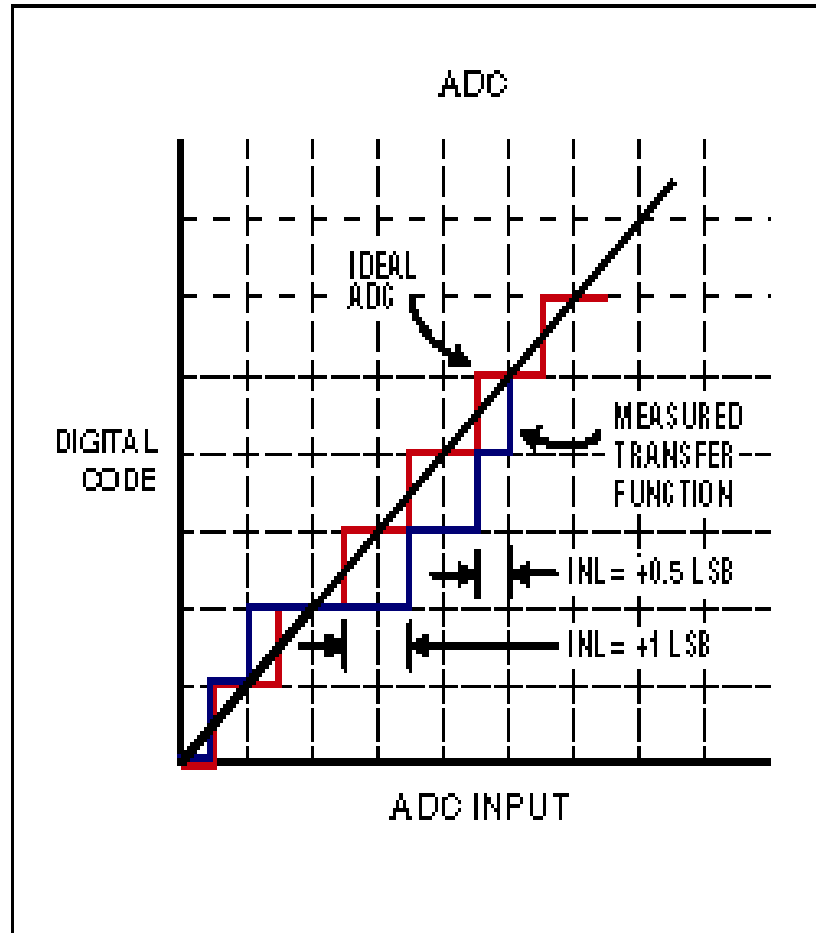


Parallel A/D Converter

- ❑ A voltage divider sets reference voltages on the inverting inputs of each of the comparators
- ❑ The voltage at the top of the divider represents the full scale value for the comparators
- ❑ The voltage to be converted is applied to the non inverting inputs of all the comparators in parallel
- ❑ If the input voltage on a comparator is greater than the reference voltage on the inverting input, the output of the comparator will go high
- ❑ The outputs of the comparators then give us a digital representation of the voltage level of the input signal

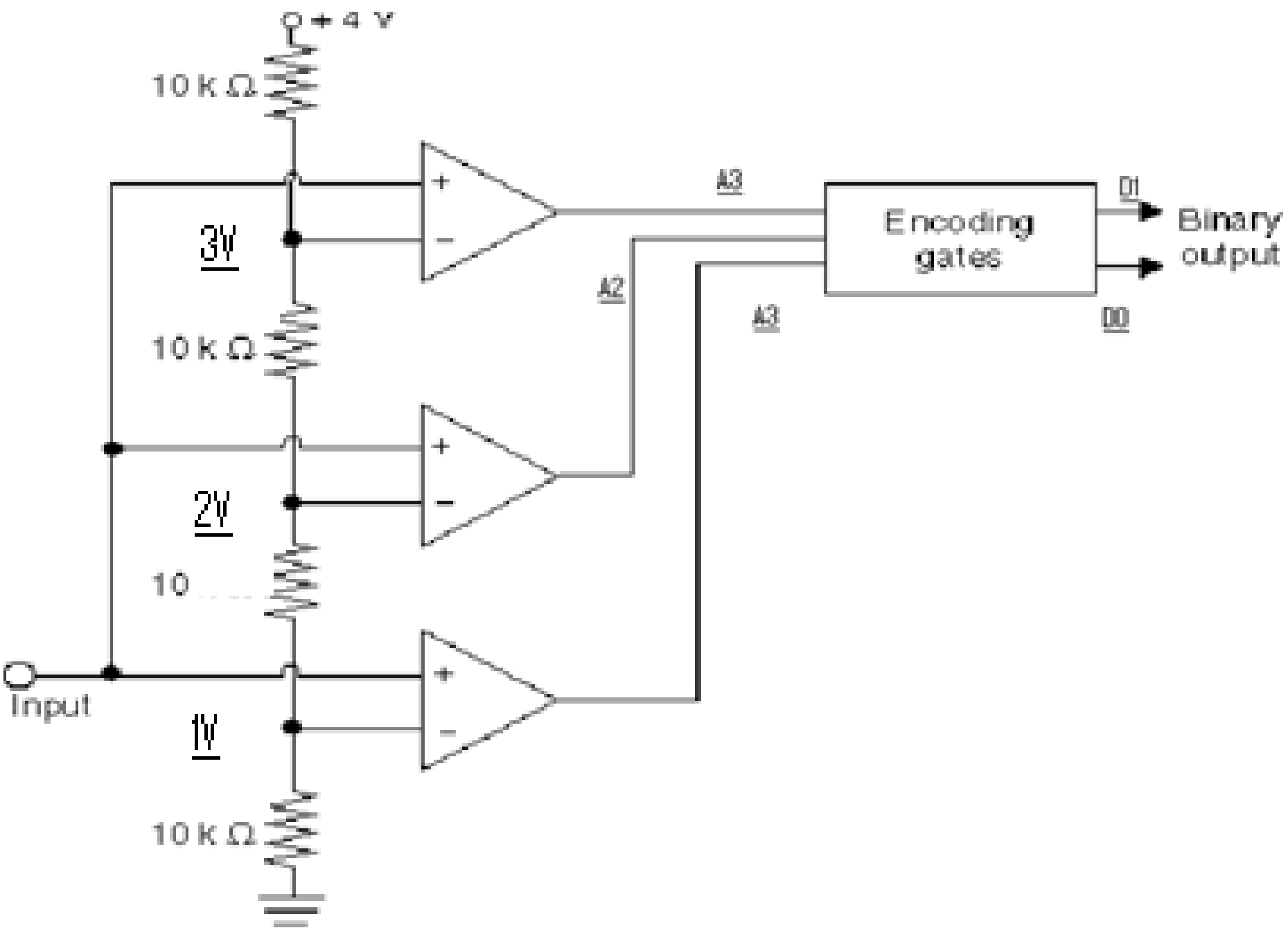Example:

- ❑ With an input voltage of 2.6V , the outputs of comparators A1 and A2 will be high



Parallel A/D Converter

Advantage:

- ❑ It is the fastest type of ADC because the conversion is performed simultaneously through a set of comparators, hence referred as flash type ADC. Typical conversion time is 100ns or less.
- ❑ The construction is simple and easier to design

Disadvantage:

- ❑ It is not suitable for higher number of bits. The number of comparators needed to produce a result with a reasonable amount of resolution
- ❑ To produce a converter with N bits of resolution we need $(2^N - 1)$ comparators

Dual-Slope A/D Converter

- ❑ Control circuitry resets all the counters to zero and connects the input of the integrator to the input voltage to be converted
- ❑ When the input voltage is positive, the output of the integrator will ramp negative
 - ❑ Comparator output will go high
 - ❑ AND gate is enabled and it lets 1 MHz clock to the counter chain
- ❑ After a fixed number of counts (typically 1000), the control circuitry switches the input of the integrator to a negative reference voltage and resets all the counters to zero
 - ❑ Integrator output ramp positive
- ❑ When integrator output crosses 0V
 - ❑ Comparator output will drop low
 - ❑ Shut of the clock signal to the counters
- ❑ The number of counts required for the integrator output to get back to zero is directly proportional to the input voltage


Dual-Slope A/D Converter

Advantage:


- ❑ Large number of bits of resolution at low cost

Disadvantage:

- ❑ Slow speed

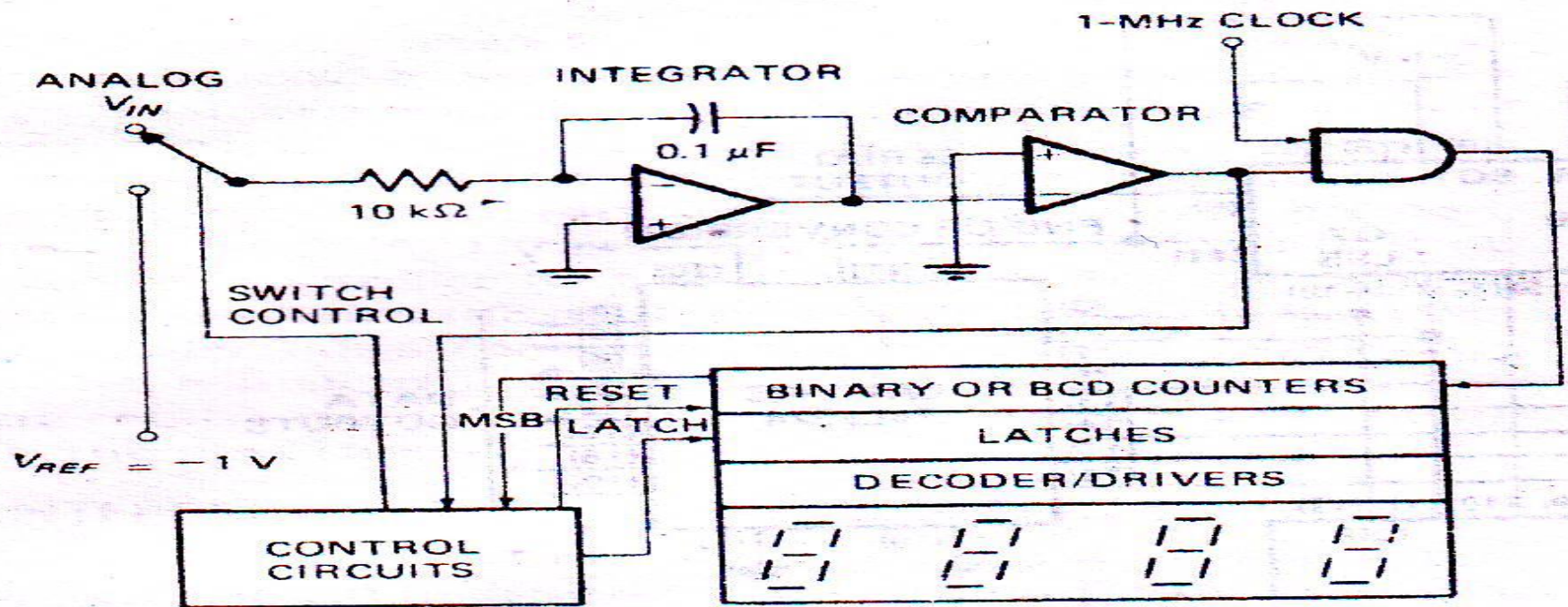

(a)

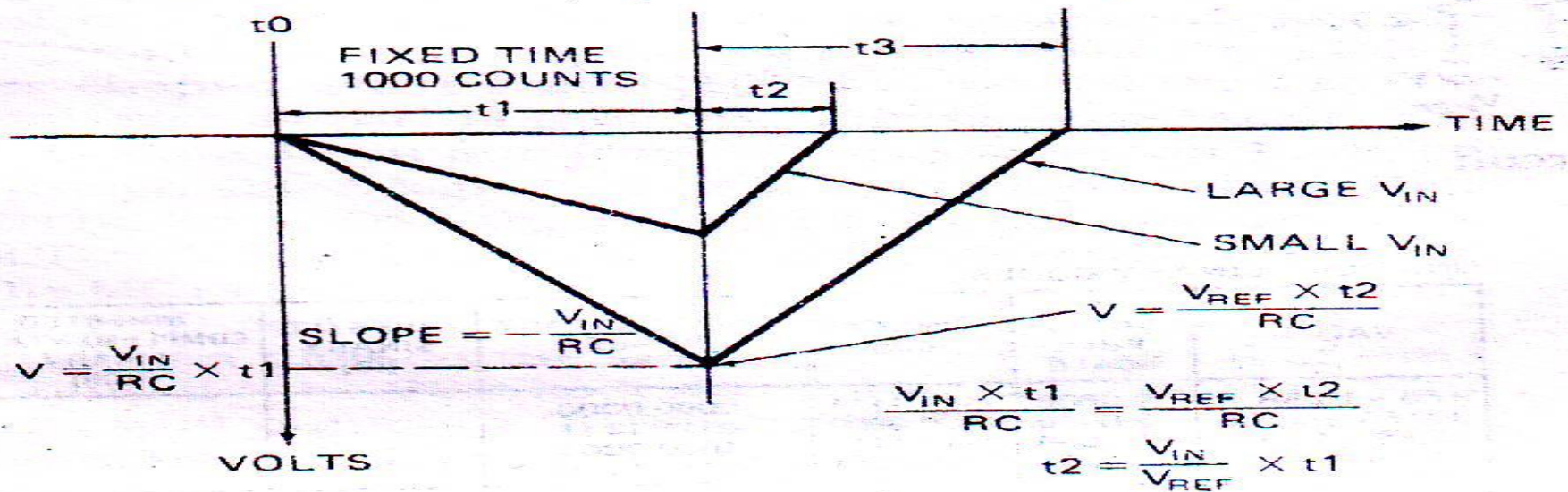


(b)

Successive Approximation Resister (SAR)


- ❑ The heart of this converter is *Successive Approximation Resister (SAR)*
- ❑ On the first clock pulse, at the start of a conversion cycle, the SAR outputs a high on its most-significant bit to the D/A converter
- ❑ The D/A converter and the amplifier convert this to a voltage and apply it to one input of a comparator
- ❑ If this voltage is higher than the input voltage on the other input of the comparator, the comparator output will go low and tell the SAR to turn off that bit- because it is too large
- ❑ If the voltage from the D/A converter is less than the input voltage, then the comparator output will be high , which tells the SAR to keep that bit on
- ❑ When the next clock pulse occurs, the SAR will turn on the next most-significant bit to the D/A converter

Successive Approximation Resister (SAR)

- ❑ Based on the answer this produces from the comparator, the SAR will keep or Reset this bit
- ❑ SAR will proceed in this way on down to the Least-significant bit adding each bit to the total in turn and using the signal from the comparator to decide whether to keep that bit in the result
- ❑ Only 9 clock pulses are required to do the actual conversion
- ❑ When the conversion is complete, binary results will be now on the parallel outputs of SAR
- ❑ SAR sends out an End-of-conversion(EOC) signal to indicate the conversion is complete
- ❑ EOC is used to strobe the binary result into latches, where it can be read by a microcomputer

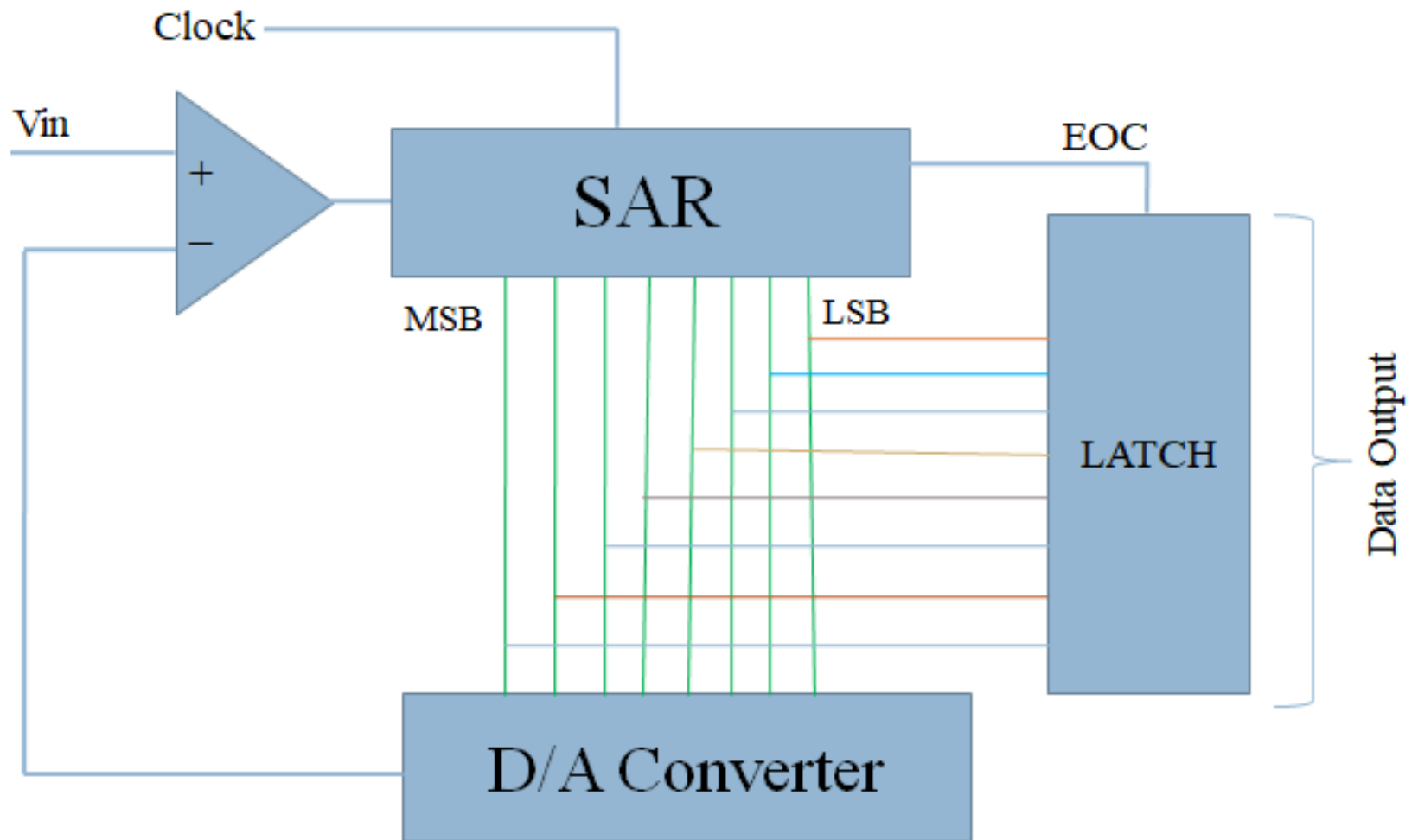

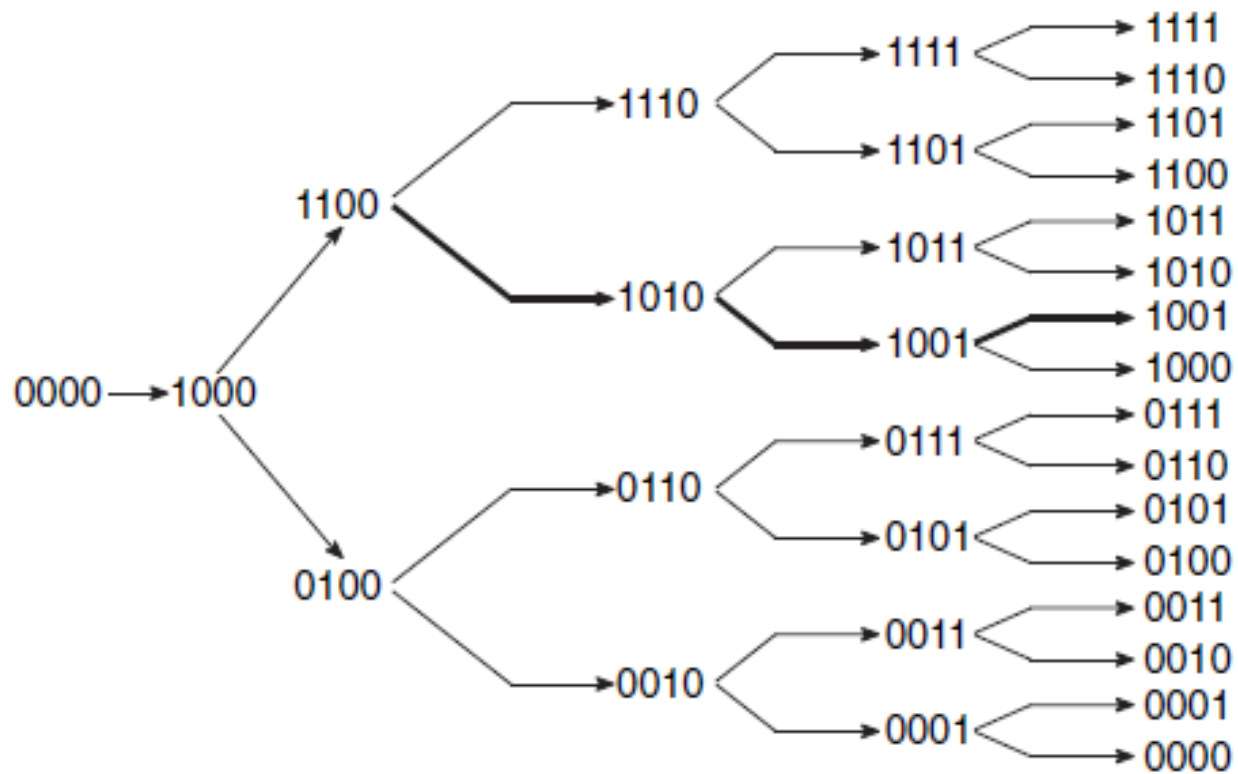8 Bit Successive approximation A/D converter



Conversion process in a successive approximation type A/D converter.

Successive Approximation Resister (SAR)

❑ **Advantages:**

- ❑ Conversion time is very small.
- ❑ Conversion time is constant and independent of the amplitude of the analog input signal V_A .

❑ **Disadvantages:**

- ❑ Circuit is complex.
- ❑ The conversion time is more compared to flash type ADC.