

Appendixes

APPENDIX 1. THE ANALOG INTERFACE

The data in a microprocessor is in digital form. This differs from the outside world where data is in analog (continuous) form. To get digital data, we need to use an *analog-to-digital (A/D) converter*; it will convert analog voltage or current into an equivalent digital word.

Conversely, after a CPU has processed data, it is often necessary to convert the digital answer into an analog voltage or current. This conversion requires a *digital-to-analog (D/A) converter*.

The *analog interface* is the boundary where digital and analog meet, where the microcomputer connects to the outside world. At this interface, we find either an A/D converter (input side) or a D/A converter (output side). This chapter discusses some of the hardware and software found at the analog interface.

A1-1 OP-AMP BASICS

Let us briefly review the *operational amplifier* (op amp) because this device is used with D/A and A/D converters. We will zero in on the key features that make the op amp useful at the analog interface.

 


Fig. A1-1 Operational amplifier.


Virtual Ground

Figure A1-1 shows the symbol for an op amp. V_{OUT} is the output voltage with respect to ground. A is the open-loop voltage gain of the op amp, often more than 100,000. When connected as an inverter, the noninverting input (+ input) is grounded. The inverting input (− input) receives the signal voltage.


Because the voltage gain of an op amp is so large, the input voltage is in microvolts. To a first approximation, the

input voltage may be treated as 0 V. Furthermore, the input impedance of the inverting input approaches infinity (sometimes FETs are used for the input stage, as in BIFET op amps). These key features, zero input voltage and infinite input impedance, make the inverting input a *virtual ground point*.

How is a virtual ground different from an ordinary ground? An ordinary ground has zero voltage while sinking any amount of current. A virtual ground, however, is a ground for voltage but not for current; it has zero voltage but can sink no current. In the discussion that follows, we will approximate the inverting input of an op amp as a virtual ground point: this means zero voltage and zero current.

 

(a)

 

(b)

Fig. A1-2 Output current equals input current.

Output Voltage and Current

Figure A1-2a shows an inverting op amp with input and output resistors. V_{IN} is the input voltage with respect to ground, and V_{OUT} is the output voltage with respect to ground. Because of the high gain and input impedance, we

can approximate the inverting input as a virtual ground point. Therefore, all the input voltage appears across the input resistor, which means that the input current is

$$I = \frac{V_{IN}}{R_{IN}} \quad (\text{A1-1})$$

Since none of the input current can enter the virtual ground point, it must pass through the output resistor. In other words, the output current equals the input current. And the output voltage is

$$V_{OUT} = -IR_{OUT} \quad (\text{A1-2})$$

The minus sign indicates phase inversion. If the input voltage is positive, the output voltage is negative.

As an example of calculating input current and output voltage, look at Fig. A1-2b. The input current is

$$I = \frac{5 \text{ V}}{2.5 \text{ k}\Omega} = 2 \text{ mA}$$

The output voltage is

$$V_{OUT} = -2 \text{ mA} \times 1 \text{ k}\Omega = -2 \text{ V}$$

 


Fig. A1-3 Output current equals sum of input currents.

Summing Circuit

Figure A1-3 is an op-amp circuit whose output current is the *sum* of the input currents. Here is the proof. Because of the virtual ground point, each input voltage appears across its resistor. This means that the input currents are

$$I_3 = \frac{V_3}{R_3} \quad I_2 = \frac{V_2}{R_2} \quad I_1 = \frac{V_1}{R_1} \quad I_0 = \frac{V_0}{R_0}$$

Kirchhoff's current law gives a total input current of

$$I = I_3 + I_2 + I_1 + I_0$$

Again, the virtual ground guarantees that all this input current goes through the output resistor. As before,

$$V_{OUT} = -IR_{OUT}$$

A1-2 A BASIC D/A CONVERTER

The op-amp summing circuit can be used to build a D/A converter by selecting input resistors that are weighted in binary progression. Figure A1-4 gives you the idea. V_{REF} is an accurate reference voltage, and the resistors are precision resistors to get accurate input currents. The switches can be open or closed. When all switches are open, all input currents are zero and the output current is zero.

All Bits High

When all switches are closed, the input currents are

$$I_3 = \frac{V_{REF}}{R} \quad I_2 = \frac{V_{REF}}{2R} \quad I_1 = \frac{V_{REF}}{4R} \quad I_0 = \frac{V_{REF}}{8R}$$

 


Fig. A1-4 D/A conversion with binary-weighted resistors.

The output current with all switches closed is the sum of all input currents and equals

$$I = \frac{V_{REF}}{R} (1 + 0.5 + 0.25 + 0.125) \quad (A1-3)$$

$$I = 1.875 \frac{V_{REF}}{R}$$

By opening and closing switches we can produce 16 different output currents from 0 to $1.875V_{REF}/R$.

Any Digital Input

If 0 stands for an open switch and 1 for a closed switch, we can rewrite Eq. A1-3 as

$$I = \frac{V_{REF}}{R} (D_3 + 0.5D_2 + 0.25D_1 + 0.125D_0) \quad (A1-4)$$

In powers of 2,

$$I = \frac{V_{REF}}{R} (D_3 + 2^{-1}D_2 + 2^{-2}D_1 + 2^{-3}D_0) \quad (A1-5)$$

This says that the output current is the sum of binary-weighted input currents. In other words, we have a D/A converter. For instance, suppose $V_{REF} = 5$ V and $R = 5$ k Ω . Then the total output current varies from 0 to 1.875 mA, as shown in Table A1-1.

Current Switches

Figure A1-5 shows how we can transistorize the switching. Data bits D_3 through D_0 drive the bases of the transistors through the current-limiting resistors. When a bit is high, it produces enough base current to saturate its transistor. When a bit is low, the transistor is cut off. Since each transistor is saturated or cut off, it acts like a closed or

TABLE A1-1. WEIGHTED D/A CONVERTER

D_3	D_2	D_1	D_0	Output current, mA	Fraction of maximum
0	0	0	0	0	0
0	0	0	1	0.125	$\frac{1}{15}$
0	0	1	0	0.25	$\frac{2}{15}$
0	0	1	1	0.375	$\frac{3}{15}$
0	1	0	0	0.5	$\frac{4}{15}$
0	1	0	1	0.625	$\frac{5}{15}$
0	1	1	0	0.75	$\frac{6}{15}$
0	1	1	1	0.875	$\frac{7}{15}$
1	0	0	0	1	$\frac{8}{15}$
1	0	0	1	1.125	$\frac{9}{15}$
1	0	1	0	1.25	$\frac{10}{15}$
1	0	1	1	1.375	$\frac{11}{15}$
1	1	0	0	1.5	$\frac{12}{15}$
1	1	0	1	1.625	$\frac{13}{15}$
1	1	1	0	1.75	$\frac{14}{15}$
1	1	1	1	1.875	$\frac{15}{15}$

open switch. (Base resistance is not critical; it need only be less than collector resistance multiplied by β_{dc} .)

If the lower 4 bits of an output port are connected to D_3 to D_0 , the circuit of Fig. A1-5 will convert digital data to analog current. For instance, assume port 22H has been programmed as an output port in a minimum system. If the lower 4 bits of port 22H are connected to D_3 to D_0 , this program segment will operate the D/A converter:

Label	Mnemonic	Comment
	MVI A, FFH	;Initialize accumulator
LOOP:	INR A	;Count up
	OUT 22H	;Output nibble
	JMP LOOP	;Get next nibble

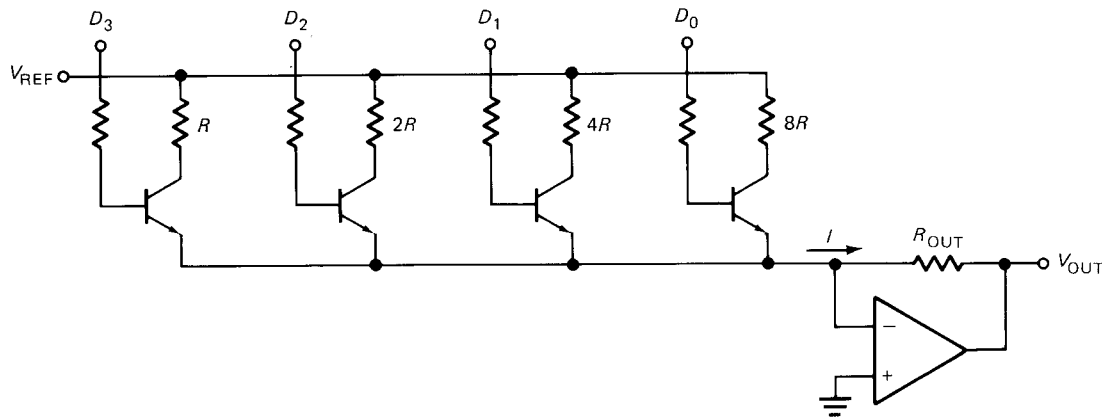


Fig. A1-5 Transistor switches for D/A converter.

 


Fig. A1-6 (a) Staircase output current; (b) each step equals an LSB increment.

The first INR A produces accumulator contents of 00H. Subsequent INR executions produce 01H, 02H, . . . , 0FH, 10H, 11H, . . . , 1FH, 20H, 21H, . . . , FFH. As far as D_3 to D_0 are concerned, they see a nibble stream of 0000, 0001, 0010, 0011, . . . , 1111, 0000, 0001, and so on.

Figure A1-6a illustrates how the output current of the D/A converter appears. As each input nibble is latched into port 22H, the output current moves one step higher until reaching the maximum current. Then the cycle repeats. If all resistors are exact and all transistors matched, all steps are identical in size.

Resolution

In the perfect staircase of Fig. A1-6b a step is called an *LSB increment* because it is produced by a change in the LSB. One way to measure the quality of a D/A converter is its *resolution*, the ratio of the LSB increment to the maximum output. As a formula,

$$\text{Resolution} = \frac{1}{2^n - 1} \quad (\text{A1-6})$$

For instance, a 4-bit D/A converter has a resolution of

$$\text{Resolution} = \frac{1}{2^4 - 1} = \frac{1}{15}$$

This is sometimes read as 1 part in 15.

The number of different steps an n -bit converter produces is

$$\text{Steps} = 2^n - 1 \quad (\text{A1-6a})$$

Therefore, an alternative way to think of resolution is

$$\text{Resolution} = \frac{1}{\text{steps}} \quad (\text{A1-6b})$$

Percent resolution is given by

$$\text{Percent resolution} = \text{resolution} \times 100\% \quad (\text{A1-7})$$

If the resolution is 1 part in 15, then

$$\text{Percent resolution} = \frac{1}{15} \times 100\% = 6.67\%$$

The greater the number of bits, the better the resolution. With Eqs. A1-6 and A1-7 we can calculate the resolution and percent resolution for more bits. Table A1-2 is a summary of the resolution for converters with 4 to 18 bits.

Because the number of bits determines the resolution in Eq. A1-6, an indirect way to specify resolution is by stating the number of bits. For instance, an 8-bit converter has 8-bit resolution, a 10-bit converter has 10-bit resolution, and so on. This is a quick and easy way to pin down the resolution. When necessary, Eqs. A1-6, A1-6a, and A1-7 can give additional information.

Accuracy

In a D/A converter, *absolute accuracy* refers to how close each output current is to its ideal value. In Fig. A1-5 absolute accuracy depends on the reference voltage, resistor tolerance, transistor mismatch, and so forth. In a typical application, a trimmer adjustment is included to set the full-scale output at a preassigned value.

Relative accuracy refers to how close each output level is to its ideal fraction of full-scale output. With a 4-bit

TABLE A1-2. RESOLUTION

Bits	Resolution	Percent
4	1 part in 15	6.67
6	1 part in 63	1.59
8	1 part in 255	0.392
10	1 part in 1,023	0.0978
12	1 part in 4,095	0.0244
14	1 part in 16,383	0.0061
16	1 part in 65,535	0.00153
18	1 part in 262,143	0.000381

converter, the ideal output levels as a fraction of full-scale should be $0, \frac{1}{15}, \frac{2}{15}, \frac{3}{15}$, and so on. Because data sheets specify relative accuracy rather than absolute accuracy, our subsequent discussions will emphasize relative accuracy.

Relative accuracy depends mainly on the tolerance of the weighted resistors in Fig. A1-5. If they are exactly $R, 2R, 4R$, and $8R$, all steps equal 1 LSB increment in Fig. A1-6a. When the resistors depart from ideal values, the steps may be larger or smaller than 1 LSB increment.

 


Fig. A1-7 Error specified in LSB increments.

Errors are specified in terms of LSB increments. For instance, Fig. A1-7a shows an error of 1 LSB; the actual output (solid line) differs from the ideal output (dashed line) by 1 LSB increment. If a negative error follows a positive error, the staircase can fall as shown in Fig. A1-7b. Here you see an error of +1 LSB followed by an error of -1 LSB.

Monotonicity

A *monotonic D/A converter* is one that produces an increase in output current for each successive digital input. The staircases of Fig. A1-7a and b are not monotonic because they do not produce an increase for each digital input. Figure A1-7a is almost monotonic, but Fig. A1-7b is far from monotonic. Monotonicity is the least we can expect from a D/A converter because it only makes sense; the output should increase when the input does.

For a D/A converter to be monotonic the error must be less than $\pm \frac{1}{2}$ LSB at each output level. Why? Because in

 


Fig. A1-8 Critical level for monotonicity.

the worst case, a $+\frac{1}{2}$ -LSB error followed by a $-\frac{1}{2}$ -LSB error produces the critical level where monotonicity is about to be lost. Figure A1-8 illustrates this critical case, an error of $+\frac{1}{2}$ LSB followed by an error of $-\frac{1}{2}$ LSB. If the error of a converter is less than $\pm \frac{1}{2}$ LSB for each output level, we are guaranteed a rising current for each successive digital input. Almost all commercially available D/A converters are monotonic because they have an accuracy of better than $\pm \frac{1}{2}$ LSB at each output level.

Settling Time

After you apply a digital input, it takes a D/A converter anywhere from nanoseconds to microseconds to produce the correct output. *Settling time* is defined as the time it takes for the converter output to stabilize to within $\frac{1}{2}$ LSB of its final value. This time depends on the stray capacitance, saturation delay time, and other factors. Settling time is important because it places a limit on how fast you can change the digital inputs.

Disadvantages of Weighted Resistors

For a weighted-resistor circuit to be monotonic the tolerance of the resistors must be less than the percent resolution. For instance, if the resolution is $\frac{1}{15}$ (6.67 percent), resistors with a tolerance of less than ± 6.67 percent will produce a monotonic staircase. If the resolution is $\frac{1}{255}$ (about 0.4 percent), the resistors need a tolerance of better than ± 0.4 percent for a monotonic output. As you see, 4 bits are no problem, but 8 bits are.

Another difficulty arises with weighted resistors. As the number of bits increases, the range of resistance values gets awkward. For 8 bits, we need resistances of $R, 2R, 4R, \dots, 128R$. The largest resistance is 128 times the smallest. For a 12-bit converter, the largest resistance needs to be 2,048 times the smallest. Because of the tolerance and range problems, mass production of weighted-resistor D/A converters is impractical.

 


Fig. A1-9 R - $2R$ ladder.

A1-3 THE LADDER METHOD

One way to get around the problems of a binary-weighted resistors is to use a *ladder* circuit. Figure A1-9a is an example of the R - $2R$ ladder commonly used in integrated D/A converters. Only two resistance values are needed; this eliminates the range problem. Furthermore, since the resistors are on the same chip, they have almost identical characteristics; this minimizes the tolerance problem. In other words, as the number of bits increases, an integrated ladder can divide the current much more accurately than a binary-weighted circuit.

Ladder Properties

An R - $2R$ ladder does something interesting to the impedance at different points in the circuit. To begin with, the two resistors at node D in Fig. A1-9a are in parallel and may be reduced to an equivalent resistance R , shown in Fig. A1-9b. Now, to the right of node C we have R in series with R , a total of $2R$. Since node C has $2R$ in parallel with $2R$, the circuit reduces to Fig. A1-9c.

Looking into the left side of node B (Fig. A1-9c), we see $2R$ in parallel with $2R$. Therefore, the circuit reduces to Fig. A1-9d. Again, $2R$ is in parallel with $2R$, so the circuit reduces to the single R shown in Fig. A1-9e.

Figure A1-10 summarizes ladder impedances. Do you see the point? Looking into the left side of a node, we always see an equivalent resistance of R . Just to the right of each node, we always see a resistance of $2R$. This impedance phenomenon is the key to analyzing modern D/A converters because they use the ladders instead of weighted resistors.

Binary Division of Current

Figure A1-11 shows how a ladder can divide the current into binary levels. The typical D/A converter has a reference current set by the user. In this example, the reference current is 2 mA. The bottom of each $2R$ resistor is grounded in either switch position. When a switch is to the right, the current through a $2R$ resistor flows to the upper ground. When a switch is to the left, the lower ground sinks the current. With all the switches to the right, as shown in Fig. A1-11, I_{OUT} is zero.

Here is how the ladder divides the 2 mA of reference current. Just to the right of node A we see an equivalent resistance of $2R$. Therefore, the 2 mA of input current divides equally at node A. Similarly, at node B we see $2R$ in parallel with $2R$; again, the current divides equally into 0.5-mA branch currents. This process continues through the ladder, so that we wind up with the upper grounds sinking 1, 0.5, 0.25, and 0.125 mA.

Other Switch Positions

When we move the switches, we do not change the way the current divides at the nodes. It still divides equally at each node. But when a switch is to the left, it steers the

 


Fig. A1-10 Ladder impedances.

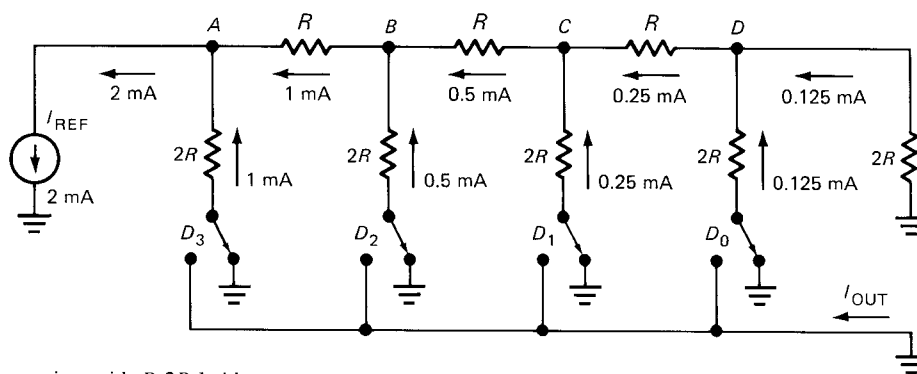


Fig. A1-11 D/A conversion with R - $2R$ ladder.

current into the lower ground. Bits D_3 to D_0 control the transistorized switches. From previous discussions, we can see that

$$I_{OUT} = (D_3 + 2^{-1}D_2 + 2^{-2}D_1 + 2^{-3}D_0) \frac{I_{REF}}{2} \quad (A1-8)$$

Therefore, the output current of a 4-bit ladder is from 0 to $\frac{15}{16}I_{REF}$.

More Bits

A similar analysis applies to longer ladders. The output current is

$$I_{OUT} = (D_{n-1} + 2^{-1}D_{n-2} + \cdots + 2^{1-n}D_0) \frac{I_{REF}}{2} \quad (A1-9)$$

For instance, an 8-bit ladder produces a maximum output current of $\frac{255}{256}I_{REF}$. The LSB increment is $\frac{1}{255}I_{REF}$.

Why Steer Current

Current steering may seem more complicated than necessary, but there is good reason for it. The currents throughout

the ladder remain constant; all that changes are the ground points. Constant current implies constant voltage, which means that stray capacitance in the ladder has little effect. In other words, we do not get the usual exponential charge and discharge associated with a change in voltage. This reduces the settling time. For this reason, IC converters often use the current-steering approach shown in Fig. A1-11.

A1-4 THE COUNTER METHOD OF A/D CONVERSION

Figure A1-12 shows the simplest but least used method of A/D conversion. V_{IN} is the analog input voltage. D_7 to D_0 are the digital output. The digital output drives a D/A converter, which produces an analog output V_{OUT} . When *COUNT* is high, the counter counts upward. When *COUNT* is low, the counter stops. For convenience, an 8-bit D/A converter and 8-bit counter are used, but the idea applies to any number of bits.

Operation

The A/D conversion takes place as follows. First, the *START* pulse goes low, clearing the counter. When the

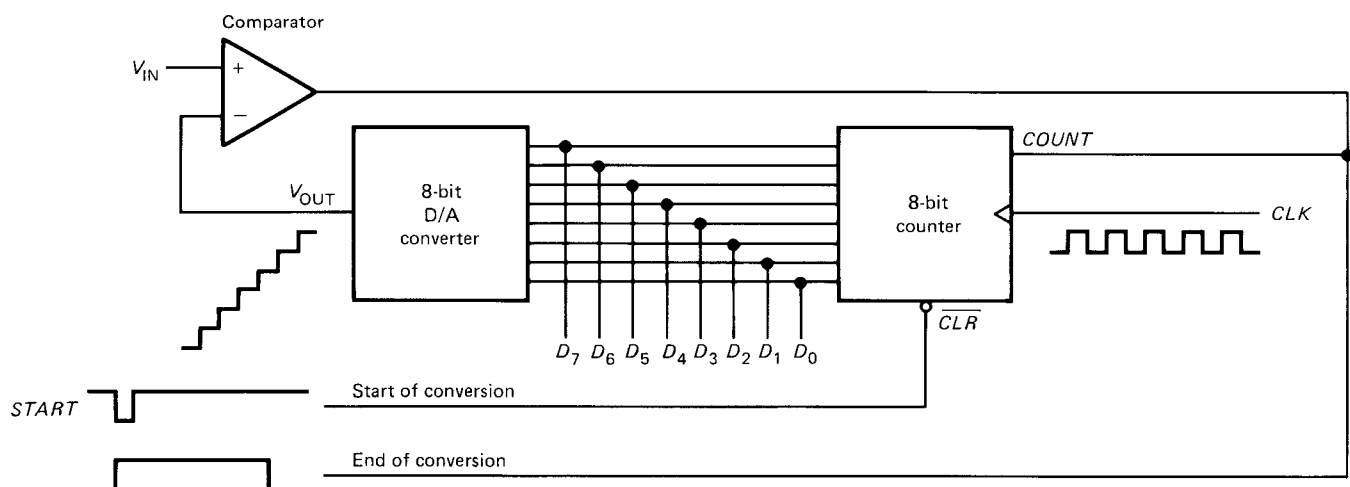


Fig. A1-12 A/D conversion with counter.

START pulse returns high, the counter is ready to go. Initially, V_{OUT} is zero; therefore, the op amp has a high output and *COUNT* is high. The counter starts counting upward from zero. Since the output of the counter drives a D/A converter, the converter output is a positive voltage staircase. As long as V_{IN} is greater than V_{OUT} , the op amp has a positive output, *COUNT* remains high, and the staircase voltage keeps rising.

At some point along the staircase, the next step makes V_{OUT} greater than V_{IN} . This forces *COUNT* to go low, and the counter stops. Now, the digital output D_7 to D_0 is the digital equivalent of the analog input. The negative-going edge of the *COUNT* signal is used as an *end-of-conversion* signal; this tells other circuits that the A/D conversion is finished.

If the analog input V_{IN} is changed, external circuits must send another *START* pulse to *start the conversion*. This clears the count and a new cycle begins. When the digital data is ready, the end-of-conversion signal has a falling edge.

Disadvantage

The main disadvantage of the *counter method* is its slow speed. In the worst case (maximum analog input) the counter has to reach the maximum count before the staircase voltage is greater than the analog input. For an 8-bit converter, this means a conversion time of 255 clock periods. For a 12-bit converter, the conversion time is 4,095 clock periods.

A1-5 SUCCESSIVE APPROXIMATION

The most widely used approach in A/D conversion is the *successive-approximation method* (see Fig. A1-13). As

before, the output of a D/A converter drives the inverting input of an op-amp comparator. The difference, however, is in how the SAR register converges on the digital equivalent. (SAR stands for *successive-approximation register*.) When the conversion is finished, the digital equivalent is transferred to the output buffer register.

MSB First

When the start-of-conversion signal goes low, the SAR register is cleared and V_{OUT} drops to zero. When the start-of-conversion signal goes high, the conversion begins. Instead of counting up 1 bit at a time, the successive-approximation method starts by setting the MSB. In other words, during the first clock pulse the control circuit loads a high MSB into the SAR register, whose output then equals

1000 0000

As soon as this digital output appears, V_{OUT} jumps to $\frac{128}{255}$ times full-scale. If this is more than V_{IN} , the negative output of the comparator signals the control circuit to reset the MSB. On the other hand, if V_{OUT} is less than V_{IN} , the positive output of the comparator indicates that the MSB is to remain set. In some designs, setting and testing the MSB take place during the first clock pulse following the start of conversion. In other designs, several clock pulses may be needed to set the MSB, test it, and reset it if necessary.

Remaining Bits

Let us assume that the MSB was not reset. The SAR register contents are now 1000 0000. The next clock pulse will set

 


Fig. A1-13 A/D conversion by successive approximation.

D_6 , giving a digital output of

1100 0000

V_{OUT} now steps to $\frac{192}{255}$ times full-scale. If V_{OUT} is greater than V_{IN} , the negative op-amp output causes D_6 to reset. If V_{OUT} is less than V_{IN} , D_6 remains set.

During the remaining clock pulses, successive bits are set and tested. Whenever a bit causes V_{OUT} to exceed V_{IN} , the bit is reset. In this way, all bits are set, tested, and reset if necessary. With the fastest circuits, the conversion is finished after eight clock pulses, and the D/A output is the analog equivalent of the register contents. Slower designs take longer because more clock pulses are needed to set, test, and possibly reset each bit.

Output Buffer

When the conversion is finished, the control circuit sends out a low end-of-conversion signal. The falling edge of this signal loads the digital equivalent into the buffer register. In this way, the digital output will remain even though we start a new conversion cycle.

Advantage

The main advantage of the successive-approximation method is speed. At best, it takes only n clock pulses to produce n -bit resolution of the analog signal. This is a big improvement over the counter method. Even with slower designs, the successive-approximation method is still considerably better than the counter method.

APPENDIX 2. BINARY-HEXADECIMAL-DECIMAL EQUIVALENTS

Binary	Hexadecimal	UB Decimal	LB Decimal	Binary	Hexadecimal	UB Decimal	LB Decimal
0000 0000	00	0	0	0011 0000	30	12,288	48
0000 0001	01	256	1	0011 0001	31	12,544	49
0000 0010	02	512	2	0011 0010	32	12,800	50
0000 0011	03	768	3	0011 0011	33	13,056	51
0000 0100	04	1,024	4	0011 0100	34	13,312	52
0000 0101	05	1,280	5	0011 0101	35	13,568	53
0000 0110	06	1,536	6	0011 0110	36	13,824	54
0000 0111	07	1,792	7	0011 0111	37	14,080	55
0000 1000	08	2,048	8	0011 1000	38	14,336	56
0000 1001	09	2,304	9	0011 1001	39	14,592	57
0000 1010	0A	2,560	10	0011 1010	3A	14,848	58
				0011 1011	3B	15,104	59
0000 1011	0B	2,816	11	0011 1100	3C	15,360	60
0000 1100	0C	3,072	12	0011 1101	3D	15,616	61
0000 1101	0D	3,328	13	0011 1110	3E	15,872	62
0000 1110	0E	3,584	14	0011 1111	3F	16,128	63
0000 1111	0F	3,840	15	0100 0000	40	16,384	64
0001 0000	10	4,096	16	0100 0001	41	16,640	65
0001 0001	11	4,352	17	0100 0010	42	16,896	66
0001 0010	12	4,608	18	0100 0011	43	17,152	67
0001 0011	13	4,864	19	0100 0100	44	17,408	68
0001 0100	14	5,120	20	0100 0101	45	17,664	69
0001 0101	15	5,376	21	0100 0110	46	17,920	70
0001 0110	16	5,632	22	0100 0111	47	18,176	71
0001 0111	17	5,888	23	0100 1000	48	18,432	72
0001 1000	18	6,144	24	0100 1001	49	18,688	73
0001 1001	19	6,400	25	0100 1010	4A	18,944	74
0001 1010	1A	6,656	26	0100 1011	4B	19,200	75
0001 1011	1B	6,912	27	0100 1100	4C	19,456	76
0001 1100	1C	7,168	28	0100 1101	4D	19,712	77
0001 1101	1D	7,424	29	0100 1110	4E	19,968	78
0001 1110	1E	7,680	30	0100 1111	4F	20,224	79
0001 1111	1F	7,936	31	0101 0000	50	20,480	80
0010 0000	20	8,192	32	0101 0001	51	20,736	81
0010 0001	21	8,448	33	0101 0010	52	20,992	82
0010 0010	22	8,704	34	0101 0011	53	21,248	83
0010 0011	23	8,960	35	0101 0100	54	21,504	84
0010 0100	24	9,216	36	0101 0101	55	21,760	85
0010 0101	25	9,472	37	0101 0110	56	22,016	86
0010 0110	26	9,728	38	0101 0111	57	22,272	87
0010 0111	27	9,984	39	0101 1000	58	22,528	88
0010 1000	28	10,240	40	0101 1001	59	22,784	89
0010 1001	29	10,496	41	0101 1010	5A	23,040	90
0010 1010	2A	10,752	42	0101 1011	5B	23,296	91
0010 1011	2B	11,008	43	0101 1100	5C	23,552	92
0010 1100	2C	11,264	44	0101 1101	5D	23,808	93
0010 1101	2D	11,520	45	0101 1110	5E	24,064	94
0010 1110	2E	11,776	46	0101 1111	5F	24,320	95
0010 1111	2F	12,032	47				

Binary	Hexadecimal	UB Decimal	LB Decimal	Binary	Hexadecimal	UB Decimal	LB Decimal
0110 0000	60	24,576	96	1001 0010	92	37,376	146
0110 0001	61	24,832	97	1001 0011	93	37,632	147
0110 0010	62	25,088	98	1001 0100	94	37,888	148
0110 0011	63	25,344	99	1001 0101	95	38,144	149
0110 0100	64	25,600	100	1001 0110	96	38,400	150
0110 0101	65	25,856	101	1001 0111	97	38,656	151
0110 0110	66	26,112	102	1001 1000	98	38,912	152
0110 0111	67	26,368	103	1001 1001	99	39,168	153
0110 1000	68	26,624	104	1001 1010	9A	39,424	154
0110 1001	69	26,880	105	1001 1011	9B	39,680	155
0110 1010	6A	27,136	106	1001 1100	9C	39,936	156
0110 1011	6B	27,392	107	1001 1101	9D	40,192	157
0110 1100	6C	27,648	108	1001 1110	9E	40,448	158
0110 1101	6D	27,904	109	1001 1111	9F	40,704	159
0110 1110	6E	28,160	110	1010 0000	A0	40,960	160
0110 1111	6F	28,416	111	1010 0001	A1	41,216	161
0111 0000	70	28,672	112	1010 0010	A2	41,472	162
0111 0001	71	28,928	113	1010 0011	A3	41,728	163
0111 0010	72	29,184	114	1010 0100	A4	41,984	164
0111 0011	73	29,440	115	1010 0101	A5	42,240	165
0111 0100	74	29,696	116	1010 0110	A6	42,496	166
0111 0101	75	29,952	117	1010 0111	A7	42,752	167
0111 0110	76	30,208	118	1010 1000	A8	43,008	168
0111 0111	77	30,464	119	1010 1001	A9	43,264	169
0111 1000	78	30,720	120	1010 1010	AA	43,520	170
0111 1001	79	30,976	121	1010 1011	AB	43,776	171
0111 1010	7A	31,232	122	1010 1100	AC	44,032	172
0111 1011	7B	31,488	123	1010 1101	AD	44,288	173
0111 1100	7C	31,744	124	1010 1110	AE	44,544	174
0111 1101	7D	32,000	125	1010 1111	AF	44,800	175
0111 1110	7E	32,256	126	1011 0000	B0	45,056	176
0111 1111	7F	32,512	127	1011 0001	B1	45,312	177
1000 0000	80	32,768	128	1011 0010	B2	45,568	178
1000 0001	81	33,024	129	1011 0011	B3	45,824	179
1000 0010	82	33,280	130	1011 0100	B4	46,080	180
1000 0011	83	33,536	131	1011 0101	B5	46,336	181
1000 0100	84	33,792	132	1011 0110	B6	46,592	182
1000 0101	85	34,048	133	1011 0111	B7	46,848	183
1000 0110	86	34,304	134	1011 1000	B8	47,104	184
1000 0111	87	34,560	135	1011 1001	B9	47,360	185
1000 1000	88	34,816	136	1011 1010	BA	47,616	186
1000 1001	89	35,072	137	1011 1011	BB	47,872	187
1000 1010	8A	35,328	138	1011 1100	BC	48,128	188
1000 1011	8B	35,584	139	1011 1101	BD	48,384	189
1000 1100	8C	35,840	140	1011 1110	BE	48,640	190
1000 1101	8D	36,096	141	1011 1111	BF	48,896	191
1000 1110	8E	36,352	142	1100 0000	C0	49,152	192
1000 1111	8F	36,608	143	1100 0001	C1	49,408	193
1001 0000	90	36,864	144	1100 0010	C2	49,664	194
1001 0001	91	37,120	145	1100 0011	C3	49,920	195

APPENDIX 2. BINARY-HEXADECIMAL-DECIMAL EQUIVALENTS (*Continued*)

Binary	Hexadecimal	UB Decimal	LB Decimal	Binary	Hexadecimal	UB Decimal	LB Decimal
1100 0100	C4	50,176	196	1110 0010	E2	57,856	226
1100 0101	C5	50,432	197	1110 0011	E3	58,112	227
1100 0110	C6	50,688	198	1110 0100	E4	58,368	228
1100 0111	C7	50,944	199	1110 0101	E5	58,624	229
1100 1000	C8	51,200	200	1110 0110	E6	58,880	230
1100 1001	C9	51,456	201	1110 0111	E7	59,136	231
1100 1010	CA	51,712	202	1110 1000	E8	59,392	232
1100 1011	CB	51,968	203	1110 1001	E9	59,648	233
1100 1100	CC	52,224	204	1110 1010	EA	59,904	234
1100 1101	CD	52,480	205	1110 1011	EB	60,160	235
1100 1110	CE	52,736	206	1110 1100	EC	60,416	236
1100 1111	CF	52,992	207	1110 1101	ED	60,672	237
1101 0000	D0	53,248	208	1110 1110	EE	60,928	238
1101 0001	D1	53,504	209	1110 1111	EF	61,184	239
1101 0010	D2	53,760	210	1111 0000	F0	61,440	240
1101 0011	D3	54,016	211	1111 0001	F1	61,696	241
1101 0100	D4	54,272	212	1111 0010	F2	61,952	242
1101 0101	D5	54,528	213	1111 0011	F3	62,208	243
1101 0110	D6	54,784	214	1111 0100	F4	62,464	244
1101 0111	D7	55,040	215	1111 0101	F5	62,720	245
1101 1000	D8	55,296	216	1111 0110	F6	62,976	246
1101 1001	D9	55,552	217	1111 0111	F7	63,232	247
1101 1010	DA	55,808	218	1111 1000	F8	63,488	248
1101 1011	DB	56,064	219	1111 1001	F9	63,744	249
1101 1100	DC	56,320	220	1111 1010	FA	64,000	250
1101 1101	DD	56,576	221	1111 1011	FB	64,256	251
1101 1110	DE	56,832	222	1111 1100	FC	64,512	252
1101 1111	DF	57,088	223	1111 1101	FD	64,768	253
1110 0000	E0	57,344	224	1111 1110	FE	65,024	254
1110 0001	E1	57,600	225	1111 1111	FF	65,280	255

APPENDIX 3. 7400 SERIES TTL

Number	Function	Number	Function
7400	Quad 2-input NAND gates	7455	Expandable 4-input 2-wide AND-OR-INVERT gates
7401	Quad 2-input NAND gates (open collector)	7459	Dual 2-3 input 2-wide AND-OR-INVERT gates
7402	Quad 2-input NOR gates	7460	Dual 4-input expanders
7403	Quad 2-input NOR gates (open collector)	7461	Triple 3-input expanders
7404	Hex inverters	7462	2-2-3-3 input 4-wide expanders
7405	Hex inverters (open collector)	7464	2-2-3-4 input 4-wide AND-OR-INVERT gates
7406	Hex inverter buffer-driver	7465	4-wide AND-OR-INVERT gates (open collector)
7407	Hex buffer-drivers	7470	Edge-triggered <i>JK</i> flip-flop
7408	Quad 2-input AND gates	7472	<i>JK</i> master-slave flip-flop
7409	Quad 2-input AND gates (open collector)	7473	Dual <i>JK</i> master-slave flip-flop
7410	Triple 3-input NAND gates	7474	Dual <i>D</i> flip-flop
7411	Triple 3-input AND gates	7475	Quad latch
7412	Triple 3-input NAND gates (open collector)	7476	Dual <i>JK</i> master-slave flip-flop
7413	Dual Schmitt triggers	7480	Gates full adder
7414	Hex Schmitt triggers	7482	2-bit binary full adder
7416	Hex inverter buffer-drivers	7483	4-bit binary full adder
7417	Hex buffer-drivers	7485	4-bit magnitude comparator
7420	Dual 4-input NAND gates	7486	Quad EXCLUSIVE-OR gate
7421	Dual 4-input AND gates	7489	64-bit random-access read-write memory
7422	Dual 4-input NAND gates (open collector)	7490	Decade counter
7423	Expandable dual 4-input NOR gates	7491	8-bit shift register
7425	Dual 4-input NOR gates	7492	Divide-by-12 counter
7226	Quad 2-input TTL-MOS interface NAND gates	7493	4-bit binary counter
7427	Triple 3-input NOR gates	7494	4-bit shift register
7428	Quad 2-input NOR buffer	7495	4-bit right-shift-left-shift register
7430	8-input NAND gate	7496	5-bit parallel-in-parallel-out shift register
7432	Quad 2-input OR gates	74100	4-bit bistable latch
7437	Quad 2-input NAND buffers	74104	<i>JK</i> master-slave flip-flop
7438	Quad 2-input NAND buffers (open collector)	74105	<i>JK</i> master-slave flip-flop
7439	Quad 2-input NAND buffers (open collector)	74107	Dual <i>JK</i> master-slave flip-flop
7440	Dual 4-input NAND buffers	74109	Dual <i>JK</i> positive-edge-triggered flip-flop
7441	BCD-to-decimal decoder-Nixie driver	74116	Dual 4-bit latches with clear
7442	BCD-to-decimal decoder	74121	Monostable multivibrator
7443	Excess 3-to-decimal decoder	74122	Monostable multivibrator with clear
7444	Excess Gray-to-decimal	74123	Monostable multivibrator
7445	BCD-to-decimal decoder-driver	74125	Three-state quad bus buffer
7446	BCD-to-seven segment decoder-drivers (30-V output)	74126	Three-state quad bus buffer
7447	BCD-to-seven segment decoder-drivers (15-V output)	74132	Quad Schmitt trigger
7448	BCD-to-seven segment decoder-drivers	74136	Quad 2-input EXCLUSIVE-OR gate
7450	Expandable dual 2-input 2-wide AND-OR-INVERT gates	74141	BCD-to-decimal decoder-driver
7451	Dual 2-input 2-wide AND-OR-INVERT gates	74142	BCD counter-latch-driver
7452	Expandable 2-input 4-wide AND-OR gates	74145	BCD-to-decimal decoder-driver
7453	Expandable 2-input 4-wide AND-OR-INVERT gates	74147	10/4 priority encoder
7454	2-input 4-wide AND-OR-INVERT gates	74148	Priority encoder
		74150	16-line-to-1-line multiplexer
		74151	8-channel digital multiplexer
		74152	8-channel data selector-multiplexer

APPENDIX 3. 7400 SERIES TTL (Continued)

Number	Function	Number	Function
74153	Dual 4/1 multiplexer	74190	Up-down decade counter
74154	4-line-to-16-line decoder-demultiplexer	74191	Synchronous binary up-down counter
74155	Dual 2/4 demultiplexer	74192	Binary up-down counter
74156	Dual 2/4 demultiplexer	74193	Binary up-down counter
74157	Quad 2/1 data selector	74194	4-bit directional shift register
74160	Decade counter with asynchronous clear	74195	4-bit parallel-access shift register
74161	Synchronous 4-bit counter	74196	Presetable decade counter
74162	Synchronous 4-bit counter	74197	Presetable binary counter
74163	Synchronous 4-bit counter	74198	8-bit shift register
74164	8-bit serial shift register	74199	8-bit shift register
74165	Parallel-load 8-bit serial shift register	74221	Dual one-shot Schmitt trigger
74166	8-bit shift register	74251	Three-state 8-channel multiplexer
74173	4-bit three-state register	74259	8-bit addressable latch
74174	Hex <i>F</i> flip-flop with clear	74276	Quad <i>JK</i> flip-flop
74175	Quad <i>D</i> flip-flop with clear	74279	Quad debouncer
74176	35-MHz presetable decade counter	74283	4-bit binary full adder with fast carry
74177	35-MHz presetable binary counter	74284	Three-state 4-bit multiplexer
74179	4-bit parallel-access shift register	74285	Three-state 4-bit multiplexer
74180	8-bit odd-even parity generator-checker	74365	Three-state hex buffers
74181	Arithmetic-logic unit	74366	Three-state hex buffers
74182	Look-ahead carry generator	74367	Three-state hex buffers
74184	BCD-to-binary converter	74368	Three-state hex buffers
74185	Binary-to-BCD converter	74390	Individual clocks with flip-flops
74189	Three-state 64-bit random-access memory	74393	Dual 4-bit binary counter

APPENDIX 4. PINOUTS AND FUNCTION TABLES

74LS83

The 74LS83 is a 4-bit full adder; the binary output is

$$S = A + B$$

 


Fig. A4-1

In Fig. A4-1, pins 1, 3, 8, and 10 are the **A** input (A_3, A_2, A_1, A_0); pins 16, 4, 7, and 11 are the **B** input (B_3, B_2, B_1, B_0); and pins 15, 2, 6, and 9 are the **S** output (S_3, S_2, S_1, S_0). Pin 13 is the CARRY IN, and pin 14 is the CARRY OUT.

74LS157

This chip is a word multiplexer. Two words of 4 bits each are the inputs; one word of 4 bits is the output. The two input words are designated **L** (left) and **R** (right); the output word is **Y**. In Fig. A4-2, pin 1 (SELECT) and pin 15 (STROBE) are control inputs. The **L** word goes to pins 14, 11, 5, 2 (L_3, L_2, L_1, L_0), and the **R** word goes to pins 13, 10, 6, and 3 (R_3, R_2, R_1, R_0).

 


Fig. A4-2

TABLE A4-1. FUNCTION TABLE

STROBE	SELECT	Y	Comment
1	X	0	Output goes low
0	0	L	Output equals left word
0	1	R	Output equals right word

As indicated in Table A4-1, a high **STROBE** input produces a low output, no matter what the input words. When **STROBE** is low, the **SELECT** input controls the operation. A low **SELECT** will send the **L** word to the output; a high **SELECT** sends the **R** word to the output.

 


Fig. A4-3

74LS173

The 74LS173 is a 4-bit buffer register with three-state outputs. In Fig. A4-3, pins 14, 13, 12, and 11 are the data inputs (D_3, D_2, D_1, D_0). Pins 3, 4, 5, and 6 are the data outputs (Q_3, Q_2, Q_1, Q_0). Pins 9 and 10 (G_1 and G_2) are the input control. Pins 1 and 2 (**M** and **N**) are the output control.

As shown in Table A4-2, both **M** and **N** must be low to get a **Q** output. If either **M** or **N** (or both) is high, the output is three-stated (floating or high impedance).

When **M** and **N** are both low, Table A4-3 applies. As indicated, a high **CLEAR** will clear all **Q** bits to 0. When **CLEAR** is low, G_1 and G_2 control input loading. If either G_1 or G_2 (or both) are high, no change takes place in the **Q** bits. When both G_1 and G_2 are low, the next positive clock edge loads the input data.

TABLE A4-2. OUTPUT CONTROL

M	N	Output
0	0	Connected
0	1	Hi-Z
1	0	Hi-Z
1	1	Hi-Z

TABLE A4-3. FUNCTION TABLE FOR $M = 0$ AND $N = 0$

CLEAR	CLOCK	G_1	G_2	D_n	Q_n	Comment
1	X	X	X	X	0	Clear output
0	0	X	X	X	NC	No change
0	↑	1	X	X	NC	No change
0	↑	X	1	X	NC	No change
0	↑	0	0	0	0	Reset bit n
0	↑	0	0	1	1	Set bit n

 


Fig. A4-4

74189

The 74189 is a 64-bit RAM organized as 16 words of 4 bits each. In Fig. A4-4 pins 1, 15, 14, and 13 are the address inputs (A_3 , A_2 , A_1 , A_0). Pins 4, 6, 10, and 12 are the data inputs (D_3 , D_2 , D_1 , D_0). Pins 5, 7, 9, and 11 are the data outputs (Q_3 , Q_2 , Q_1 , Q_0).

TABLE A4-4. FUNCTION TABLE

\overline{CE}	\overline{WE}	Output	Comment
1	X	Hi-Z	Do nothing
0	0	Hi-Z	Write complement
0	1	Stored word	Read

Table A4-4 summarizes the operation of this read-write memory. When \overline{CE} is high, the output is three-stated (high impedance). When \overline{CE} is low and \overline{WE} is low, the complement of the input data word is stored at the addressed memory location; during this write operation, the output is three-stated. When \overline{CE} is low and \overline{WE} is high, the stored word appears at the output.

APPENDIX 5. SAP-1 PARTS LIST

Chips

C1: 74LS107, dual *JK* master-slave flip-flop
C2: 74LS107
C3: 74LS126, quad three-state normally open switches
C4: 74LS173, buffer register, three-state outputs, 4 bits
C5: 74LS157, 2-to-1 nibble multiplexer
C6: 74189, 64-bit (16×4) static RAM, three-state outputs
C7: 74189
C8: 74LS173
C9: 74LS173
C10: 74LS173
C11: 74LS173
C12: 74LS126
C13: 74LS126
C14: 74LS86, quad 2-input EXCLUSIVE-OR gates
C15: 74LS86
C16: 74LS83, quad full adders
C17: 74LS83
C18: 74LS126
C19: 74LS126
C20: 74LS173
C21: 74LS173
C22: 74LS173
C23: 74LS173
C24: 7400, quad 2-input NAND gates
C25: 74LS10, triple 3-input NAND gates
C26: 74LS00
C27: 7404, hex inverter
C28: NE555, timer
C29: 74LS107
C30: LM340T-5, voltage regulator, 5 V
C31: 74LS04, hex inverter
C32: 74LS20, dual 4-input NAND gates
C33: 74LS20
C34: 74LS20
C35: 74LS04
C36: 74LS107
C37: 74LS107
C38: 74LS107

C39: 74LS00
C40: 74LS00
C41: 74LS00
C42: 74LS00
C43: 74LS00
C44: 74LS20
C45: 74LS10
C46: 74LS00
C47: 74LS04
C48: 74LS04

Diodes

D1: 1N4001, rectifier diode, 50 PIV, 1 A
D2: 1N4001
D3: 1N4001
D4: 1N4001

Switches

S1: SPST DIP switch, 4 bits
S2: DPST on-off
S3: SPST DIP, 8 bits
S4: SPST push button, momentary, normally open
S5: SPDT push button, momentary
S6: SPDT push button, momentary
S7: SPDT on-on switch

Miscellaneous

Resistors: eight 1-k Ω , fourteen 10-k Ω , one 18-k Ω , one 36-k Ω
Capacitors: 0.01- μ F, 0.1- μ F, 1000- μ F (50 V)
Transformer: F-25X = 115 V primary, 12.6 V secondary CT, 1.5 A
Fuse: $\frac{3}{8}$ -A slow blow

Totals

1N4001-4	74LS20-4
LM340T-5-1	74LS83-2
NE555-1	74LS86-2
7400-1	74LS107-6
74LS00-7	74LS126-5
7404-1	74LS157-1
74LS04-4	74LS173-9
74LS10-2	74189-2

APPENDIX 6. 8085 INSTRUCTIONS

Instruction	Op Code	T states	Flags	Main Effect
ACI byte	CE	7	All	$A \leftarrow A + CY + \text{byte}$
ADC A	8F	4	All	$A \leftarrow A + A + CY$
ADC B	88	4	All	$A \leftarrow A + B + CY$
ADC C	89	4	All	$A \leftarrow A + C + CY$
ADC D	8A	4	All	$A \leftarrow A + D + CY$
ADC E	8B	4	All	$A \leftarrow A + E + CY$
ADC H	8C	4	All	$A \leftarrow A + H + CY$
ADC L	8D	4	All	$A \leftarrow A + L + CY$
ADC M	8E	7	All	$A \leftarrow A + M_{HL} + CY$
ADD A	87	4	All	$A \leftarrow A + A$
ADD B	80	4	All	$A \leftarrow A + B$
ADD C	81	4	All	$A \leftarrow A + C$
ADD D	82	4	All	$A \leftarrow A + D$
ADD E	83	4	All	$A \leftarrow A + E$
ADD H	84	4	All	$A \leftarrow A + H$
ADD L	85	4	All	$A \leftarrow A + L$
ADD M	86	7	All	$A \leftarrow A + M_{HL}$
ADI byte	C6	7	All	$A \leftarrow A + \text{byte}$
ANA A	A7	4	All	$A \leftarrow A \text{ AND } A$
ANA B	A0	4	All	$A \leftarrow A \text{ AND } B$
ANA C	A1	4	All	$A \leftarrow A \text{ AND } C$
ANA D	A2	4	All	$A \leftarrow A \text{ AND } D$
ANA E	A3	4	All	$A \leftarrow A \text{ AND } E$
ANA H	A4	4	All	$A \leftarrow A \text{ AND } H$
ANA L	A5	4	All	$A \leftarrow A \text{ AND } L$
ANA M	A6	7	All	$A \leftarrow A \text{ AND } M_{HL}$
ANI byte	E6	7	All	$A \leftarrow A \text{ AND byte}$
CALL address	CD	18	None	$PC \leftarrow \text{address}$
CC address	DC	18/9	None	$PC \leftarrow \text{address if } CY = 1$
CM address	FC	18/9	None	$PC \leftarrow \text{address if } S = 1$
CMA	2F	4	None	$A \leftarrow \overline{A}$
CMC	3F	4	CY	$CY \leftarrow \overline{CY}$
CMP A	BF	4	All	$Z \leftarrow 1 \text{ if } A = A$
CMP B	B8	4	All	$Z \leftarrow 1 \text{ if } A = B$
CMP C	B9	4	All	$Z \leftarrow 1 \text{ if } A = C$
CMP D	BA	4	All	$Z \leftarrow 1 \text{ if } A = D$
CMP E	BB	4	All	$Z \leftarrow 1 \text{ if } A = E$
CMP H	BC	4	All	$Z \leftarrow 1 \text{ if } A = H$
CMP L	BD	4	All	$Z \leftarrow 1 \text{ if } A = L$
CMP M	BE	7	All	$Z \leftarrow 1 \text{ if } A = M_{HL}$
CNC address	D4	18/9	None	$PC \leftarrow \text{address if } CY = 0$
CNZ address	C4	18/9	None	$PC \leftarrow \text{address if } Z = 0$
CP address	F4	18/9	None	$PC \leftarrow \text{address if } S = 0$
CPE address	EC	18/9	None	$PC \leftarrow \text{address if } P = 1$
CPI byte	FE	7	All	$Z \leftarrow 1 \text{ if } A = \text{byte}$
CPO address	E4	18/9	None	$PC \leftarrow \text{address if } P = 0$
CZ address	CC	18/9	None	$PC \leftarrow \text{address if } Z = 1$
DAA	27	4	All	$A \leftarrow \text{BCD number}$
DAD B	09	10	CY	$HL \leftarrow HL + BC$
DAD D	19	10	CY	$HL \leftarrow HL + DE$
DAD H	29	10	CY	$HL \leftarrow HL + HL$

Instruction	Op Code	T states	Flags	Main Effect
DAD SP	39	10	CY	$HL \leftarrow HL + SP$
DCR A	3D	4	All but CY	$A \leftarrow A - 1$
DCR B	05	4	All but CY	$B \leftarrow B - 1$
DCR C	0D	4	All but CY	$C \leftarrow C - 1$
DCR D	15	4	All but CY	$D \leftarrow D - 1$
DCR E	1D	4	All but CY	$E \leftarrow E - 1$
DCR H	25	4	All but CY	$H \leftarrow H - 1$
DCR L	2D	4	All but CY	$L \leftarrow L - 1$
DCR M	35	10	All but CY	$M_{HL} \leftarrow M_{HL} - 1$
DCX B	0B	6	None	$BC \leftarrow BC - 1$
DCX D	1B	6	None	$DE \leftarrow DE - 1$
DCX H	2B	6	None	$HL \leftarrow HL - 1$
DCX SP	3B	6	None	$SP \leftarrow SP - 1$
DI	F3	4	None	Disable interrupts
EI	FB	4	None	Enable interrupts
HLT	76	5	None	Stop processing
IN byte	DB	10	None	$A \leftarrow \text{byte}$
INR A	3C	4	All but CY	$A \leftarrow A + 1$
INR B	04	4	All but CY	$B \leftarrow B + 1$
INR C	0C	4	All but CY	$C \leftarrow C + 1$
INR D	14	4	All but CY	$D \leftarrow D + 1$
INR E	1C	4	All but CY	$E \leftarrow E + 1$
INR H	24	4	All but CY	$H \leftarrow H + 1$
INR L	2C	4	All but CY	$L \leftarrow L + 1$
INR M	34	10	All but CY	$M_{HL} \leftarrow M_{HL} + 1$
INX B	03	6	None	$BC \leftarrow BC + 1$
INX D	13	6	None	$DE \leftarrow DE + 1$
INX H	23	6	None	$HL \leftarrow HL + 1$
INX SP	33	6	None	$SP \leftarrow SP + 1$
JC address	DA	10/7	None	$PC \leftarrow \text{address if } CY = 1$
JM address	FA	10/7	None	$PC \leftarrow \text{address if } S = 1$
JMP address	C3	10	None	$PC \leftarrow \text{address}$
JNC address	D2	10/7	None	$PC \leftarrow \text{address if } CY = 0$
JNZ address	C2	10/7	None	$PC \leftarrow \text{address if } Z = 0$
JP address	F2	10/7	None	$PC \leftarrow \text{address if } S = 0$
JPE address	EA	10/7	None	$PC \leftarrow \text{address if } P = 1$
JPO address	E2	10/7	None	$PC \leftarrow \text{address if } P = 0$
JZ address	CA	10/7	None	$PC \leftarrow \text{address if } Z = 1$
LDA address	3A	13	None	$A \leftarrow M_{\text{adr}}$
LDAX B	0A	7	None	$A \leftarrow M_{BC}$
LDAX D	1A	7	None	$A \leftarrow M_{DE}$
LHLD address	2A	16	None	$H \leftarrow M_{\text{adr}}$
LXI B, dble	01	10	None	$BC \leftarrow \text{dble}$
LXI D, dble	11	10	None	$DE \leftarrow \text{dble}$
LXI H, dble	21	10	None	$HL \leftarrow \text{dble}$
LXI SP, dble	31	10	None	$SP \leftarrow \text{dble}$
MOV A,A	7F	4	None	$A \leftarrow A$
MOV A,B	78	4	None	$A \leftarrow B$
MOV A,C	79	4	None	$A \leftarrow C$
MOV A,D	7A	4	None	$A \leftarrow D$
MOV A,E	7B	4	None	$A \leftarrow E$
MOV A,H	7C	4	None	$A \leftarrow H$

APPENDIX 6. 8085 INSTRUCTIONS (Continued)

Instruction	Op Code	T states	Flags	Main Effect
MOV A,L	7D	4	None	$A \leftarrow L$
MOV A,M	7E	7	None	$A \leftarrow M_{HL}$
MOV B,A	47	4	None	$B \leftarrow A$
MOV B,B	40	4	None	$B \leftarrow B$
MOV B,C	41	4	None	$B \leftarrow C$
MOV B,D	42	4	None	$B \leftarrow D$
MOV B,E	43	4	None	$B \leftarrow E$
MOV B,H	44	4	None	$B \leftarrow H$
MOV B,L	45	4	None	$B \leftarrow L$
MOV B,M	46	7	None	$B \leftarrow M_{HL}$
MOV C,A	4F	4	None	$C \leftarrow A$
MOV C,B	48	4	None	$C \leftarrow B$
MOV C,C	49	4	None	$C \leftarrow C$
MOV C,D	4A	4	None	$C \leftarrow D$
MOV C,E	4B	4	None	$C \leftarrow E$
MOV C,H	4C	4	None	$C \leftarrow H$
MOV C,L	4D	4	None	$C \leftarrow L$
MOV C,M	4E	7	None	$C \leftarrow M_{HL}$
MOV D,A	57	4	None	$D \leftarrow A$
MOV D,B	50	4	None	$D \leftarrow B$
MOV D,C	51	4	None	$D \leftarrow C$
MOV D,D	52	4	None	$D \leftarrow D$
MOV D,E	53	4	None	$D \leftarrow E$
MOV D,H	54	4	None	$D \leftarrow H$
MOV D,L	55	4	None	$D \leftarrow L$
MOV D,M	56	7	None	$D \leftarrow M_{HL}$
MOV E,A	5F	4	None	$E \leftarrow A$
MOV E,B	58	4	None	$E \leftarrow B$
MOV E,C	59	4	None	$E \leftarrow C$
MOV E,D	5A	4	None	$E \leftarrow D$
MOV E,E	5B	4	None	$E \leftarrow E$
MOV E,H	5C	4	None	$E \leftarrow H$
MOV E,L	5D	4	None	$E \leftarrow L$
MOV E,M	5E	7	None	$E \leftarrow M_{HL}$
MOV H,A	67	4	None	$H \leftarrow A$
MOV H,B	60	4	None	$H \leftarrow B$
MOV H,C	61	4	None	$H \leftarrow C$
MOV H,D	62	4	None	$H \leftarrow D$
MOV H,E	63	4	None	$H \leftarrow E$
MOV H,H	64	4	None	$H \leftarrow H$
MOV H,L	65	4	None	$H \leftarrow L$
MOV H,M	66	7	None	$H \leftarrow M_{HL}$
MOV L,A	6F	4	None	$L \leftarrow A$
MOV L,B	68	4	None	$L \leftarrow B$
MOV L,C	69	4	None	$L \leftarrow C$
MOV L,D	6A	4	None	$L \leftarrow D$
MOV L,E	6B	4	None	$L \leftarrow E$
MOV L,H	6C	4	None	$L \leftarrow H$
MOV L,L	6D	4	None	$L \leftarrow L$
MOV L,M	6E	7	None	$L \leftarrow M_{HL}$
MOV M,A	77	7	None	$M_{HL} \leftarrow A$

Instruction	Op Code	T states	Flags	Main Effect
MOV M,B	70	7	None	$M_{HL} \leftarrow B$
MOV M,C	71	7	None	$M_{HL} \leftarrow C$
MOV M,D	72	7	None	$M_{HL} \leftarrow D$
MOV M,E	73	7	None	$M_{HL} \leftarrow E$
MOV M,H	74	7	None	$M_{HL} \leftarrow H$
MOV M,L	75	7	None	$M_{HL} \leftarrow L$
MVI A,byte	3E	7	None	$A \leftarrow \text{byte}$
MVI B,byte	06	7	None	$B \leftarrow \text{byte}$
MVI C,byte	0E	7	None	$C \leftarrow \text{byte}$
MVI D,byte	16	7	None	$D \leftarrow \text{byte}$
MVI E,byte	1E	7	None	$E \leftarrow \text{byte}$
MVI H,byte	26	7	None	$H \leftarrow \text{byte}$
MVI L,byte	2E	7	None	$L \leftarrow \text{byte}$
MVI M,byte	36	10	None	$M_{HL} \leftarrow \text{byte}$
NOP	00	4	None	Delay
ORA A	B7	4	All	$A \leftarrow A \text{ OR } A$
ORA B	B0	4	All	$A \leftarrow A \text{ OR } B$
ORA C	B1	4	All	$A \leftarrow A \text{ OR } C$
ORA D	B2	4	All	$A \leftarrow A \text{ OR } D$
ORA E	B3	4	All	$A \leftarrow A \text{ OR } E$
ORA H	B4	4	All	$A \leftarrow A \text{ OR } H$
ORA L	B5	4	All	$A \leftarrow A \text{ OR } L$
ORA M	B6	7	All	$A \leftarrow A \text{ OR } M_{HL}$
ORI byte	F6	7	All	$A \leftarrow A \text{ OR byte}$
OUT byte	D3	10	None	Port byte $\leftarrow A$
PCHL	E9	6	None	$PC \leftarrow HL$
POP B	C1	10	None	$B \leftarrow M_{stk}$
POP D	D1	10	None	$D \leftarrow M_{stk}$
POP H	E1	10	None	$H \leftarrow M_{stk}$
POP PSW	F1	10	None	$F \leftarrow M_{stk}, A \leftarrow M_{stk} - 1$
PUSH B	C5	12	None	$M_{stk} - 1 \leftarrow B, M_{stk} - 2 \leftarrow C$
PUSH D	D5	12	None	$M_{stk} - 1 \leftarrow D, M_{stk} - 2 \leftarrow E$
PUSH H	E5	12	None	$M_{stk} - 1 \leftarrow H, M_{stk} - 2 \leftarrow L$
PUSH PSW	F5	12	None	$M_{stk} - 1 \leftarrow A, M_{stk} - 2 \leftarrow F$
RAL	17	4	CY	Rotate all left
RAR	1F	4	CY	Rotate all right
RC	D8	12/6	None	$PC \leftarrow \text{return address if } CY = 1$
RET	C9	10	None	$PC \leftarrow \text{return address}$
RIM	20	4	None	$A \leftarrow I$
RLC	07	4	CY	Rotate left with carry
RM	F8	12/6	None	$PC \leftarrow \text{return address if } S = 1$
RNC	D0	12/6	None	$PC \leftarrow \text{return address if } CY = 0$
RNZ	C0	12/6	None	$PC \leftarrow \text{return address if } Z = 0$
RP	F0	12/6	None	$PC \leftarrow \text{return address if } S = 0$
RPE	E8	12/6	None	$PC \leftarrow \text{return address if } P = 1$
RPO	E0	12/6	None	$PC \leftarrow \text{return address if } P = 0$
RRC	0F	4	CY	Rotate right with carry
RST 0	C7	12	None	$PC \leftarrow 0000H$
RST 1	CF	12	None	$PC \leftarrow 0008H$
RST 2	D7	12	None	$PC \leftarrow 0010H$
RST 3	DF	12	None	$PC \leftarrow 0018H$
RST 4	E7	12	None	$PC \leftarrow 0020H$
RST 5	EF	12	None	$PC \leftarrow 0028H$

APPENDIX 6. 8085 INSTRUCTIONS (Continued)

Instruction	Op Code	T states	Flags	Main Effect
RST 6	F7	12	None	$PC \leftarrow 0030H$
RST 7	FF	12	None	$PC \leftarrow 0038H$
RZ	C8	12/6	None	$PC \leftarrow$ return address if $Z = 1$
SBB A	9F	4	All	$A \leftarrow A - A - CY$
SBB B	98	4	All	$A \leftarrow A - B - CY$
SBB C	99	4	All	$A \leftarrow A - C - CY$
SBB D	9A	4	All	$A \leftarrow A - D - CY$
SBB E	9B	4	All	$A \leftarrow A - E - CY$
SBB H	9C	4	All	$A \leftarrow A - H - CY$
SBB L	9D	4	All	$A \leftarrow A - L - CY$
SBB M	9E	7	All	$A \leftarrow A - M - CY$
SBI byte	DE	7	All	$A \leftarrow A - \text{byte} - CY$
SHLD address	22	16	None	$M_{\text{adr}+1} \leftarrow H, M_{\text{adr}} \leftarrow L$
SIM	30	4	None	$I \leftarrow A$
SPHL	F9	6	None	$SP \leftarrow HL$
STA address	32	13	None	$M_{\text{adr}} \leftarrow A$
STAX B	02	7	None	$M_{BC} \leftarrow A$
STAX D	12	7	None	$M_{DE} \leftarrow A$
STC	37	4	CY	$CY \leftarrow 1$
SUB A	97	4	All	$A \leftarrow A - A$
SUB B	90	4	All	$A \leftarrow A - B$
SUB C	91	4	All	$A \leftarrow A - C$
SUB D	92	4	All	$A \leftarrow A - D$
SUB E	93	4	All	$A \leftarrow A - E$
SUB H	94	4	All	$A \leftarrow A - H$
SUB L	95	4	All	$A \leftarrow A - L$
SUB M	96	7	All	$A \leftarrow A - M$
SUI byte	D6	7	All	$A \leftarrow A - \text{byte}$
XCHG	EB	4	None	$HL \leftrightarrow DE$
XRA A	AF	4	All	$A \leftarrow A \text{ XOR } A$
XRA B	A8	4	All	$A \leftarrow A \text{ XOR } B$
XRA C	A9	4	All	$A \leftarrow A \text{ XOR } C$
XRA D	AA	4	All	$A \leftarrow A \text{ XOR } D$
XRA E	AB	4	All	$A \leftarrow A \text{ XOR } E$
XRA H	AC	4	All	$A \leftarrow A \text{ XOR } H$
XRA L	AD	4	All	$A \leftarrow A \text{ XOR } L$
XRA M	AE	7	All	$A \leftarrow A \text{ XOR } M$
XRI byte	EE	7	All	$A \leftarrow A \text{ XOR } \text{byte}$
XTHL	E3	16	None	$HL \leftrightarrow \text{stack}$

APPENDIX 7. MEMORY LOCATIONS: POWERS OF 2

Address Bits	Hexadecimal	Decimal	Power of 2
0000 0000 0000 0001	0001H	1	0
0000 0000 0000 0010	0002H	2	1
0000 0000 0000 0100	0004H	4	2
0000 0000 0000 1000	0008H	8	3
0000 0000 0001 0000	0010H	16	4
0000 0000 0010 0000	0020H	32	5
0000 0000 0100 0000	0040H	64	6
0000 0000 1000 0000	0080H	128	7
0000 0001 0000 0000	0100H	256	8
0000 0010 0000 0000	0200H	512	9
0000 0100 0000 0000	0400H	1,024	10
0000 1000 0000 0000	0800H	2,048	11
0001 0000 0000 0000	1000H	4,096	12
0010 0000 0000 0000	2000H	8,192	13
0100 0000 0000 0000	4000H	16,384	14
1000 0000 0000 0000	8000H	32,768	15

APPENDIX 8. MEMORY LOCATIONS: 16K AND 8K INTERVALS

Address Bits	Hexadecimal	Decimal	Zone
Zone bits = A ₁₅ A ₁₄			
0000 0000 0000 0000	0000H	0	0
0011 1111 1111 1111	3FFFH	16,383	
0100 0000 0000 0000	4000H	16,384	1
0111 1111 1111 1111	7FFFH	32,767	
1000 0000 0000 0000	8000H	32,768	2
1011 1111 1111 1111	BFFFH	49,151	
1100 0000 0000 0000	C000H	49,152	3
1111 1111 1111 1111	FFFFH	65,535	
Zone bits = A ₁₅ A ₁₄ A ₁₃			
0000 0000 0000 0000	0000H	0	0
0001 1111 1111 1111	1FFFH	8,191	
0010 0000 0000 0000	2000H	8,192	1
0011 1111 1111 1111	3FFFH	16,383	
0100 0000 0000 0000	4000H	16,384	2
0101 1111 1111 1111	5FFFH	24,575	
0110 0000 0000 0000	6000H	24,576	3
0111 1111 1111 1111	7FFFH	32,767	
1000 0000 0000 0000	8000H	32,768	4
1001 1111 1111 1111	9FFFH	40,959	

1010 0000 0000 0000	A000H	40,960	5
1011 1111 1111 1111	BFFFH	49,151	
1100 0000 0000 0000	C000H	49,152	6
1101 1111 1111 1111	DFFFH	57,343	
1110 0000 0000 0000	E000H	57,344	7
1111 1111 1111 1111	FFFFH	65,535	

APPENDIX 9. MEMORY LOCATIONS: 4K INTERVALS

Address Bits	Hexadecimal	Decimal	Zone
Zone bits = $A_{15}A_{14}A_{13}A_{12}$			
0000 0000 0000 0000	0000H	0	0
0000 1111 1111 1111	0FFFH	4,095	
0001 0000 0000 0000	1000H	4,096	1
0001 1111 1111 1111	1FFFH	8,191	
0010 0000 0000 0000	2000H	8,192	2
0010 1111 1111 1111	2FFFH	12,287	
0011 0000 0000 0000	3000H	12,288	3
0011 1111 1111 1111	3FFFH	16,383	
0100 0000 0000 0000	4000H	16,384	4
0100 1111 1111 1111	4FFFH	20,479	
0101 0000 0000 0000	5000H	20,480	5
0101 1111 1111 1111	5FFFH	24,575	
0110 0000 0000 0000	6000H	24,576	6
0110 1111 1111 1111	6FFFH	28,671	
0111 0000 0000 0000	7000H	28,672	7
0111 1111 1111 1111	7FFFH	32,767	
1000 0000 0000 0000	8000H	32,768	8
1000 1111 1111 1111	8FFFH	36,863	
1001 0000 0000 0000	9000H	36,864	9
1001 1111 1111 1111	9FFFH	40,959	
1010 0000 0000 0000	A000H	40,960	10
1010 1111 1111 1111	AFFFH	45,055	
1011 0000 0000 0000	B000H	45,056	11
1011 1111 1111 1111	BFFFH	49,151	
1100 0000 0000 0000	C000H	49,152	12
1100 1111 1111 1111	CFFFH	53,247	
1101 0000 0000 0000	D000H	53,248	13
1101 1111 1111 1111	DFFFH	57,343	
1110 0000 0000 0000	E000H	57,344	14
1110 1111 1111 1111	EFFFH	61,439	
1111 0000 0000 0000	F000H	61,440	15
1111 1111 1111 1111	FFFFH	65,535	

APPENDIX 10. MEMORY LOCATIONS: 2K INTERVALS

Address Bits	Hexadecimal	Decimal	Zone	Address Bits	Hexadecimal	Decimal	Zone
Zone bits = A ₁₅ A ₁₄ A ₁₃ A ₁₂ A ₁₁							
0000 0000 0000 0000	0000H	0	0	1000 0000 0000 0000	8000H	32,768	16
0000 0111 1111 1111	07FFH	2,047		1000 0111 1111 1111	87FFH	34,815	
0000 1000 0000 0000	0800H	2,048	1	1000 1000 0000 0000	8800H	34,816	17
0000 1111 1111 1111	0FFFH	4,095		1000 1111 1111 1111	8FFFH	36,863	
0001 0000 0000 0000	1000H	4,096	2	1001 0000 0000 0000	9000H	36,864	18
0001 0111 1111 1111	17FFH	6,143		1001 0111 1111 1111	97FFH	38,911	
0001 1000 0000 0000	1800H	6,144	3	1001 1000 0000 0000	9800H	38,912	19
0001 1111 1111 1111	1FFFH	8,191		1001 1111 1111 1111	9FFFH	40,959	
0010 0000 0000 0000	2000H	8,192	4	1010 0000 0000 0000	A000H	40,960	20
0010 0111 1111 1111	27FFH	10,239		1010 0111 1111 1111	A7FFH	43,007	
0010 1000 0000 0000	2800H	10,240	5	1010 1000 0000 0000	A800H	43,008	21
0010 1111 1111 1111	2FFFH	12,287		1010 1111 1111 1111	AFFFH	45,055	
0011 0000 0000 0000	3000H	12,288	6	1011 0000 0000 0000	B000H	45,056	22
0011 0111 1111 1111	37FFH	14,335		1011 0111 1111 1111	B7FFH	47,103	
0011 1000 0000 0000	3800H	14,336	7	1011 1000 0000 0000	B800H	47,104	23
0011 1111 1111 1111	3FFFH	16,383		1011 1111 1111 1111	BFFFH	49,151	
0100 0000 0000 0000	4000H	16,384	8	1100 0000 0000 0000	C000H	49,152	24
0100 0111 1111 1111	47FFH	18,431		1100 0111 1111 1111	C7FFH	51,199	
0100 1000 0000 0000	4800H	18,432	9	1100 1000 0000 0000	C800H	51,200	25
0100 1111 1111 1111	4FFFH	20,479		1100 1111 1111 1111	CFFFH	53,247	
0101 0000 0000 0000	5000H	20,480	10	1101 0000 0000 0000	D000H	53,248	26
0101 0111 1111 1111	57FFH	22,527		1101 0111 1111 1111	D7FFH	55,295	
0101 1000 0000 0000	5800H	22,538	11	1101 1000 0000 0000	D800H	55,296	27
0101 1111 1111 1111	5FFFH	24,575		1101 1111 1111 1111	DFFFH	57,343	
0110 0000 0000 0000	6000H	24,576	12	1110 0000 0000 0000	E000H	57,344	28
0110 0111 1111 1111	67FFH	26,623		1110 0111 1111 1111	E7FFH	59,391	
0110 1000 0000 0000	6800H	26,624	13	1110 1000 0000 0000	E800H	59,392	29
0110 1111 1111 1111	6FFFH	28,671		1110 1111 1111 1111	EFFFH	61,439	
0111 0000 0000 0000	7000H	28,672	14	1111 0000 0000 0000	F000H	61,440	30
0111 0111 1111 1111	77FFH	30,719		1111 0111 1111 1111	F7FFH	63,487	
0111 1000 0000 0000	7800H	30,720	15	1111 1000 0000 0000	F800H	63,488	31
0111 1111 1111 1111	7FFFH	32,767		1111 1111 1111 1111	FFFFH	65,535	

APPENDIX 11. MEMORY LOCATIONS: 1K INTERVALS

Address Bits	Hexadecimal	Decimal	Zone	Address Bits	Hexadecimal	Decimal	Zone
Zone bits = A ₁₅ A ₁₄ A ₁₃ A ₁₂ A ₁₁ A ₁₀							
0000 0000 0000 0000	0000H	0	0	0101 0000 0000 0000	5000H	20,480	20
0000 0011 1111 1111	03FFH	1,023		0101 0011 1111 1111	53FFH	21,503	
0000 0100 0000 0000	0400H	1,024	1	0101 0100 0000 0000	5400H	21,504	21
0000 0111 1111 1111	07FFH	2,047		0101 0111 1111 1111	57FFH	22,527	
0000 1000 0000 0000	0800H	2,048	2	0101 1000 0000 0000	5800H	22,528	22
0000 1011 1111 1111	0BFFH	3,071		0101 1011 1111 1111	5BFFH	23,551	
0000 1100 0000 0000	0C00H	3,072	3	0101 1100 0000 0000	5C00H	23,552	23
0000 1111 1111 1111	0FFFH	4,095		0101 1111 1111 1111	5FFFH	24,575	
0001 0000 0000 0000	1000H	4,096	4	0110 0000 0000 0000	6000H	24,576	24
0001 0011 1111 1111	13FFH	5,119		0110 0011 1111 1111	63FFH	25,599	
0001 0100 0000 0000	1400H	5,120	5	0110 0100 0000 0000	6400H	25,600	25
0001 0111 1111 1111	17FFH	6,143		0110 0111 1111 1111	67FFH	26,623	
0001 1000 0000 0000	1800H	6,144	6	0110 1000 0000 0000	6800H	26,624	26
0001 1011 1111 1111	1BFFH	7,167		0110 1011 1111 1111	6BFFH	27,647	
0001 1100 0000 0000	1C00H	7,168	7	0110 1100 0000 0000	6C00H	27,648	27
0001 1111 1111 1111	1FFFH	8,191		0110 1111 1111 1111	6FFFH	28,671	
0010 0000 0000 0000	2000H	8,192	8	0111 0000 0000 0000	7000H	28,672	28
0010 0011 1111 1111	23FFH	9,215		0111 0011 1111 1111	73FFH	29,695	
0010 0100 0000 0000	2400H	9,216	9	0111 0100 0000 0000	7400H	29,696	29
0010 0111 1111 1111	27FFH	10,239		0111 0111 1111 1111	77FFH	30,719	
0010 1000 0000 0000	2800H	10,240	10	0111 1000 0000 0000	7800H	30,720	30
0010 1011 1111 1111	2BFFH	11,263		0111 1011 1111 1111	7BFFH	31,743	
0010 1100 0000 0000	2C00H	11,264	11	0111 1100 0000 0000	7C00H	31,744	31
0010 1111 1111 1111	2FFFH	12,287		0111 1111 1111 1111	7FFFH	32,767	
0011 0000 0000 0000	3000H	12,288	12	1000 0000 0000 0000	8000H	32,768	32
0011 0011 1111 1111	33FFH	13,311		1000 0011 1111 1111	83FFH	33,791	
0011 0100 0000 0000	3400H	13,312	13	1000 0100 0000 0000	8400H	33,792	33
0011 0111 1111 1111	37FFH	14,335		1000 0111 1111 1111	87FFH	34,815	
0011 1000 0000 0000	3800H	14,336	14	1000 1000 0000 0000	8800H	34,816	34
0011 1011 1111 1111	3BFFH	15,359		1000 1011 1111 1111	8BFFH	35,839	
0011 1100 0000 0000	3C00H	15,360	15	1000 1100 0000 0000	8C00H	35,840	35
0011 1111 1111 1111	3FFFH	16,383		1000 1111 1111 1111	8FFFH	36,863	
0100 0000 0000 0000	4000H	16,384	16	1001 0000 0000 0000	9000H	36,864	36
0100 0011 1111 1111	43FFH	17,407		1001 0011 1111 1111	93FFH	37,887	
0100 0100 0000 0000	4400H	17,408	17	1001 0100 0000 0000	9400H	37,888	37
0100 0111 1111 1111	47FFH	18,431		1001 0111 1111 1111	97FFH	38,911	
0100 1000 0000 0000	4800H	18,432	18	1001 1000 0000 0000	9800H	38,912	38
0100 1011 1111 1111	4BFFH	19,455		1001 1011 1111 1111	9BFFH	39,935	
0100 1100 0000 0000	4C00H	19,456	19	1001 1100 0000 0000	9C00H	39,936	39
0100 1111 1111 1111	4FFFH	20,479		1001 1111 1111 1111	9FFFH	40,959	

APPENDIX 11. MEMORY LOCATIONS: 1K INTERVALS (Continued)

Address Bits	Hexadecimal	Decimal	Zone	Address Bits	Hexadecimal	Decimal	Zone
Zone bits = $A_{15}A_{14}A_{13}A_{12}A_{11}A_{10}$							
1010 0000 0000 0000	A000H	40,960	40	1101 0000 0000 0000	D000H	53,248	52
1010 0011 1111 1111	A3FFH	41,983		1101 0011 1111 1111	D3FFH	54,271	
1010 0100 0000 0000	A400H	41,984	41	1101 0100 0000 0000	D400H	54,272	53
1010 0111 1111 1111	A7FFH	43,007		1101 0111 1111 1111	D7FFH	55,295	
1010 1000 0000 0000	A800H	43,008	42	1101 1000 0000 0000	D800H	55,296	54
1010 1011 1111 1111	ABFFH	44,031		1101 1011 1111 1111	DBFFH	56,319	
1010 1100 0000 0000	AC00H	44,032	43	1101 1100 0000 0000	DC00H	56,320	55
1010 1111 1111 1111	AFFFH	45,055		1101 1111 1111 1111	DFFFH	57,343	
1011 0000 0000 0000	B000H	45,056	44	1110 0000 0000 0000	E000H	57,344	56
1011 0011 1111 1111	B3FFH	46,079		1110 0011 1111 1111	E3FFH	58,367	
1011 0100 0000 0000	B400H	46,080	45	1110 0100 0000 0000	E400H	58,368	57
1011 0111 1111 1111	B7FFH	47,103		1110 0111 1111 1111	E7FFH	59,391	
1011 1000 0000 0000	B800H	47,104	46	1110 1000 0000 0000	E800H	59,392	58
1011 1011 1111 1111	BBFFH	48,127		1110 1011 1111 1111	EBFFH	60,415	
1011 1100 0000 0000	BC00H	48,128	47	1110 1100 0000 0000	EC00H	60,416	59
1011 1111 1111 1111	BFFFH	49,151		1110 1111 1111 1111	EBFFH	61,439	
1100 0000 0000 0000	C000H	49,152	48	1111 0000 0000 0000	F000H	61,440	60
1100 0011 1111 1111	C3FFH	50,175		1111 0011 1111 1111	F3FFH	62,463	
1100 0100 0000 0000	C400H	50,176	49	1111 0100 0000 0000	F400H	62,464	61
1100 0111 1111 1111	C7FFH	51,199		1111 0111 1111 1111	F7FFH	63,487	
1100 1000 0000 0000	C800H	51,200	50	1111 1000 0000 0000	F800H	63,488	62
1100 1011 1111 1111	CBFFH	52,223		1111 1011 1111 1111	FBFFH	64,511	
1100 1100 0000 0000	CC00H	52,224	51	1111 1100 0000 0000	FC00H	64,512	63
1100 1111 1111 1111	CFFFH	53,247		1111 1111 1111 1111	FFFFH	65,535	

APPENDIX 12. PROGRAMMING MODELS

 


Fig. A12-1 6502 programming model.

 


Fig. A12-3 8085/Z80 (8085/8080 subset) programming model.

 


Fig. A12-2 6800/6808 programming model.

 


Fig. A12-4 8088/8086 programming model.

Answers to Odd-Numbered Problems

CHAP. 1. 1-1. a. 1 b. 2 c. $2\frac{1}{2}$ 1-3. a. 10 b. 2 c. 5 d. 16 1-5. 1,024, 4,096, 8K 1-7. 1010 1100, 172 1-9. 201 1-11. 1100 0111, 199 1-13. 111000 1-15. 1001 0110 1-17. F52B, F52C, F52D, F52E, F52F, F530 1-19. a. 1111 1111 b. 1010 1011 1100 c. 1100 1101 0100 0010 d. 1111 0011 0010 1001 1-21. 0011 1110, 0000 1110, 1101 0011, 0010 0000, 0111 0110 1-23. a. 4,095 b. 16,383 c. 32,740 d. 46,040 1-25. 16,384, 16K 1-27. 0000, FFFF 1-29. a. EE b. 1D7B c. 3BFF d. B8B5 1-31. a. 87 b. 9,043 c. 597,266 1-33. 100 1100, 100 1001, 101 0011, 101 0100


CHAP. 2. 2-1. One or more, one 2-3. Noninverter 2-5. 64, 000000 2-7. 3, 9, C, F 2-9. 128, 1111111 2-11. 0, 59 2-13. $Y = \overline{A} + \overline{B}$, low 2-15. 8 2-17. 0, $Y = \overline{A} + \overline{B} + \overline{C}$, 000 to 110, 111 2-19. $Y = \overline{ABC}$, 0 2-21. $Y = \overline{AB} + \overline{CD}$, 16, 0000, 0001, 0010, 0100, 0101, 0110, 1000, 1001, 1010 2-23. a. 0000 b. 0001 c. JIM d. OPR 2-25. a. Positive b. Negative c. Positive d. Negative

CHAP. 3. 3-1. High; low; inverter 3-3. None, Z_5 , Z_6 3-5. Q is 1, \overline{Q} is 0 3-7. Change the output NOR gate of Fig. 3-28a to a bubbled AND gate; all bubbles cancel leaving the simplified circuit of Fig. 3-28b. 3-9. 0, 1 3-11. 512 3-13. 16; 0, 1, 1, 0 3-15. 1, 0, inverter 3-17. a. None b. Z_7 c. Z_2 d. X_2 and Y_2 3-19. 0, 1 3-21. 512 3-23. Low; high 3-25. a. 0 b. 1 c. 1 d. 1 3-27. a. 11010b. 01001 c. 11111 d. 10010 3-29. Remove the inverter 3-31. a. $CARRY = 0$, $SUM = 0$ b. 0, 1 c. 0, 1 d. 1, 0 3-33. a. 0011 1100 b. 0101 0000 1100 c. 0001 1110 0101 1100 d. 1111 0000 1101 0010


CHAP. 4. 4-1. 1.075 mA, 1.387 mA 4-3. 5 4-5. All; b, c, f, g

CHAP. 5. 5-1. \overline{ABCD} , $AB\overline{CD}$, $AB\overline{CD}$

5-3.

 

5-5.

 


5-7.

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	0	0	0
$\overline{A}B$	0	0	0	0
AB	1	1	1	1
$A\overline{B}$	1	1	1	1


5-9.

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	1	0	1
$\overline{A}B$	0	0	1	1
AB	1	0	1	1
$A\overline{B}$	0	0	1	0

 


5-11.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	1	1
$\bar{A}B$	1	0	1	0
AB	0	0	1	0
$A\bar{B}$	0	1	0	1

 


5-13.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	1
$\bar{A}B$	0	0	1	1
AB	X	X	X	X
$A\bar{B}$	0	0	X	X

 

5-15.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	1	1
$\bar{A}B$	1	0	1	0
AB	X	X	X	X
$A\bar{B}$	0	1	X	X

 

CHAP. 6. 6-1. a. 0001 1000, 18H b. 0010 0100, 24H
c. 0010 1010, 2AH d. 0110 0011, 63H 6-3. a. 7BH
b. 78H c. A8H d. D1H 6-5. a. +30 b. -7 c. -28
d. +49 6-7. a. F9H b. 01H c. 03H d. 1FH 6-9.
a. 1110 1101, EDH b. 1101 0000, D0H c. 0010 0101,
25H d. 1101 1111, DFH 6-11. 9BH, DDH

CHAP. 7. 7-1. a. C b. G 7-3. a. 0000 b. 1001 7-5. 3
MHz; the output frequency is half the input frequency
7-7. $Q = 0, Y = 1; Q = 1, Y = CLK$

CHAP. 8. 8-1. a. 0001 0111 b. 1000 1101 8-3. 385 Ω
8-5. 4 μs 8-7. 6.4 μs 8-9. 65,535 8-11. 1 μs , 6 μs
8-13. 1.6 μs , 0.2 μs 8-15. Two answers: 7490 (divide by
10) and 7492 (divide by 6), or 7490 (divide by 5) and 7492
(divide by 12) 8-17. 136 8-19. a. 0, 1 b. 1, 1 c. 0

CHAP. 9. 9-1. 16,384 9-3. 12

9-5.

Address	Data
DDDD	UDDD UDDU
DDDU	DUUU UDD
DDUD	DDUU DUUD
DDUU	DDUD DDUU
DUDD	DDDU DUUU
DUDU	DUDU UUUU
DUUD	UUUD UUDU
DUUU	UUUU UDDD

9-7. 63 9-9. BFFFH; 49,151 9-11. a. 47, 212, 207, 110,
83, 122 b. 36,357


CHAP. 10. 10-1. Address Mnemonic

0H	LDA DH
1H	ADD EH
2H	SUB FH
3H	OUT
4H	HLT
DH	05H
EH	04H
FH	06H

10-3. Address Mnemonic

0H	LDA BH
1H	ADD CH
2H	SUB DH
3H	ADD EH
4H	SUB FH
5H	HLT
BH	08H
CH	04H
DH	03H
EH	05H
FH	02H

10-5.

 

10-7. LDA: 1A3H or 0001 1010 0011, 2C3H or 0010 1100 0011, 3E3H or 0011 1110 0011; SUB: 1A3H or 0001 1010 0011, 2E1H or 0010 1110 0001, 3CFH or 0011 1100 1111 10-9. a. Negative edge; *CLK* is on its rising edge b. High c. Low d. High 10-11. a. Low b. Low c. High

CHAP. 11. 11-1. Mnemonic

MVI A,64H
MVI B,96H
MVI C,C8H
HLT

11-3.

Mnemonic

MVI A,32H
STA 4000H
MVI A,33H
STA 4001H
MVI A,34H
STA 4002H
HLT

11-5.

Mnemonic

MVI A,44H
MVI B,22H
ADD B
STA 5000H
HLT

11-7. a. 120 b. 119 c. Change the first instruction to MVI C,D2H

11-9.

Mnemonic

MVI A,00H
MVI B,19H
MVI C,07H
CALL F006H
STA 2000H
HLT

11-11.

Label Mnemonic

IN 01H
ANI 01H
JNZ ODD
MVI A,45H
JMP DONE
ODD: MVI A,4FH
DONE: MVI C,08H
AGAIN: OUT 04H
RAR
DCR C
JNZ AGAIN
HLT

11-13.	Address	Contents
	2000H	DBH
	2001H	02H
	2002H	E6H
	2003H	01H
	2004H	CAH
	2005H	00H
	2006H	20H
	2007H	DBH
	2008H	01H
	2009H	32H
	200AH	00H
	200BH	40H
	200CH	76H

11-15.	Address	Contents
	2000H	0EH
	2001H	23H
	2002H	0DH
	2003H	C2H
	2004H	02H
	2005H	20H
	2006H	C9H

11-17.	Label	Mnemonic
	LOOP:	MVI A,05H
		CALL F020H
		DCR A
		JNZ LOOP
		RET
	Address	Contents
	E100H	3EH
	E101H	05H
	E102H	CDH
	E103H	20H
	E104H	F0H
	E105H	3DH
	E106H	C2H
	E107H	02H
	E108H	E1H
	E109H	C9H

11-19.	Address	Contents
	F080H	3EH
	F081H	06H
	F082H	32H
	F083H	93H
	F084H	F0H
	F085H	CDH
	F086H	60H
	F087H	F0H
	F088H	3AH
	F089H	93H
	F08AH	F0H

F08BH	3DH
F08CH	32H
F08DH	93H
F08EH	F0H
F08FH	C2H
F090H	85H
F091H	F0H
F092H	C9H

11-21.	Address	Contents
	2000H	D3H
	2001H	04H
	2002H	0EH
	2003H	42H
	2004H	0DH
	2005H	C2H
	2006H	04H
	2007H	20H
	2008H	2FH
	2009H	00H
	200AH	C3H
	200BH	00H
	200CH	20H

CHAP. 12.	12-1.	Mnemonic
		MVI A,00H
		MVI B,01H
		MVI C,59H
		MVI D,02H
		MVI E,F1H
		ADD C
		ADD E
		MOV L,A
		MVI A,00H
		ADC B
		ADD D
		MOV H,A
		HLT

An alternative solution is

Mnemonic
MVI A,F1H
ADI 59H
MOV L,A
MVI A,02H
ACI 01H
MOV H,A
HLT

12-3.	Label	Mnemonic
	LOOP:	LXI H,4FFFH
		INX H
		MOV B,M
		MOV A,H

ADI 40H
MOV H,A
MOV M,B
SUI 40H
MOV H,A
CPI 53H
JNZ LOOP
MOV A,L
CPI FFH
JNZ LOOP
HLT

12-9.

Label

Mnemonic

LXI SP,E000H
LXI H,4FFFH
LOOP: INX H
MOV A,M
MOV B,08H
AGAIN: OUT 22H
CALL F010H
RAR
DCR B
JNZ AGAIN
MOV A,L
CPI FFH
JNZ LOOP
HLT

12-5.

Label

Mnemonic

LXI SP,E000H
MVI A,00H
MVI B,FFH
LOOP: INR A
OUT 22H
CALL F010H
DCR B
JNZ LOOP
HLT

CHAP. 14. 14-1. How you would accomplish your task without a computer. 14-3. Branch. 14-5. The subroutine (part of the program) needs to be written only once but can then be used many times. 14-7. Formula translation. 14-9. Creating a language which would encourage programmers to write by using what are considered "correct" programming practices.

12-7.

Label

Mnemonic

LXI SP,E000H
LXI H,5FFFH
LOOP: INX H
MOV A,M
OUT 22H
CALL F020H
MOV A,H
CPI 61H
JNZ LOOP
MOV A,L
CPI FFH
JNZ LOOP
HLT

CHAP. 15. 15-1. By its address. 15-3. 1,048,576. 15-5. The accumulator. 15-7. Registers are faster. 15-9. The status register (or condition code register or flag register). 15-11. The carry flag. 15-13. No. 15-15. DE. 15-17. C581. 15-19. 8 bits. 15-21. 256 bytes. 15-23. 16 bits. 15-25. Nothing. They are always set. 15-27. None. 15-29. It is named AX and is 16 bits wide with an 8-bit upper half (called AH) and an 8-bit lower half (called AL). 15-31. The instruction pointer. 15-33. 65,536 bytes.

CHAP. 16. 16-1. Nothing. 16-3. The original number in the accumulator is still there. 16-5. 00. 16-7. It copies the contents of the Y register to the accumulator. 16-9. STY. 16-11. 01. 16-13. 16. 16-15. Clear accumulator A.

16-17.

Addr	Obj	Assembler	Comment
0000	C6	LDAB #\$89	Load the number immediately following the LDAB op code (C6) into accumulator B (89)
0001	89		
0002	17	TBA	Transfer (copy) the contents of B to A
0003	3E	WAI	Stop

16-19. 76. 16-21. It copies the contents of register C to register B. 16-23. STA aaaa [LD (aaaa),A]. 16-25. DEBUG. 16-27. Register or memory. 16-29. DL. 16-31. The contents of memory location 4456₁₆. 16-33. It stands for assemble and it translates 8088/8086 mnemonics into machine code. 16-35. It executes one instruction and then displays the current values of all registers and stops.

16-37.

-a

```
9522:0100 mov BL,89
9522:0102 mov CL,BL
9522:0104
```

-u 100 103

```
9522:0100 B389      MOV BL,89
9522:0102 88D9      MOV CL,BL
```

-r

```
AX=0000 BX=0000 CX=0000 DX=0000 SP=ADDE BP=0000 SI=0000 DI=0000
DS=9522 ES=9522 SS=9522 CS=9522 IP=0100 NV UP EI PL NZ NA PO NC
9522:0100 B389      MOV BL,89
```

-t

```
AX=0000 BX=0089 CX=0000 DX=0000 SP=ADDE BP=0000 SI=0000 DI=0000
DS=9522 ES=9522 SS=9522 CS=9522 IP=0102 NV UP EI PL NZ NA PO NC
9522:0102 88D9      MOV CL,BL
```

-t

```
AX=0000 BX=0089 CX=0089 DX=0000 SP=ADDE BP=0000 SI=0000 DI=0000
DS=9522 ES=9522 SS=9522 CS=9522 IP=0104 NV UP EI PL NZ NA PO NC
```

Note: Answers to Chapters 18 to 23 are in the teacher's manual.

Index

Note: For entries marked with (#), refer also to specific families listed under "Microprocessor families."

- Absolute accuracy, 488
- Absolute addressing, 265, 333–334
- Access time, 132–133
- Accumulator, 142, 158, 174, 176, 184, 226, 230, 232, 233, 235 (*See also* ALU)
- Accumulator addressing, 264–268
- Accuracy, 488–489
- Active low state, 98
- ADD instruction, 143, 148–150, 178, 197–198
- Adder-subtractor, 85–87, 142, 158
- Addition, 79–87, 199, 271–272, 281–282, 284–287, 290–292, 294, 298–300
- Addition-with-carry, 274, 276–277
- Address, 12, 131, 133, 135–137, 330 (*See also* Addressing mode)
- Address bus, 225
- Address field, 145
- Address line, 131
- Address mapping, 183
- Address state, 147 (*See also* T state)
- #Addressing mode, 224–226
 - absolute, 265, 333–334
 - base plus index, 340
 - base relative plus index, 340–341
 - direct, 187, 264–268
 - extended, 266
 - immediate, 187, 244, 247, 264–268
 - implied, 188, 264–267
 - indexed, 332–336
 - indexed indirect, 335
 - indirect, 205, 331, 333, 336, 338–340
 - indirect indexed, 334–335
 - paging, 263–264
 - program direct, 268
 - program indirect, 340
 - program relative, 337–338
 - range, 225
 - register (accumulator), 188, 264–268
 - register indirect, 336, 338–340
 - register relative, 337
 - relative, 330, 332–333, 335, 337–338
 - zero page, 333–334
- Alphanumerics, 14
- ALU, 7, 79, 175
- American Standard Code for Information Exchange, 14–15, 271
- ANA instruction, 184
- Analog interface, 485
- Analog-to-digital (A/D) converter, 485, 491–493
- AND gate, 22–23, 33–34, 49, 54
- AND instruction, 305–306, 308–310, 312–314
- AND operations, 65–66
- AND sign, 24–25
- AND-OR gate, 55
- AND-OR-INVERT gate, 55–57
- ANI instruction, 184
- #Architecture, 224–226
 - of SAP-1, 140–142
 - of SAP-2, 173–176
 - of SAP-3, 195–196
- #Arithmetic instructions, 271–276
- Arithmetic-logic unit, 7, 79, 175
- ASCII code, 14–15, 271
- Assembler, 181, 222, 354–355, 357, 358 (*See also* Machine language)
- Assembly language, 145, 221–222, 337
- Associative law, 64
- Asynchronous operation, 142 (*See also* Clocking)
- B register, 142, 158, 175
- Base, 6–7
- Base plus index addressing, 340
- Base register, 340
- Base relative plus index addressing, 340–341
- BASIC, 221
- BCD number, 13–14, 270–271
- BCD-to-decimal conversion, 13–14
- Bidirectional register, 173
- Binary adder, 82–83
- Binary adder-subtractor, 85–87, 142, 158
- Binary addition, 79–87 (*See also* Addition)
- Binary code, 2–3
- Binary digit, 4
- Binary number, 2–3, 6–15, 270, 271, 274
- Binary odometer, 1–2, 84
- Binary programming (*see* Machine language)
- Binary subtraction, 80–81, 85–87 (*See also* Subtraction)
- Binary weight, 6
- Binary word, 20
- Binary-coded-decimal number, 13–14, 270–271
- Binary-to-decimal conversion, 3, 6–7
- Binary-to-decimal decoder, 27
- Binary-to-hexadecimal conversion, 10–11, 12
- Bipolar families, 48
- Bit, 4
- Bit comparison, 42
- BIT instruction, 309–310, 311
- Bit position, 271
- Bit-serial form (*see* Serial data stream; Serial loading)
- Boldface notation, 42
- Boolean algebra, 19, 23–27, 64–70
- Boolean function generator, 58–60
- Borrow, 196, 275–276, 281
- #Branch instruction, 179–180, 219, 342–343
- Branch-back instruction (*see* Return instruction)
- Breakpoint, 294
- Broadside loading, 110
- Bubble memory, 135
- Bubbled AND gate, 33–34
- Bubbled OR gate, 36
- Buffer, 54 (*See also* Buffer register)
- Buffer register, 54, 106–107, 110, 122
- Bus, 69, 122
- Bus transient, 152
- Bus-organized computer, 121, 122–125, 152
- Byte, 6, 189–193
 - defined, 345, 348, 351
- C language, 221
- C register, 175
- CALL instruction, 180, 182, 210–211
- Carry flag, 196–197, 272, 274–277, 281, 312
- Cell, 134
- Central processing unit (*see* CPU)
- Chip, 4, 49
- Chip enable, 134
- Chunking, 11
- Clear, 97
- Clear-start debouncer, 158–159
- Clock, 93, 158
- Clock generator, 102–103
- Clocking:
 - edge-triggered, 96–100
 - level, 93–97, 102
 - master-slave, 100–103
 - positive and negative, 94
- CMA instruction, 184
- CMOS, 48
- COBOL, 221
- Code, binary, 2–3
- Code segment register, 268
- Comment, 181–182
- Commutative law, 64
- #Compare and test instruction, 343
- Compatibility, 51–52
- Complement, 19
- Complement instruction, 311, 314
- Complementary MOSFETs, 48
- Computer, 7
 - architecture, 224–226
 - bus-organized, 121, 122–125, 152 (*See also* Microprocessor)
- CON (*see* Control unit)
- Condition code register, 227–228, 232–233
- #Conditional jump (branching), 179, 180, 187, 342–343
- Contact bounce, 92–93
- Content, 131, 224–225
- Control input, 90
- Control matrix, 36–37, 161
- Control ROM, 163
- Control routine, 148–152
- Control unit, 7, 146–152
- Controlled buffer register, 106–107
- Controlled inverter, 41–42
- Controlled shift register, 108–110
- Controller-sequencer, 141–142, 161, 174
- Conversion, 331
 - analog-to-digital, 485, 491–493
 - BCD-to-decimal, 13–14
 - binary-to-decimal, 6–7
 - binary-to-hexadecimal, 10–11, 494–496
 - decimal-to-binary, 8
 - decimal-to-hexadecimal, 13
 - digital-to-analog, 485, 486, 489
 - hexadecimal-to-binary, 10–11, 270
 - hexadecimal-to-decimal, 11–13
- Core RAM, 133

- Counter:
 - down, 118
 - mod-10, 116–118
 - presettable, 118–120, 162
 - program, 113, 140, 147, 153, 173, 227, 230–232, 234, 330
 - programmable modulus, 120
 - ring, 114–116, 146–147, 159–161
 - ripple, 110–113
 - software, 181
 - synchronous, 113–114
 - TTL, 120
 - up-down, 118
- Counter method of A/D conversion, 491–492
- #CPU, 7, 213 (*See also* ALU; Control unit)
- CPU register, 195–196
- Current sink, 52
- Current steering, 491
- D flip-flop, 96–98
- D latch, 95–96
- DAD instruction, 204–205
- Data, 3
- Data bus, 225
- Data processor, 3
- Data segment, 338
- Data selector, 58–59
- Data settling (*see* Bus transient; Settling time)
- #Data transfer instructions, 241–260
- Date pointer, 205
- De Morgan's theorem, 33–37, 66
- Debouncer, 92–93, 158–159
- DEBUG, 253, 255–260, 293–302, 337–340
- Decade counter, 118, 120
- Decimal addition, 284–285, 290–292, 298–300
- Decimal adjust, 280, 284–285, 290, 298
- Decimal flag, 279–281
- Decimal number, 84–85
- Decimal odometer, 1
- Decimal weight, 6
- Decimal-to-binary conversion, 8, 21–22
- Decimal-to-hexadecimal conversion, 13
- Decision-making element, 25
- Decoder:
 - binary-to-decimal, 27
 - binary-to-hexadecimal, 54
 - decimal-to-BCD, 54
 - instruction, 125, 158–159
 - seven-segment, 54
- #Decrement instruction, 178, 180–181, 200, 205, 343
- Define byte, 345, 348, 351
- Delay, 189–190
- Digit, 1
- Digital-to-analog (D/A) converter, 485, 486–489
- Diode ROM, 130–131
- Diode-transistor logic, 48
- Direct addressing, 187, 264–268
- Direct reset, 97
- Direct set, 97
- Disassembler, 222
- Distributive law, 65
- Division, 276, 302
- Don't care condition, 75–77, 95
- Do-nothing state (*see* NOP instruction)
- Double-byte addition, 199
- Double-byte subtraction, 202
- Double-dabble, 8
- Double inversion, 34, 66
- Double-precision number, 274
- Down counter, 118
- Driver, 54
- DTL, 48
- Duality theorem, 66–67
- Dynamic RAM, 133–134
- ECL, 48
- Edge triggering, 96–100
- Effective address, 330
- 8080/8085/Z80 family, 214, 417–422, 502–506
 - addressing, 266–267, 336, 409
 - architecture, 233–235, 329
 - arithmetic instructions, 286–287, 292–293, 391–395, 411–412, 416
 - conditional jump (branch) instructions, 351–352, 402, 413–414, 417
 - CPU control instructions, 381, 410, 415
 - data transfer instructions, 249–253, 381–390, 410–411, 415–416
 - flag instructions, 287–292, 390–391, 408–409, 411, 416
 - increment and decrement instructions, 398–400, 413, 416–417
 - input-output instructions, 408, 415, 417
 - interrupt instructions, 407–408, 415, 417
 - logical instructions, 395–398, 412, 416
 - programming, 511
 - rotate and shift instructions, 323–324, 398, 412–413, 416
 - stack instructions, 406–407, 415, 417
 - subroutine instructions, 370–373, 402–406, 414–415, 417
 - test and compare instructions, 352, 401, 413, 417
 - unconditional jump instructions, 350–351, 400, 413, 417
- 8086/8088 family, 214, 469–470
 - addressing, 267–269, 336–341
 - architecture, 235–237, 329
 - arithmetic instructions, 293–294, 300–302, 447–450, 466
 - conditional jump (branch) instructions, 357–358, 456–459, 467
 - CPU control instructions, 445, 465
 - data transfer instructions, 253–260, 445–446, 466
 - flag instructions, 294–299, 446–447, 466
 - increment and decrement instructions, 455, 467
 - input-output instructions, 462–463, 468
 - interrupt instructions, 461–462, 468
 - logical instructions, 314–317, 450–451, 466
 - loop instructions, 464–465, 468
 - programming, 511
 - rotate and shift instructions, 324–327, 451–455, 467
 - stack instructions, 460–461, 468
 - string instructions, 463–464, 468
 - subroutine instructions, 373–377, 459–460, 468
 - test and compare instructions, 358, 456, 467
 - unconditional jump instructions, 355–357, 455, 467
- Emitter-coupled logic, 48
- ENABLE input, 23
- Encoder, 21–22, 54
- End-of-conversion signal, 492
- Erasable PROM (EPROM), 132, 224
- Even parity, 39, 234
- EXCLUSIVE-NOR gate, 42
- EXCLUSIVE-OR gate, 37–42, 307–309
- Execution cycle, 148–152
- Expandable gate, 56–57
- Expander gate, 56–57
- Extended addressing, 266
- Extended register, 204–205
- Factoring, 69, 70
- Fanout, 52–53
- Fetch cycle, 148, 150, 151, 227
- Fetch microroutine, 152, 161
- Firmware, 243, 247, 251
- First-in-last-out (FILO) structure, 228, 363
- #Flag instructions, 175, 175, 179, 180–181, 187, 227–228, 272–276, 310
- Flip-flop, 90–103
- Floating TTL input, 50–51
- Flowchart, 217, 218–220
- FORTH, 221
- FORTTRAN, 221
- Full adder, 81–82
- Function tables, 499–500
- Fundamental product, 67
- Gate:
 - AND, 22–23, 33–34, 49, 54
 - AND-OR, 55
 - AND-OR-INVERT, 55–57
 - expandable, 56–57
 - NAND, 34–36, 49, 53–55, 118–120
 - NOR, 32–34, 49, 53–54
 - NOT, 19–20
 - OR, 20–22, 36, 54
 - standard TTL, 49
 - XNOR, 42
 - XOR, 37–42, 49
- General-purpose register, 227, 230, 232–236
- Half-adder, 81
- Half-carry flag, 272
- Halt instruction, 143, 151, 185, 241
- Hand-assembly, 178, 183, 244, 248, 251
- Handshaking, 176, 186
- Hardware, 3–4, 213
- Hardwired control, 161
- Hex inverter, 20
- Hexadecimal address, 133, 136–137
- Hexadecimal number, 9–13, 14, 270
- Hexadecimal-to-binary conversion, 10–11, 270
- Hexadecimal-to-decimal conversion, 11–13
- Hex-dabble, 13
- High-level language, 221
- High-speed TTL, 50
- Hold time, 98
- Immediate addressing, 187, 244, 247, 264–268
- Immediate instruction, 176, 184, 201–202, 204, 206
- Implied addressing, 188, 264–267
- IN instruction, 185
- Inactive state, 90
- INCLUSIVE OR (*see* OR gate)
- #Increment instruction, 147, 178, 180–181, 199–200, 205, 343
- Index register, 227, 231, 232, 234, 236, 332, 340
- Indexed addressing, 332, 333–336
- Indexed indirect addressing, 335
- Indirect addressing, 205, 331, 333, 336, 340
- Indirect indexed addressing, 334–335
- Indirect instruction, 205–207
- Inherent addressing, 264–267
- Input gate lead, 69
- Input-output unit, 7
- Input register, 173
- Input unit, 7
- Instruction cycle, 151 (*See also* Machine cycle)
- Instruction decoder, 125, 158–159
- Instruction field, 145
- Instruction pointer, 205, 236, 330
- Instruction register, 125, 141, 153, 174

- Instruction set, 142–144, 240
- Integrated circuit, 4, 48
- Interface circuit (*see* Analog interface)
- Inversion:
 - bubble, 19–20
 - double, 34, 66
 - sign, 19, 23–24
 - symbol, 19–20
- Inverter, 19–20, 41–42
- I/O unit, 7
- Italic notation, 25
- JK* flip-flop, 99–103
- JK* master-slave flip-flop, 100–103
- Jump flag, 187
- #Jump instruction, 173, 179–180, 182, 183, 202–204, 342–343
- K- (kilo-), 7
- K* input, 99–100
- Karnaugh maps, 70–77
- Label, 181–182
- Ladder, 490–491
- Large-scale integration, 48
- Latch, 90–96
- LDA instruction, 142, 148, 149, 176
- LDA microroutine, 161–162
- LED display, 3
- Level clocking, 93–97, 102
- Light-emitting diode, 3
- Load the accumulator instruction, 142, 148, 149, 176, 242–248, 252–253
- Loading:
 - parallel, 110
 - serial, 108–110
 - TTL device, 52–53
- Logic circuit, 19, 68
- #Logical instructions, 305–308
- Loop, 181, 218–219, 342–344
- Loop counter, 181
- Low-level language, 221
- Low-power Schottky TTL, 50, 52–53
- Low-power TTL, 50
- LSB (least significant byte), 274, 488
- LSI, 48
- Machine cycle:
 - definition, 151
 - fixed, 161–162, 163
 - variable, 163–164
- Machine language, 145, 146, 220, 221, 337
- Machine phase (*see* *T* state)
- Macroinstruction, 152–153
- Magnetic core, 5
- Magnetic tape, 5
- Manual assembly, 221
- Manual-auto debouncer, 158–159
- Mapping (*see* Address mapping)
- MAR, 140, 153, 174
- Mask, 131, 186, 306–308
- Master-slave flip-flop, 100–103
- Medium-scale integration, 48
- Memory, 5–7, 130–137, 224, 268
- Memory address register, 140, 153, 174
- Memory data register, 174
- Memory element, 90–103
- Memory enable (*see* Chip enable; Write enable)
- Memory-intensive architecture, 329
- Memory location, 10–12, 331, 507–510
- Memory-reference instruction, 143–144, 176–177
- Memory register (*see* Memory location)
- Memory state, 147
- Microcode (*see* Microprogram)
- Microcomputer, 7
- Microcontroller, 161–164
- Microinstruction, 152
- Microprocessor, 7, 213–216, 226–237, 270–271
- Microprocessor families (*see* 8080/8085/Z80 family; 8086/8088 family; 6502 family; 6800/6808 family)
- Microprogram, 152–153, 161–164
- Microroutine (*see* Microprogram)
- Mnemonic, 143, 221
- Modulus, 116–120
- Monitor, 174, 241
 - assembly, 222
- Monotonic D/A converter, 489
- MOS families, 48
- Move instruction, 177–178, 195–196, 199, 206
- MRI, 143–144, 176
- MSB (most significant bit), 200, 273, 274, 492
- MSI, 48
- Multiplexer, 58–60, 153
- Multiplication, 182, 183, 276, 300–302
- MVI, 189, 195–196, 199
- NAND gate, 34–36, 49, 53–55, 118–120
- NAND latch, 92–95
- Natural modulus, 120
- n-channel MOSFETs, 48
- NEG instruction, 308, 311–312, 316–317
- Negative (sign) flag, 275, 277–278, 282–283
- Negative clocking, 94
- Negative logic, 25
- Negative toggle, 118
- Nesting, 343–344
 - loop, 343–344
 - subroutine, 189–190, 364, 367, 369–371, 373–374
- Nibble, 13–14
- NMOS, 48
- No operation instruction, 241, 242, 245, 249
- Noise margin, 52
- Noninverter, 20
- Nonsaturated circuit, 4–5
- Nonvolatile memory, 133
- NOP instruction, 148, 185, 241, 242
- NOR gate, 32–34, 49, 53–54
- NOR latch, 91, 92
- NOT gate, 19–20
- NOT instruction, 308, 315–316
- Notation:
 - boldface, 42
 - italic, 25
 - positional, 11–12
 - roman, 25
- Number:
 - binary, 2, 3, 6–15, 270, 271, 274
 - binary-coded-decimal, 13–14, 270–271
 - decimal, 1, 84–85
 - hexadecimal, 9–13, 14, 270
 - (*See also* Conversion)
- Object code, 221
- Object program, 145
- Octet, 72, 73
- Odd parity, 39, 234
- Odd-parity generator, 40
- Odd-parity tester, 39
- Odometer, 330
 - binary, 1–2, 84
 - decimal, 1
 - hexadecimal, 9
- Offset, 332
- On-chip decoding, 131, 132
- 1's complement, 41–42, 312
- Open-collector gate, 58
- Operand, 145, 176
- Operation code, 144, 176–177, 241
- Operational amplifier (op amp), 485–486
- OR gate, 20–22, 36, 54
- OR instruction, 65, 66, 184, 306–307, 309, 310, 313, 314–315
- OR sign, 24
- OUT instruction, 143, 150–151, 185
- Output buffer, 493
- Output register, 7, 106–107, 110, 142, 158, 176
- Overflow, 87, 196, 272–274, 279, 284, 288–289, 296–297
- Overlapping, 74
- Paging, 263–264
- Pair, 72
- Parallel loading, 110
- Parameter passing, 183
- Parity, 39, 234
- Parity flag, 203, 288–289, 296
- Parity generator, 39–40
- Pascal, 221
- PC, 113, 140, 147, 153
- p-channel MOSFETs, 48
- Phase (*see* *T* state)
- Pinouts, 499–500
- PMOS, 48
- Pointer, 140, 205, 227
- POP instruction, 209–210
- Port instruction, 185–186
- Positional notation, 11–12
- Positive clocking, 94
- Positive logic, 25
- Positive toggle, 118
- Power dissipation, 49
- Power of 2, 7
- Power supply, 158
- Preset, 97
- Presetable counter, 118–120, 162
- Prime memory (*see* Dynamic RAM; Static RAM)
- Program, 3, 216
- Program counter, 113, 140, 147, 153, 173, 227, 230–232, 234, 330
- Program direct addressing, 268
- Program indirect addressing, 340
- Program relative addressing, 337–338
- Program status word, 208
- Programmable modulus, 120
- Programmable ROM (PROM), 131–132, 224
- Programmed multiplication, 182, 183
- #Programming, 135–136, 216–222
 - data transfer instructions, 241–260
 - models, 511
- PROM, 131–132, 224
- Propagation delay time, 49, 98
- Punched cards, 5
- PUSH instruction, 208–209 (*See also* Stack)
- Pushing and popping registers, 366, 367–368, 370, 371, 374
- Quad, 72–73
- Race condition, 91, 94, 95, 100
- Radix, 6–7
- RAL instruction, 185, 200, 201
- Random-access memory (RAM), 133–137, 153, 224
- RAR instruction, 185, 200, 201
- Read-only memory (ROM), 130–133, 161–164, 224

- Redundant Karnaugh group, 74–75
- Refresh, 133–134
- Register, 4, 217
 - bidirectional, 173
 - buffer, 54, 106–107, 110, 122
 - controlled, 106–110
 - CPU, 195–196
 - 8-bit, 229–230
 - input, 173
 - output, 7, 106–107, 110, 142, 158, 176
 - pair, 204
 - shift, 108–110
 - shift-left, 108, 109
 - shift-right, 108, 109
 - 16-bit, 230
 - three-state, 121–122
 - transfers, 122–123
 - width of, 229–230
- (See also specific types of register)
- Register addressing, 188, 264–268
- Register indirect addressing, 336, 338–340
- Register-intensive architecture, 329
- Register parameter passing, 183
- Register relative addressing, 337
- Relative accuracy, 488–489
- Relative addressing, 330, 332–333, 335, 337–338
- Reset-and-carry, 1
- Resolution, 488
- Return instruction, 180, 210–211, 364–366
- Ring counter, 114–116, 146–147, 159–161
- Ripple counter, 110–113
- Rolling, Karnaugh map, 74
- ROM (see Read-only memory)
- Roman notation, 25
- #Rotate instruction, 185, 200, 319–321
- RS latch, 90–94
- SAP–1, 140–164
 - counters, 106, 107, 113, 116, 117
 - parts list, 501
 - RAM, 115–116
- SAP–2, 144, 151, 173–193
- SAP–3, 144, 195–212
- Saturated circuit, 4
- Saturation delay time, 4, 50
- Schmitt trigger, 54–55
- Schottky TTL, 50, 52–53
- Segment register, 236
- Serial data stream, 191–193
- Serial loading, 108–110
- Settling time, 489
- Setup time, 98
- Seven-segment decoder, 54
- #Shift instruction, 319, 320
- Shift register, 108–110
- SHL control, 108–110
- Sign bit, 83
- Sign flag, 175, 179, 180–181, 287, 294–296
- Signed binary number, 83, 272, 284, 289
- Sign-magnitude number, 83
- Single-precision number, 274
- Single-step debouncer, 158–159
- Sink, 52
- 6502 family, 214, 481–483
 - addressing, 265, 332–335, 476, 477
 - architecture, 230–231, 329
 - arithmetic instructions, 276–277, 472, 478, 480–481
 - conditional jump (branch) instructions, 345–346, 475, 479–480, 481
 - CPU control instructions, 242, 471, 478, 480
 - data transfer instructions, 242–245, 471–472, 478, 480
- 6502 family (Cont.):
 - flag instructions, 277–281, 472, 476–478, 480
 - increment and decrement instructions, 473–474, 479, 481
 - input-output instructions, 476, 480, 481
 - interrupt instructions, 476, 480, 481
 - logical instructions, 308–310, 472–473, 478–479, 481
 - programming, 511
 - rotate and shift instructions, 321–322, 473, 479, 481
 - stack instructions, 475–476, 480, 481
 - subroutine instructions, 366–369, 475, 480, 481
 - test and compare instructions, 346, 474, 479, 481
 - unconditional jump instructions, 344, 474, 479, 481
- 6800/6808 family, 214, 434–437, 443, 444
 - addressing, 265–266, 335–336, 433
 - architecture, 329, 632–633
 - arithmetic instructions, 281–282, 285–286, 424–425, 438, 441
 - conditional jump (branch) instructions, 348–349, 429–431, 440, 442
 - CPU control instructions, 422, 437, 441
 - data transfer instructions, 245–249, 423, 437, 441
 - flag instructions, 282–285, 423–424, 433, 437–438, 441
 - increment and decrement instructions, 428, 439, 442
 - input-output instructions, 432, 441, 442
 - interrupt instructions, 432, 441, 442
 - logical instructions, 310–314, 425–426, 438–439, 441–442
 - programming, 511
 - rotate and shift instructions, 322–323, 426–427, 439, 442
 - stack instructions, 431–432, 440–441, 442
 - subroutine instructions, 369–370, 431, 440, 442
 - test and compare instructions, 349, 428–429, 439, 442
 - unconditional jump instructions, 347–348, 428, 439, 442
- Small-scale integration, 48
- Software, 3–4, 218
- Software emulation program, 215
- Source, 52
- Source code, 221
- Source program, 145
- SSI, 48
- #Stack, 195, 207–211, 228–229, 231, 233, 234, 236, 363–364
- Stack pointer, 195, 207–208, 228–229, 231, 233, 234, 236, 363–364, 366–367, 369, 371, 373
- Stack segment, 338
- Standard TTL, 49–52
- State diagram, 117
- Static RAM, 133–134
- Status register, 227–228, 231–234, 236
- Store the accumulator, 176
- Straight-line program, 218
- String, 1
- #Subroutine, 180, 219, 363–377
 - branching vs., 364
 - nested, 189–190, 364, 367, 369–371, 373–374
 - pushing and popping registers, 366, 367–368, 370, 371, 374
- #Subroutine (Cont.):
 - return instruction, 180, 210–211, 364–366
 - stack and stack pointer, 363–364, 366–367, 369, 371, 373
- Subtract instruction, 143, 150, 178, 198–199
- Subtraction, 80–81, 86–87, 202, 275, 285–286, 292–293, 300
- Subtraction-with-carry (borrow), 196, 275–276, 281
- Successive-approximation method, 492–493
- Sum-of-products circuit, 67–68
- Switch, current, 487–488
- Switch debouncer, 92–93
- Synchronous counter, 113–114
- T state, 146–151, 187
- Temporary register, 175
- Three-state RAM, 134
- Three-state register, 121–122
- Three-state switch, 121
- Time delay, 189–190
- Timing diagram, 91, 92, 94, 95
- Timing signal, 36, 116
- Timing state, 146–151
- Toggle, 99–100, 102, 118
- Totem-pole output, 49
- Trace command, 293
- Traffic light, 190–191
- Trainer, microprocessor, 215
- Transistor, 4
 - inverter, 19
 - latch, 90–91
 - register, 4
- Transistor-transistor logic, 48–63
- Transparent latch, 95
- Triple-precision number, 274
- Tristate switch, 111–112
- Truth table, 20, 21
 - deriving logic circuit from, 68
 - JK master-slave, 102
 - Karnaugh maps from, 70–77
 - transistor latch, 90–91, 94
- TTL, 48–63, 120, 135–136, 497–498
- 2's complement, 83–87, 312, 331
- Two-state design, 4–6
- #Unconditional jump, 179, 180, 342
- Universal logic circuit, 60
- Unsigned binary number, 272, 284, 289–290
- Up-down counter, 118
- Virtual ground point, 485
- Volatile RAM, 134
- Weight:
 - binary, 6
 - decimal, 6
 - hexadecimal, 11–12
- Weighted resistors, 489
- Word, 20, 208
- Word comparator, 42–43
- Word multiplexer, 60
- Worksheet, 222
- Worst-case TTL characteristics, 50–51
- Write enable, 134
- XNOR gate, 42
- XOR gate, 37–42, 49
- XOR instruction, 313, 315
- XRA instruction, 184
- XRI instruction, 184
- Zero flag, 175, 179, 180–181, 275, 278–279, 283–284, 287–289, 296, 332
- Zero page addressing, 333–334