

Military Institute of Science and Technology
Department of Computer Science and Engineering
CSE-17A, Level-3, Term-II
CSE-316 (Digital System Design Sessional)
Project-2

Instructions:

1. Design the 4-bit ALU with full adder and basic gates [Use of multiplexer is strictly prohibited].
2. In next week first you have to submit the design of the ALU [Hardcopy(in paper) and softcopy(in Circuit Maker) both].
3. Then in next to next week you have to submit the final hardware connection.
4. Finally you have to submit a report on ALU.

Problem (Grp-1 & Grp-2):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = A$	Transfer A
$F = A + 1$	Increment A
$F = A - B - 1$	Subtract with borrow
$F = A - B$	Subtraction
$F = A \text{ OR } B$	OR
$F = A \text{ AND } B$	AND

Problem (Grp-3 & Grp-4):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = A + B$	Addition
$F = A + B + 1$	Add with carry
$F = A - 1$	Decrement A
$F = A$	Transfer A
$F = A \text{ XOR } B$	Exclusive-OR
$F = A'$	Complement A

Problem (Grp-5 & Grp-9):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = B - A - 1$	Subtract with borrow
$F = B - A$	Subtraction
$F = B - 1$	Decrement B
$F = B$	Transfer B
$F = A \text{ XOR } B$	Exclusive-OR
$F = B'$	Complement B

Problem (Grp-6 & Grp-7):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = A + B$	Addition
$F = A + B + 1$	Add with carry
$F = A - B - 1$	Subtract with borrow
$F = A - B$	Subtraction
$F = A \text{ XOR } B$	Exclusive-OR
$F = A \text{ XNOR } B$	Exclusive-NOR

Problem (Grp-8 & Grp-10):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = A - B - 1$	Subtract with borrow
$F = A - B$	Subtraction
$F = A - 1$	Decrement A
$F = A$	Transfer A
$F = A \text{ XNOR } B$	Exclusive-NOR
$F = A'$	Complement A

Problem (Grp-11):

Design a 4-bit Arithmetic Logic Unit (ALU), which generates the following operations. Also show four status register (Sign flag, Carry flag, Overflow flag, Zero flag).

Operation	Function
$F = A$	Transfer A
$F = A + 1$	Increment A
$F = A - 1$	Decrement A
$F = A$	Transfer A
$F = A \text{ OR } B$	OR
$F = A'$	Complement A