

\* Fall time is found to match with actual data

\* But rise time ( $t_r$ ) is found to be

$$t_r = \frac{60 C_{out}}{W_2/L_2} \text{ ns}$$

• This is because of body effect

• As the output rises, the threshold voltage of  $T_2$  also rises, reducing current to delay the rise time

Example:

$T_1 \Rightarrow$  aspect ratio  $3/1$

$T_2 \Rightarrow$  "  $1/2$

input Capacitance = 0.05 pF

output " = 0.10 pF

$$t_r = \frac{60 \times 0.10 \times 10^{-12}}{1/2} \text{ ns} = 12 \text{ ns}$$

$$t_f = \frac{35 C_{out}}{3/1} = \frac{42 \times 0.10}{1/2} = 35 \times 0.10 \times \frac{1}{3} = 1.2 \text{ ns}$$

$$t_r = 12 \text{ ns}$$

$$t_f = 1.2 \text{ ns}$$

Maximum freq (in hertz)  
at which the gate can operate  
$$= \frac{1}{t_r + t_f}$$



## 2.11 Ratioed and Ratioless Design

\* previously, we have seen depends on aspect ratio  $W_1/L_1$  and  $W_2/L_2$

\* So it is necessary to choose suitable gate geometry to obtain desired output.

↳ Ratioed Circuits

The  $W/L$  ratio determines

(i) Circuit speed since edge times are inversely proportional to  $W/L$

$$t_{\text{tr}} \propto \frac{1}{W_2/L_2}$$


$$t_{\text{f}} \propto \frac{1}{W_1/L_1}$$

(ii) Power dissipation is also determined by gate geometry. Since current flow through a device is dependent on its aspect ratio.

Ratioed  
Ckt




# Ratioless Design

 

- \* Both switch will NOT be closed at the same time
- \* One switch is closed, another remains OPEN.
- \* No current flows bet<sup>n</sup>  $V_p$  and 0.
- So no static power dissipation.

- \* However, both switches may get closed at transition states, causing transient current flow.
- \* Output voltage does not depend on aspect ratio. So ratioless inverter

## 2.12 CMOS Inverter

 

(i) When  $V_{in} = 0$ ,

\* NMOS ( $T_1$ ) off

\* PMOS  $\Rightarrow V_{sg} = V_s - V_g = 5 - 0 = 5 > V_{tp}$

So PMOS on.

\* The current flow through  $T_1$  is very less (only some leakage current).

\* So voltage drop across  $T_2$  is 0.

Hence  $V_{out} = 5V$

$T_2$  For  $V_{in} = 0V$ ,

$$V_{sg} = 5 - 0 = 5, \quad V_{tp} = 1$$

$$V_{sg} - V_{tp} = 4$$

$$V_{sd} = V_p - V_{out} = 5 - V_{out}$$



So When  $V_{out} = 0$  to  $1V$

$$V_{sd} = 5 - V_{out} \approx \text{between } 5 \text{ to } 4 \text{ volt}$$

$$\text{So } V_{sd} \geq V_{sg} - V_{tp}$$

# Hence  $T_2$  is in Sat<sup>n</sup> region when  $V_{out} = 0$  to  $1V$

# Otherwise,  $T_2$  is in Resistive region

(ii) When  $V_{in} = 5V$

$$T_2 \Rightarrow V_{sg} = 5 - 5 = 0V,$$

So  $T_2$  off (PMOS off)

$$T_1: V_{gs} = 5 - 0 = 5, T_1 \text{ (NMOS)} \Rightarrow \text{on}$$

$$\text{So } V_{ds1} = V_{out} = 0V$$

$$V_{gs} - V_t = 5 - 1 = 4$$

$$V_{ds} = 0V$$

$$\therefore V_{ds} < V_{gs} - V_t \quad \text{for } T_1$$

So  $T_1$  is ~~sat~~ resistive region

If the current capability of  $T_1$  and  $T_2$  during switching is the same, the rising and falling edge will be equal.