

# **ANALOG INTERFACING AND INDUSTRIAL CONTROL (PART II)**

**Book: Microprocessors and Interfacing-Douglas V. Hall (Chapter 10)**

Prepared By: Anika Binte Islam, Lecture, CSE Dept, MIST

# Microcomputer based smart scale

- ❑ Load cell converts applied weight into a proportional electrical signal
- ❑ It is then amplified and converted into a digital value
- ❑ Can be read by the microprocessor and sent to the attached display
- ❑ User can enter price per pound by using keyboard
  - ❑ Shown on the display
- ❑ When the user presses compute key on the keyboard
  - ❑ Microprocessor multiplies the weight times the price per pound and displays the computed price
- ❑ After holding the price display long enough for the user to read it, the scale goes back to reading the weight and displaying it


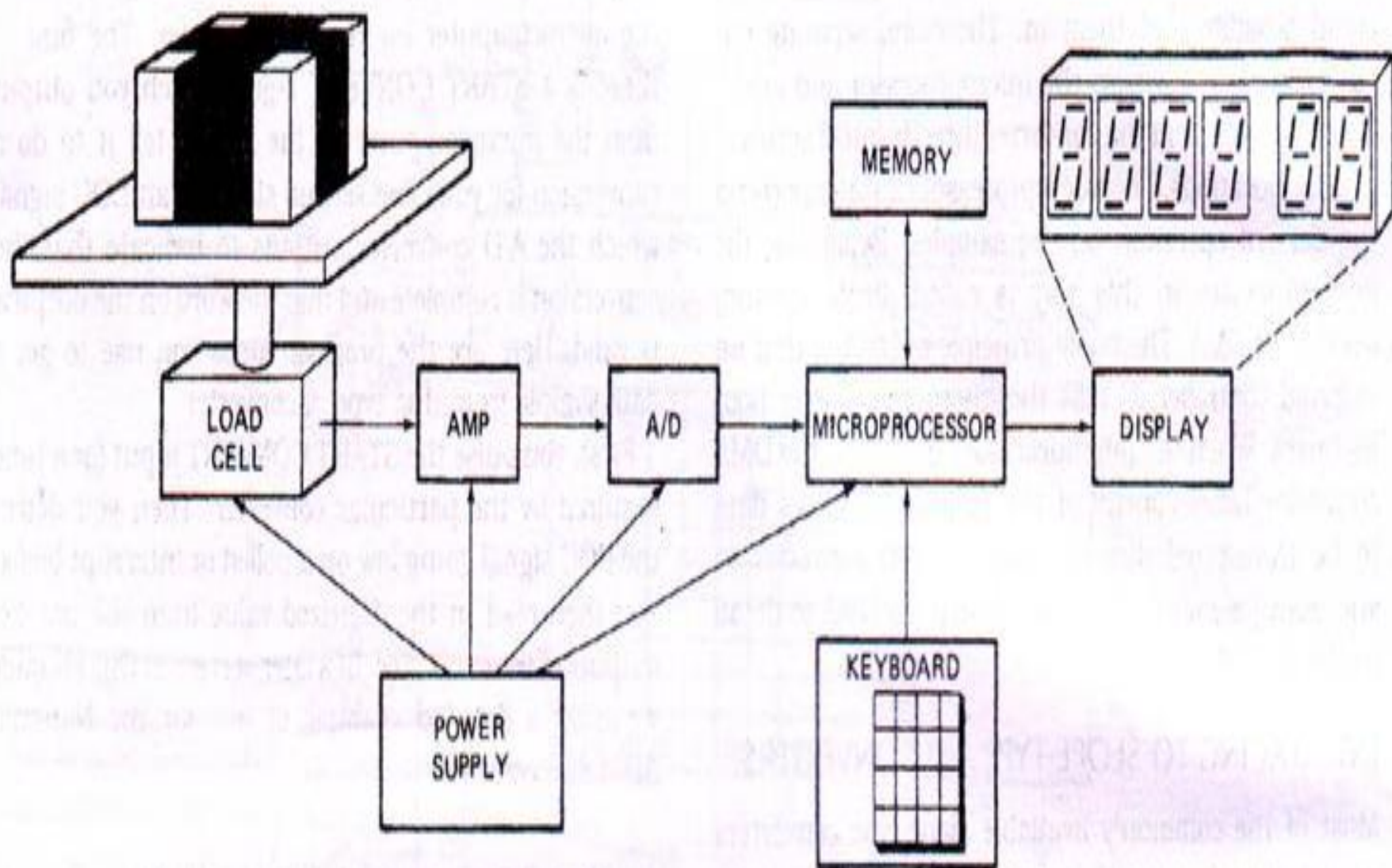


FIGURE 10-22 Block diagram of microcomputer-based smart scale.

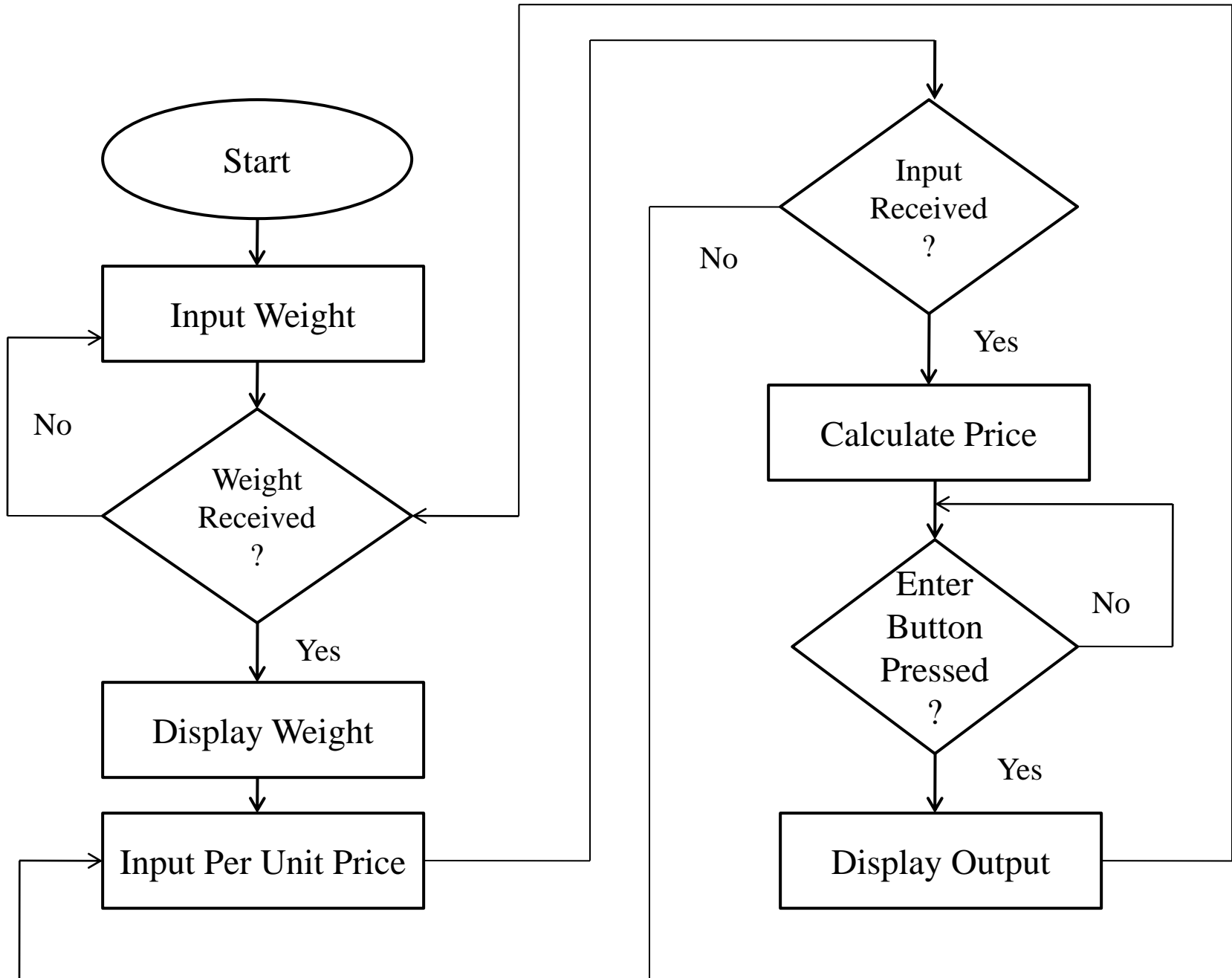

# Microprocessor Based Industrial Control System

- ❑ One area in which microprocessors and microcomputers have had a major impact is industrial process control.
- ❑ Process control involves first measuring system variables such as motor speed, temperature, the flow of reactants, the level of liquid in a tank, the thickness of a material etc.
- ❑ The output of the controller then adjusts the value of each variable until it is equal to a predetermined value called a *set point*.
- ❑ System controller must maintain each variable as close as possible to its set point value.
- ❑ It must compensate as quickly and accurately as possible for any change in the variable caused by, for example , increased load on the motor.

# Controlling the Speed of a dc motor

- ❑ A dc generator or tachometer is attached to the shaft of the motor .
- ❑ It puts out a voltage proportional to the speed of the motor.
- ❑ A fraction of the tachometer output voltage is fed back to the inverting input of the power amplifier driving the motor.
- ❑ In the non-inverting input of the amplifier, a positive voltage is applied as set point.
- ❑ When the power is turned on, the motor accelerates
  - ❑ Until voltage fed back from the tachometer is nearly equal to the set point voltage.

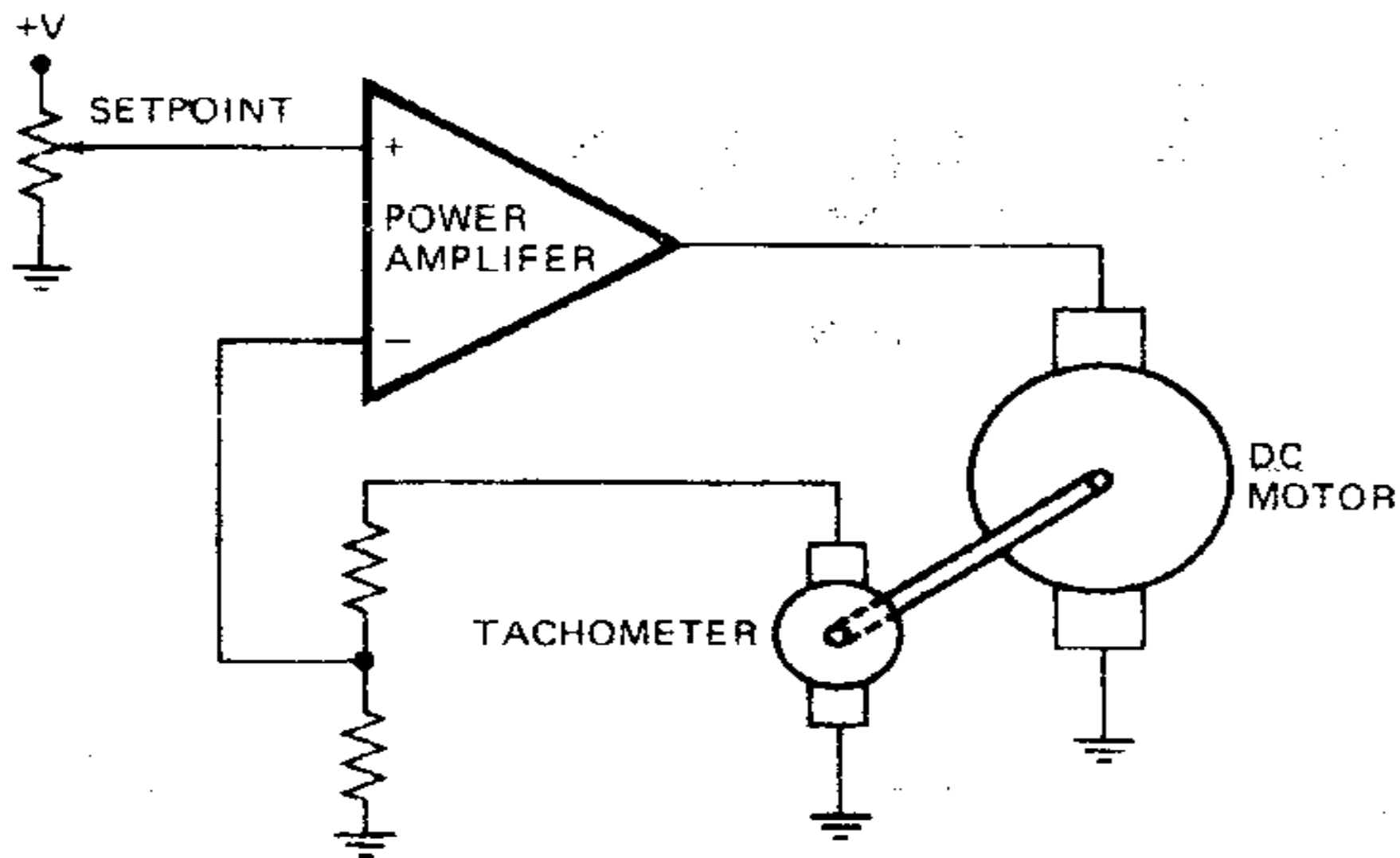


FIGURE 10-27 Circuit for controlling speed of dc motor using feedback from tachometer.

# Controlling the Speed of a dc motor

- ❑ If the load on the motor is increased, the motor will initially slow down
  - ❑ Voltage output from the tachometer will decrease
    - ❑ Increase the difference in voltage between the inputs of the amplifiers
      - ❑ Cause it to drive more current in the motor.
- ❑ Now, the increased current will increase the speed of the motor to nearly the speed it had before the increased load has added
- ❑ The similar reaction takes place if the load on the motor is decreased






# Problems

- ❖ For the applications in which the load and/or the set point changes drastically, there are several potential problems

## ❑ Overshoot
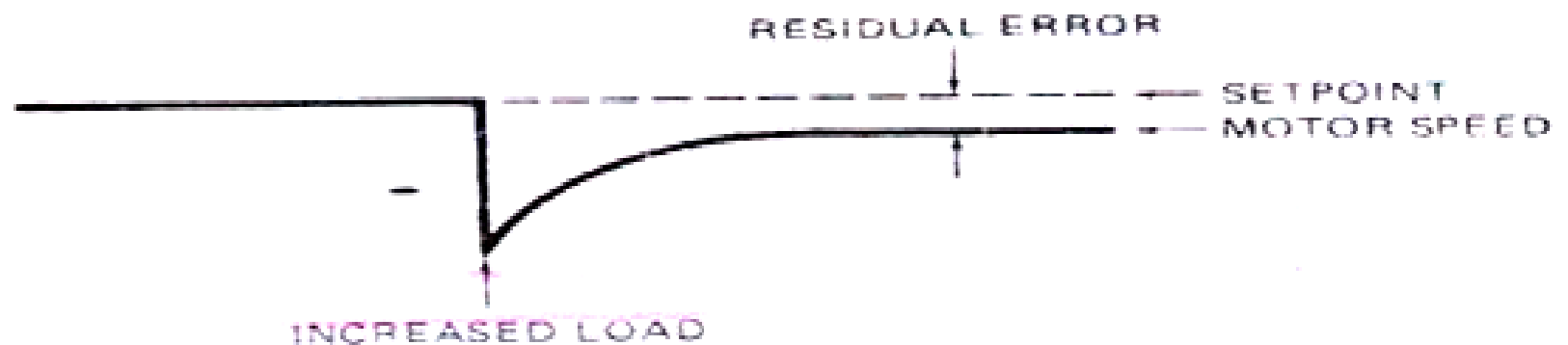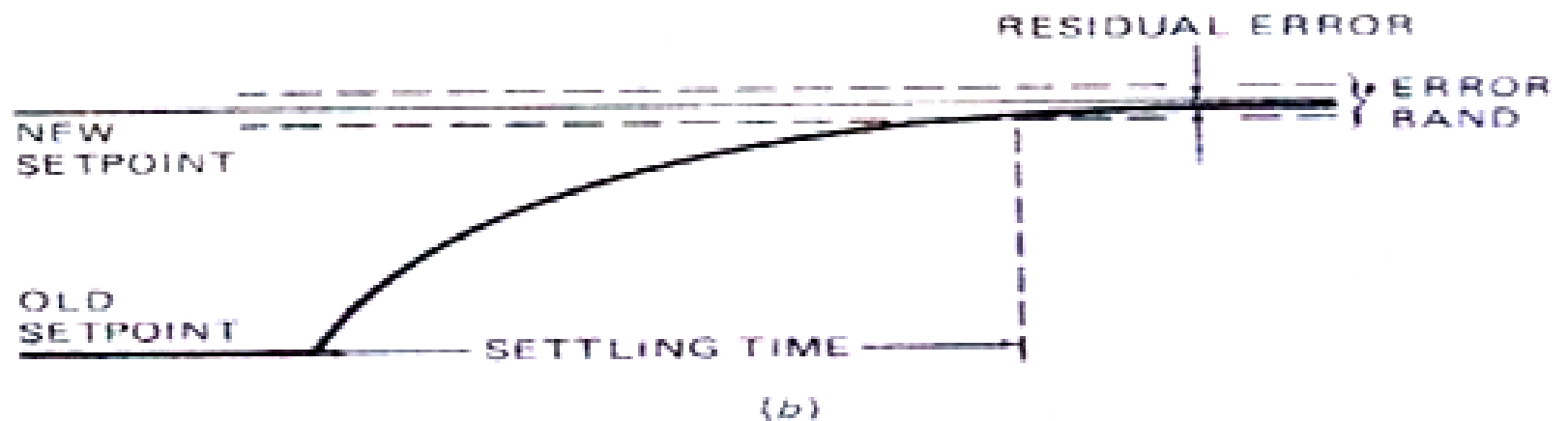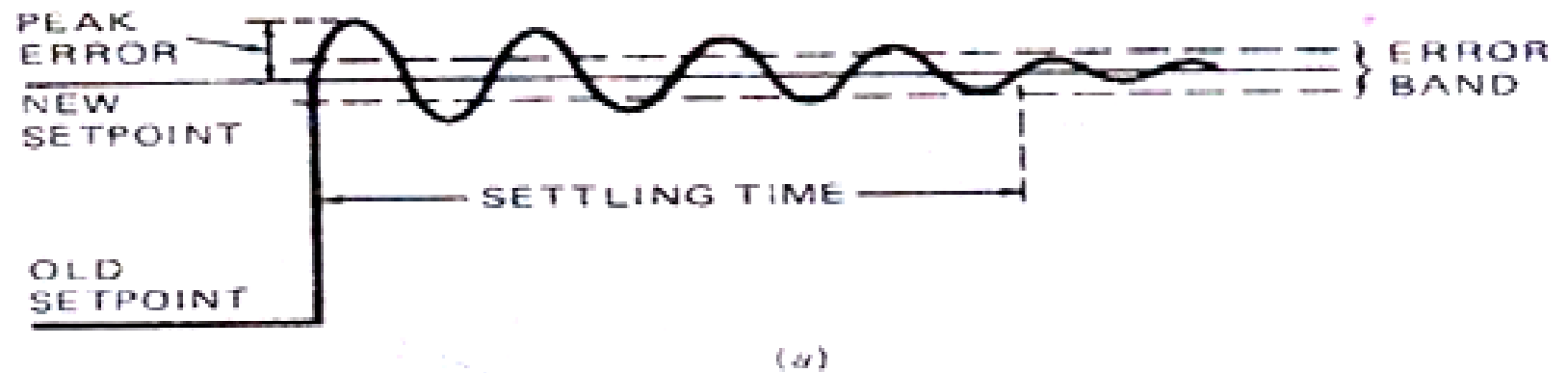
### ➤ When the set point is changed

- In this case, the variable- motor speed (for example) overshoots the new set point and bounces ups and downs for a while.
- The time it takes the bouncing to settle within a specified error range or error band is called the *settling time*.
- This type of response is referred to as *underdamped*.
- Damping can be added.



# Problems

## ❑ Undershoot

- If too much damping is added.
- This type of response is referred to as an over-damped response.
- The difficulty is that it takes a long time for the variable to reach the new set point.

## ❑ Residual Error

- There is some noticeable difference between the set point and the voltage fed back from the tachometer.
- This difference is amplified by the gain of the amplifier to produce the additional drive for the motor.
- For stability reason, gain of many control systems cannot be too high.
- Therefore some residual error always exists between the set point and actual output.

# Solution-PID Controller

- ❑ Circuits with more complex feedback are used
- ❑ Here the power amplifier is an adder with 4 inputs
- ❑ The current supplied to the summing point of the adder by the set point input produces the basic drive output current
- ❑ If there is no difference between the set point and the feedback voltage from the tachometer
  - ❑ Other 3 inputs do not supply any current
- ❑ Amplifier 1 compares the set point value with the feedback voltage from the tachometer
- ❑ If speed of the motor is at set point value
  - ❑ Amplifier 1 output will be zero
  - ❑ Amplifier 2,3,4 will contribute no current to the summing junction of the power amp

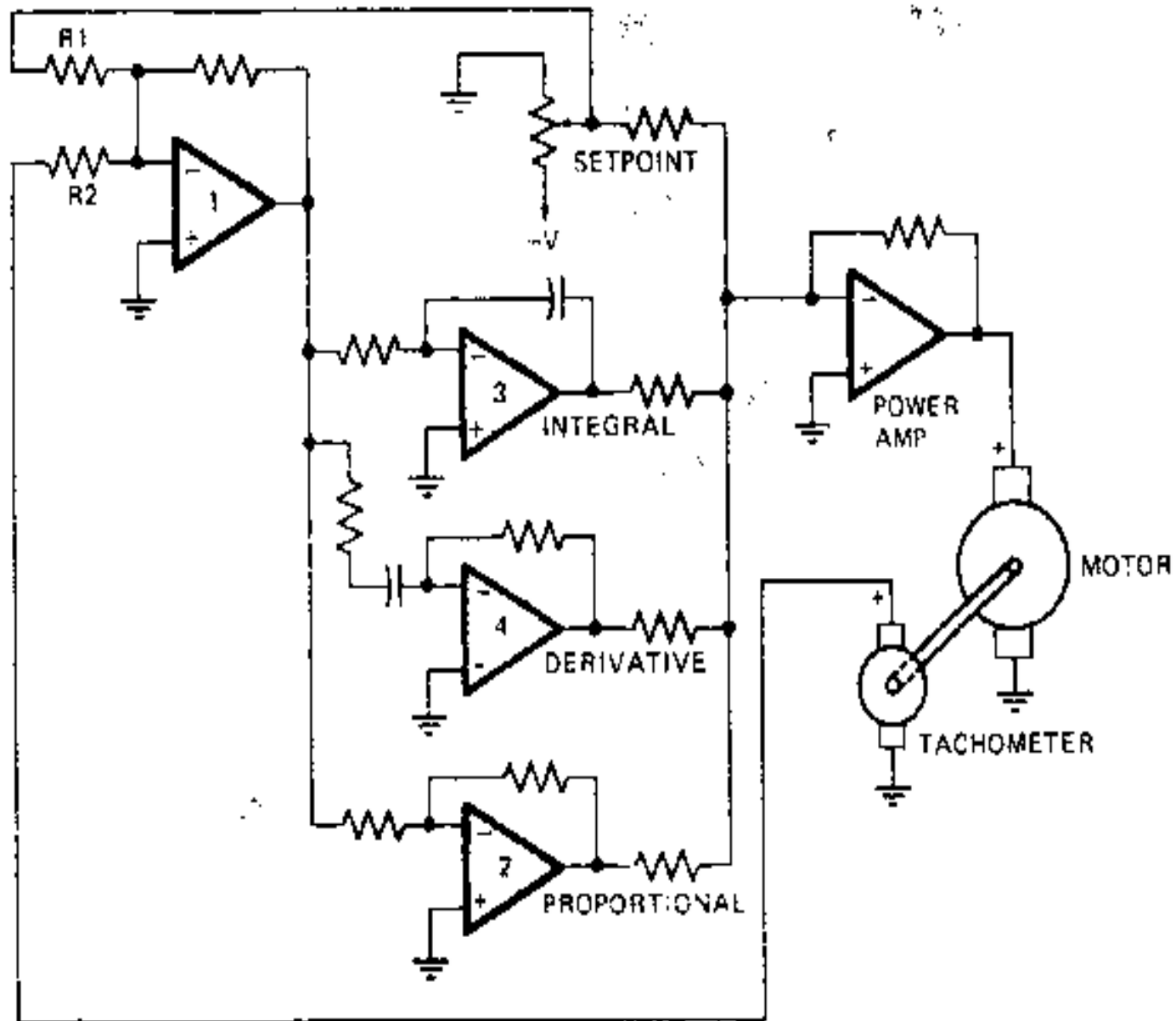


FIGURE 10-29 Circuit showing proportional, integral, and derivative feedback control.

# Solution-PID Controller

- ❑ If speed of the motor is not at set point value
  - ❑ Amplifier 1 now has some output
  - ❑ Amplifier 2,3,4 produces three types of feedback of this error signal to the summing junction of the power amp
- ❑ Amplifier 3 provides integral feedback
  - ❑ The cure for residual error
- ❑ Amplifier 4 improves the response time of the system
  - ❑ Provides derivative feedback
  - ❑ Produces signal, proportional to the rate of the change of the error signal
  - ❑ If the load on the system is suddenly changed, this circuit will give a quick feedback to try to correct the error

# Solution-PID Controller

- ❑ By using combination of these types of feedback , a system can be adjusted for optimum response to changes in load or set point
- ❑ Amplifier 2 provides proportional feedback
- ❑ Process control loops that uses all these three types of feedback are called *proportional Integral derivative* or PID control loops