

2.10 Edge times for NMOS inverter with a depletion


Load

Charging of load capacitor

is done from V_p to V_L through transistor T_2 .

Thus, $V_{out} = 5V$ after charging finishes.

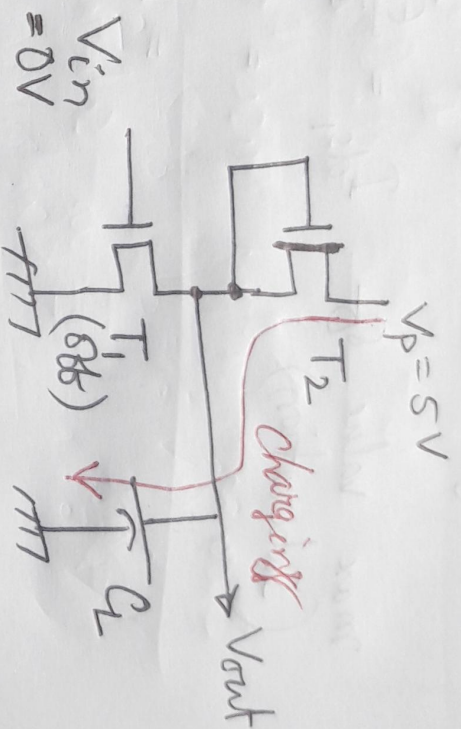
So I_{ds2} plays the role while charging.



Discharging

when $V_{in} = 5V$, T_1 is on

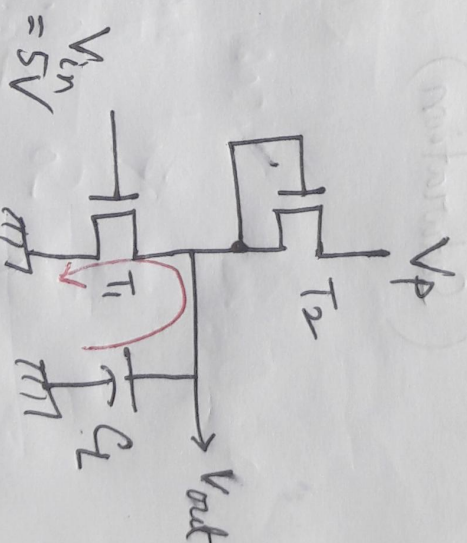Now C_L is discharged through T_1 to ground (0V)




So I_{ds1} plays the role while discharging.

t_r = rise time

= output voltage rises from 0 to 5V

The more value of I_{ds2} ,
the quicker V_{out} rises
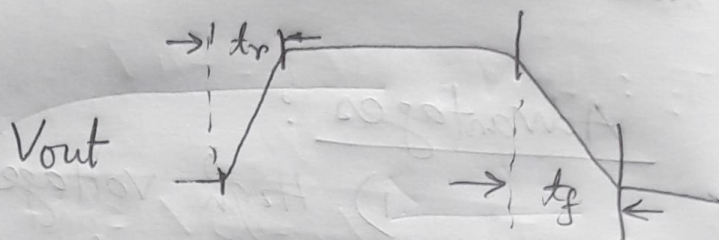
$$\text{So } t_r \propto \frac{1}{I_{ds2}}$$



Similarly $t_f \propto \frac{1}{I_{ds1}}$
fall time



$$\begin{aligned} \text{max value of } I_{ds1} &= \frac{\epsilon \mu_n}{D} \times \frac{W_1}{L_1} \times \frac{1}{2} (V_{gs1} - V_t)^2 \\ (\text{Saturation}) &= 30 \times \frac{W_1}{L_1} \times \frac{1}{2} (5-1)^2 \\ &= 240 \left(\frac{W_1}{L_1} \right) \mu A \end{aligned}$$

$$\begin{aligned} \text{max value of } I_{ds2} &= \frac{\epsilon \mu_n}{D} \times \frac{W_2}{L_2} \times \frac{1}{2} (V_{gs2} - V_{td})^2 \\ (\text{Saturation}) &= 25 \times \frac{W_2}{L_2} \times \frac{1}{2} (0+4)^2 \\ &= 200 \left(\frac{W_2}{L_2} \right) \mu A \end{aligned}$$

$$\frac{t_r}{t_f} = \frac{I_{ds1}}{I_{ds2}} = \frac{240}{200} \times \frac{(W_1/L_1)}{(W_2/L_2)}$$

$$\therefore \boxed{\frac{t_r}{t_f} = \frac{6K}{5}}$$

Let total output capacitance = C_{out}

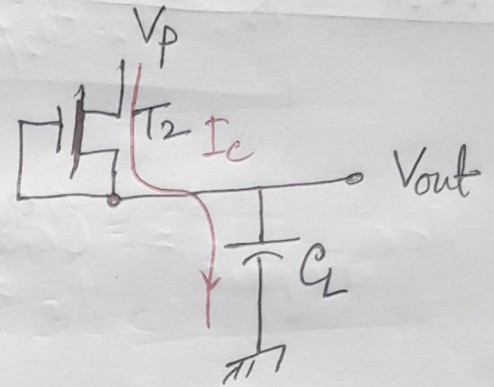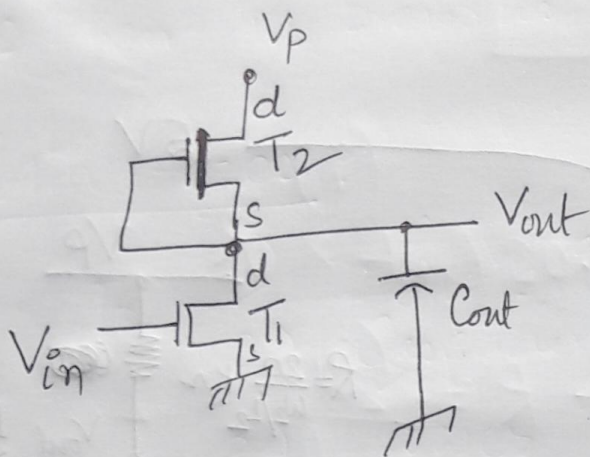

Let $V_{in} = 5V$, $V_{out} = 0.3V$


Now if $V_c = 0.3V$, then

T_1 turns off (see red)
 T_2 remains ON
 C_L gradually charges to $5V$


The current I_c is proportional to rate of change of output voltage

$$I_c = C_{out} \frac{dV_{out}}{dt}$$

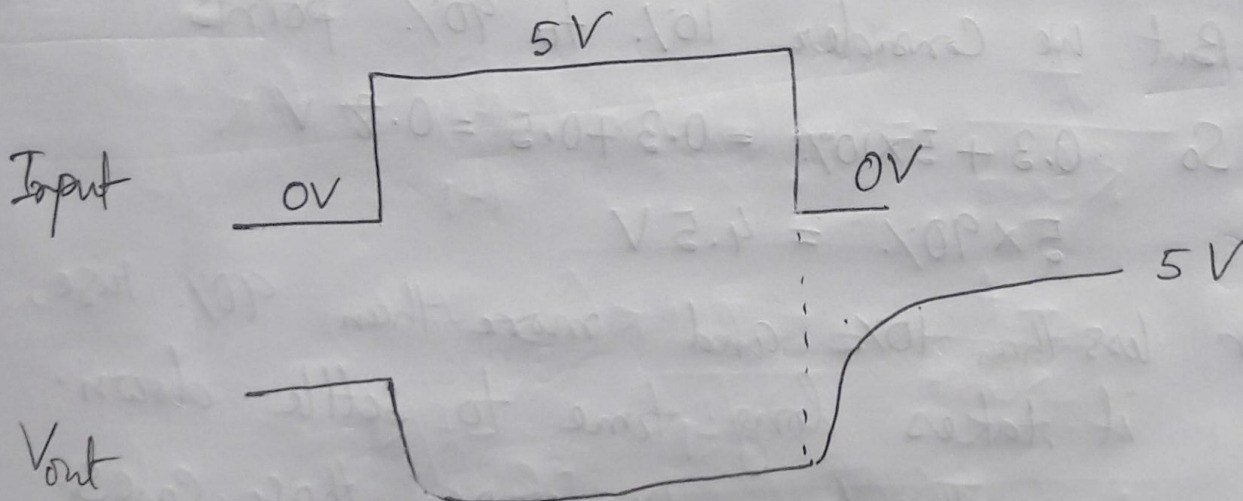The rise time depends on current I_c . Thus, in turn, the rise time depends on T_2



Rise time behavior

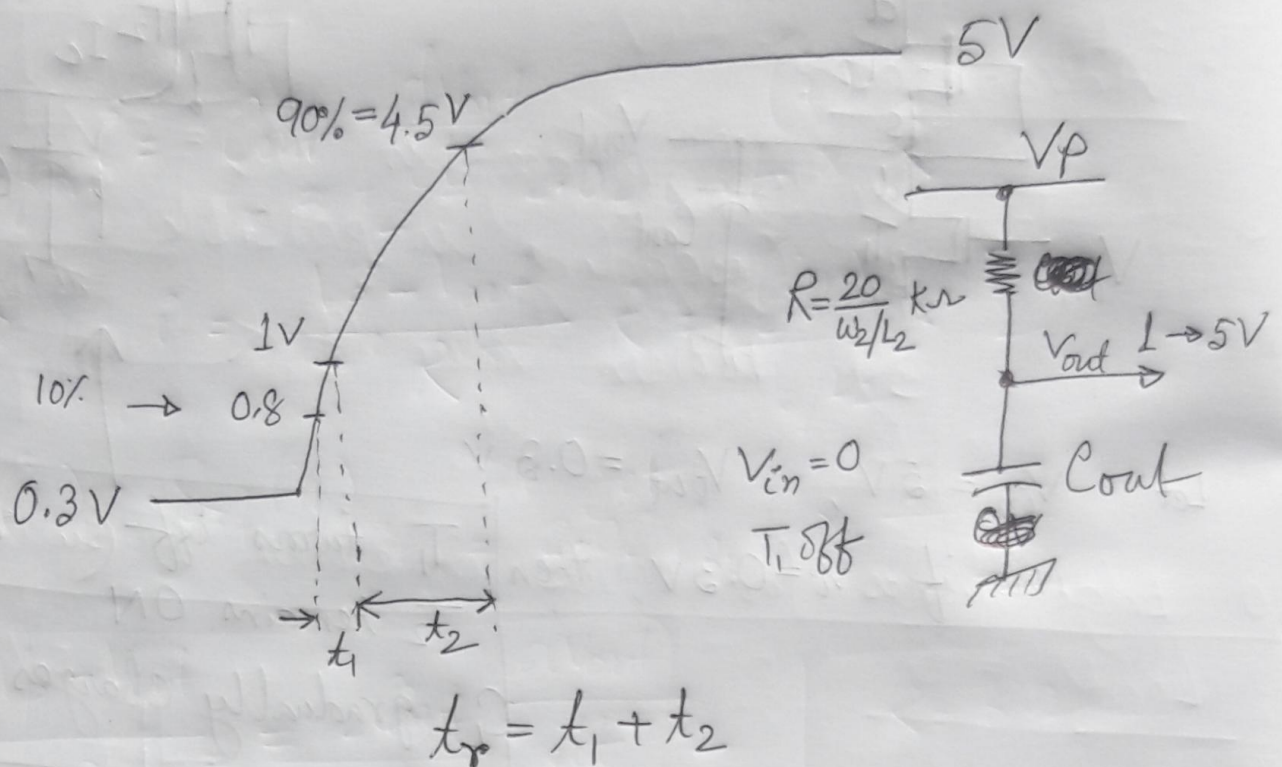

During output rise

when

Case (i) T_2 is saturated, $V_{out} = 0.8$ to $1V$

Case (ii) T_2 is in resistive region when $V_{out} = 1V$ to $5V$

* Output rises from 0.3 to $5V$.

But we consider 10% to 90% points

$$\text{So } 0.3 + 5 \times 10\% = 0.3 + 0.5 = 0.8V$$

$$5 \times 90\% = 4.5V$$

for less than 10% and more than 90% rise, it takes long time to settle down.

Therefore, we ignore those cases.

(i) When $V_{out} = 0.8$ to 1.0 Volt

$$V_{ds} = V_d - V_s = 5 - 0.8 = 4.2$$

$$V_{gs} - V_{td} = 0 + 4 = 4$$

$$\therefore V_{ds} > V_{gs} - V_{td}$$

So T_2 is in satⁿ region

(ii) When $V_{out} = \underline{1.0}$ to 4.5

$$V_{ds} = V_d - V_s = 5 - 1 = 4 \text{ or less}$$

$$V_{gs} - V_{td} = 0 + 4 = 4$$

$\therefore V_{ds} \leq V_{gs} - V_{td}$, So T_2 is in resistive

$$t_r = t_1 + t_2 \approx t_2$$

t_1 very small, and satⁿ current cause t_1 to be very low

So resistive region

$$R = \frac{\text{pinch-off voltage}}{\text{pinch-off current}}$$

$$= \frac{(V_{gs} - V_{td})}{\frac{\epsilon \mu_n}{D} \times \frac{W_2}{L_2} \times \frac{1}{2} (V_{gs} - V_{td})^2}$$

$$= \frac{(0+4)}{25 \times 10^{-6} \times \frac{W_2}{L_2} \times \frac{1}{2} (0+4)^2} = \frac{20 \times 10^3}{W_2/L_2} \Omega$$

$$R = \frac{20}{W_2/L_2} \text{ k}\Omega$$

Again $i = C_{out} \frac{dV_{out}}{dt} \dots (i)$

$$\Rightarrow i = \frac{V_p - V_{out}}{R} \dots (ii)$$

From (i) & (ii), we get

$$\frac{V_p - V_{out}}{R} = C_{out} \frac{dV_{out}}{dt}$$

$$\Rightarrow \frac{dt}{RC_{out}} = \frac{dV_{out}}{V_p - V_{out}}$$

$$\int \frac{dt}{RC_{out}} = \int \frac{dV_{out}}{V_p - V_{out}}$$

Say $\ln K =$

$$\Rightarrow \frac{t}{RC_{out}} = -\ln(V_p - V_{out}) - \ln K$$

$$\Rightarrow \frac{-t}{RC_{out}} = \ln K(V_p - V_{out})$$

$$\therefore K(V_p - V_{out}) = e^{-t/RC_{out}} \dots (iii)$$

Now when $t=0$, $V_{out} = V_i$ $V_i = \text{initial voltage across Capacitor } C_{out}$

$$\therefore K(V_p - V_i) = e^{-0/RC_{out}} = 1$$

$$\therefore K = \frac{1}{V_p - V_i}$$

putting value of K in eqnⁿ(iii), we get

$$\frac{1}{V_p - V_i} (V_p - V_{out}) = e^{-t/RC_{out}}$$

$$\Rightarrow V_p - V_{out} = (V_p - V_i) e^{-t/RC_{out}}$$

$$\Rightarrow \boxed{V_{out} = V_p - (V_p - V_i) e^{-t/RC_{out}}} \dots (iv)$$

Now at time $t = t_2$ $V_{out} = 4.5V$,
and initial voltage of $1V$ in Eqn (iv)

$$4.5 = 5 - (5 - 1) e^{-t_2/RC_{out}}$$

$$\Rightarrow 4 e^{-t_2/RC_{out}} = 5 - 4.5 = 0.5$$

$$\Rightarrow e^{-t_2/RC_{out}} = \frac{0.5}{4}$$

$$\Rightarrow \log_e e^{-t_2/RC_{out}} = \log_e \left(\frac{0.5}{4} \right)$$

$$\Rightarrow -t_2/RC_{out} = -2.08$$

$$\therefore t_2 = 2.08 R C_{out}$$

Therefore, $t_r \approx t_2 = 2.08 C_{out} \times R$

putting value of $R = \frac{20}{W_2/L_2} K\Omega$

We get $t_r = 2.08 C_{out} \times \frac{20}{W_2/L_2}$

$$t_r = \frac{42 C_{out}}{W_2/L_2} ns$$

$$R = K\Omega$$

$$C_{out} = \text{pico Farad}$$

$$R C_{out} = K \times \text{pico} = 10^{-9} = n$$

$$\frac{t_r}{t_f} = \frac{6K}{5}$$

$$\Rightarrow t_f = \frac{5 t_r}{6K} = \frac{5}{6K} \times \frac{42 C_{out}}{W_2/L_2}$$

$$= \frac{5}{6} \times \frac{(W_2/L_2)}{W_1/L_1} \times \frac{42 C_{out}}{(W_2/L_2)}$$

$$t_f = \frac{35 C_{out}}{W_1/L_1}$$