

Noise Margin

V_{IL} : Highest voltage reliably recognized as logic LOW

V_{OL} : Nominal logic LOW voltage generated by a stage

V_{IH} : Lowest voltage reliably recognized as logic HIGH


V_{OH} : Nominal logic HIGH voltage generated by a stage

Say $V_{in} = 1.5$

in NMOS, $V_{gs} = 1.5$
 $V_{ds} = 4.5$

$$V_{gs} - V_t = 1.5 - 1 = 0.5 < V_{ds}$$

So NMOS in Saturation

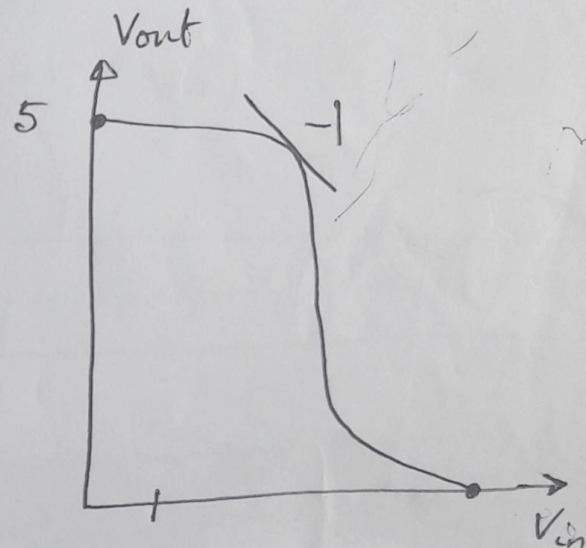


PMOS

$$V_{sg} = V_p - V_{in} = 5 - 1.5 = 3.5$$

$$V_{sd} = V_p - V_{out} = 5 - 4.5 = 0.5$$

$$\therefore V_{sd} < V_{sg} - V_t$$

So PMOS in Resistive

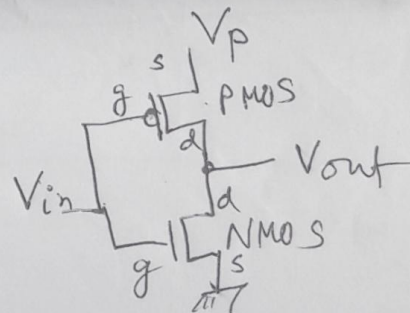

$$\therefore I_{P(res)} = I_{N(sat)}$$

$$\frac{\epsilon \cdot \mu_p}{D} \cdot \frac{W_p}{L_p} \left[(V_{sg} - V_{tp}) V_{sd} - \frac{V_{sd}^2}{2} \right]$$

$$= \frac{\epsilon \mu_n}{D} \cdot \frac{W_N}{L_N} \cdot \frac{1}{2} (V_{gs} - V_{tn})^2$$

We know $\mu_p = \frac{1}{2} \mu_n$

Let $\frac{W_p}{L_p} = 2 \cdot \frac{W_N}{L_N}$

$$\therefore (V_{gs} - V_{tp})V_{sd} - \frac{V_{sd}^2}{2} = \frac{1}{2}(V_{gs} - V_{tn})^2$$

$$\Rightarrow 2(V_p - V_i - V_{tp})(V_p - V_o) - (V_p - V_o)^2 = (V_i - V_{tn})^2$$

$$\Rightarrow \frac{(V_p - V_o)^2}{x^2} - \frac{2(V_p - V_o)(V_p - V_i - V_{tp})}{x} + (V_i - V_{tn})^2 = 0$$

$$\therefore V_p - V_o = \frac{+2(V_p - V_i - V_{tp}) \pm \sqrt{4(V_p - V_i - V_{tp})^2 - 4(V_i - V_{tn})^2}}{2 \cdot 1}$$

$$\Rightarrow \cancel{V_p} - V_o = \cancel{V_p} - V_i - V_{tp} \pm \sqrt{(V_p - V_i - V_{tp})^2 - (V_i - V_{tn})^2}$$

$$\Rightarrow V_o = V_i + V_{tp} \pm \sqrt{(\cancel{V_p} - \cancel{V_i} - V_{tp} + \cancel{V_i} - V_{tn}) \times (\cancel{V_p} - \cancel{V_i} - V_{tp} - \cancel{V_i} + V_{tn})}$$

$$= V_i + V_{tp} \pm \sqrt{(V_p - V_{tp} - V_{tn})(V_p - 2V_i - V_{tp} + V_{tn})}$$

Differentiating w.r.t. V_i

$$\therefore \frac{dV_o}{dV_i} = 1 + 0 + (V_p - V_{tp} - V_{tn})^{\frac{1}{2}} \cdot \frac{1}{2} \cdot \frac{-2(V_p - 2V_i - V_{tp} + V_{tn})}{(V_p - V_{tp} - V_{tn})^{\frac{1}{2}}}$$

$$\Rightarrow \text{Putting } \frac{dV_o}{dV_i} = -1$$

$$-1 = +1 - \frac{\sqrt{V_p - V_{tp} - V_{tn}}}{\sqrt{V_p - 2V_i - V_{tp} + V_{tn}}}$$

$$\therefore 4V_p - 8V_i - 4V_{tp} + 4V_{tn} = V_p - V_{tp} - V_{tn}$$

$$\Rightarrow 3V_p - 3V_{tp} + 5V_{tn} = 8V_i$$

$$\therefore V_i = \frac{3V_p - 3V_{tp} + 5V_{tn}}{8} = V_{IL}$$

putting $V_p = 5$
 $V_{tp} = 1$
 $V_{tn} = 1$

$$V_{IL} = \frac{3 \cdot 5 - 3 \cdot 1 + 5 \cdot 1}{8} = \frac{15 - 3 + 5}{8} = \frac{17}{8} = 2.13 \text{ V}$$

So Noise Margin for low

$$= V_{IL} - V_{OL} = 2.13 - 0 = 2.13 \text{ volts}$$

Similarly $V_{IH} = \frac{5V_p - 5V_{tp} + 3V_{tn}}{8}$

$$V_{IH} = \frac{25 - 5 + 3}{8} = \frac{23}{8} = 2.875$$

$$\therefore NM(1) = 5 - 2.875 = 2.125 \approx 2.13 \text{ V}$$